

**ANALOG & DIGITAL ELECTRONICS
(ELE2102)**

Time Allotted : 2½ hrs

Full Marks : 60

Figures out of the right margin indicate full marks.

*Candidates are required to answer Group A and
any 4 (four) from Group B to E, taking one from each group.*

Candidates are required to give answer in their own words as far as practicable.

Group – A

1. Answer any twelve: **12 × 1 = 12**

Choose the correct alternative for the following

- (i) A zero crossing detector circuit generates
(a) triangular waveform (b) sinusoidal waveform
(c) sawtooth waveform (d) square waveform
- (ii) If A is the open loop gain and β is the feedback path gain then the closed loop gain AF with feedback of a voltage series amplifier is given by
(a) $AF = A/\beta$ (b) $AF = A*\beta$
(c) $AF = A*(1+A\beta)$ (d) $AF = A/(1+A\beta)$
- (iii) To avoid false triggering, the RESET pin of 555 timer is generally connected to
(a) Threshold (b) Trigger
(c) Ground (d) $+V_{CC}$
- (iv) Which of the following oscillators uses one inductor and two capacitors in the feedback circuit?
(a) Hartley oscillator (b) Phase shift oscillator
(c) Wien bridge oscillator (d) Colpitts oscillator.
- (v) Minimization of the function $Y=A + AC$ will result into
(a) 0 (b) A (c) 1 (d) AC
- (vi) Minimum number of NAND gates required to realize an XOR gate is
(a) 3 (b) 4 (c) 2 (d) 5
- (vii) Which of the following is not a type of sequential circuit?
(a) Latch (b) Multiplexer (c) Flip-Flop (d) Counter.
- (viii) What happens to a JK flip-flop when both J and K inputs are set to 1?
(a) The output resets to 0 (b) The output toggles
(c) The output sets to 1 (d) The output remains unchanged.
- (ix) What is the modulus of a counter that counts from 0 to 15?
(a) 8 (b) 16 (c) 32 (d) 6.

- (x) The loop gain of a 3-stage RC phase shift oscillator should be
 (a) 29 (b) 3 (c) 2 (d) 1

Fill in the blanks with the correct word

- (xi) A transistor acts as an amplifier in the _____ region.
 (xii) The ability of certain materials to generate an ac voltage in response to mechanical stress is known as _____ effect.
 (xiii) 2's complement of the number $(1010101)_2$ is _____.
 (xiv) Race around condition occurs in _____ flip flop.
 (xv) The number of clock pulses required to shift the data completely out of a 4-bit shift register is _____.

Group - B

2. (a) The silicon transistor shown in Fig.1 has $\beta = 75$ and collector voltage $V_c = 9V$. Determine the ratio of R_B and R_C . [[CO1](Analyse/IOCQ)]

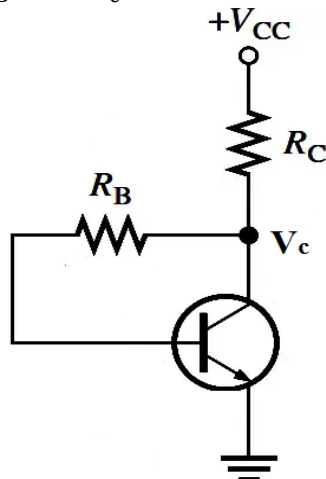


Fig.1

- (b) Calculate the values of I , I_Z and I_L for the circuit shown in Fig.2. It is given that breakdown voltage of the zener diode is 4.5V, $R_L = 1.5\text{ k}\Omega$ and $R = 1\text{ k}\Omega$.

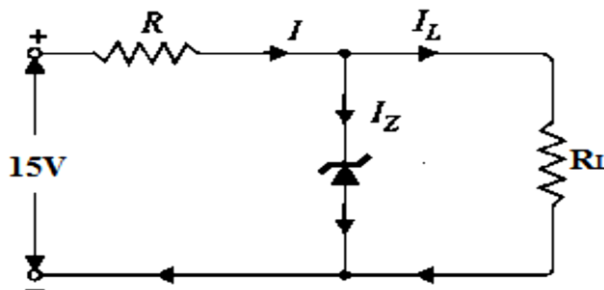


Fig.2

[[CO1](Analyse/IOCQ)]

- (c) Design an inverting adder circuit to obtain an output voltage V_o where

$$V_o = -(2V_1 + V_2)$$
 where V_1 and V_2 are the input voltages.

[[CO2](Create/HOCQ)]

4 + 4 + 4 = 12

3. (a) Determine the Q-point for the dual input, balanced-output differential amplifier shown in Fig.3. The following specifications are given: $R_C = 2.2 \text{ k}\Omega$, $R_E = 4.7 \text{ k}\Omega$, $+V_{CC} = 10\text{V}$, $-V_{EE} = -10 \text{V}$, $\beta = 100$ and $V_{BE} = 0.7\text{V}$. [[CO1](Apply/IOCQ)]

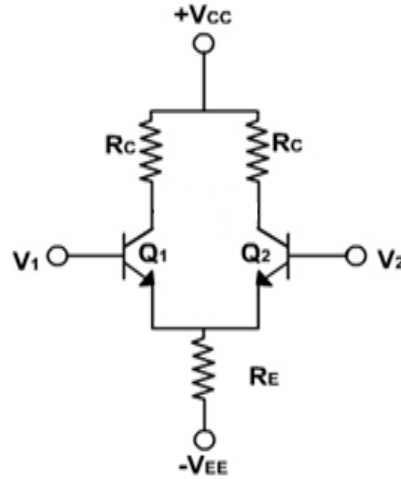


Fig.3

- (b) Derive the expression of output voltage for a basic integrator circuit using operational amplifier. Mention the problems in the circuit and how do we modify the circuit to overcome them? [[CO1](Understand/LOCQ)]
- (c) Explain the working principle of the circuit shown in Fig.4. Also draw its transfer characteristics. [[CO2](Evaluate/HOCQ)]

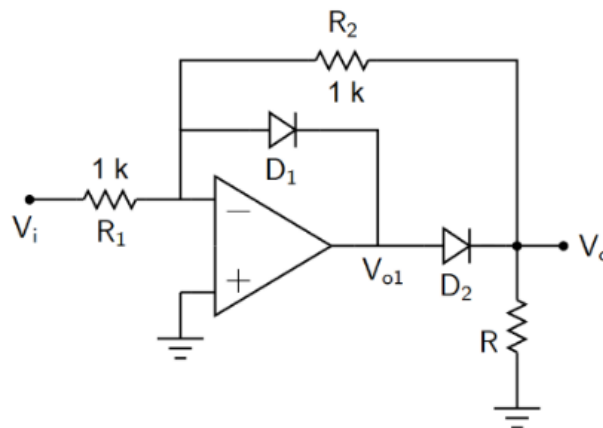


Fig.4

$$4 + 4 + 4 = 12$$

Group - C

4. (a) Draw a neat circuit diagram of a monostable multivibrator using operational amplifier. Explain its principle of operation. Draw the output and capacitor voltage waveforms. Derive the expression of timing period. [[CO3](Analyse/IOCQ)]
- (b) Design a voltage controlled oscillator circuit with nominal frequency, $f_o = 25\text{kHz}$ for a control voltage $V_c = 6\text{V}$. Consider supply voltage of IC LM566 $V_{CC} = 12\text{V}$. [[CO3](Apply/IOCQ)]
8 + 4 = 12
5. (a) Draw a neat diagram of Colpitts oscillator and derive the expression of oscillation frequency. [[CO3](Analyse/IOCQ)]
- (b) Design an RC phase shift oscillator with oscillation frequency $f_o = 200 \text{ Hz}$. [[CO3](Apply/IOCQ)]

(c) State and explain Barkhausen criteria.

[[CO3](Remember/LOCQ)]

4 + 4 + 4 = 12

Group - D

6. (a) Simplify the following Boolean function F and implement the logic diagram of the circuit using NAND gates only.

$$F = \sum_m(0,4,8,9,10,11,12,14)$$

[[CO4](Understand/LOCQ)]

(b) Construct a 5-to-32 line decoder using four 3-to-8 line decoder with enable input and a 2-to-4 line decoder. Use block diagrams for the components. [[CO5](Apply/IOCQ)]

(c) Create a single bit magnitude comparator circuit using NAND gate only.

[[CO5](Create/HOCQ)]

4 + 5 + 3 = 12

7. (a) Design a full adder circuit with three inputs A,B,C_i and two outputs S,C_o using NAND gates. The circuit adds A+B+ C_i, where C_i= input carry, C_o = output carry, S = sum.

[[CO5](Apply/IOCQ)]

(b) Construct an 8:1 multiplexer using 2:1 multiplexer only. Use block diagrams.

[[CO5](Apply/IOCQ)]

(c) Design a full subtractor using two half subtractors and one external gate.

[[CO5](Create/HOCQ)]

4 + 5 + 3 = 12

Group - E

8. (a) Explain how JK flip flop can be used as a frequency divider.

[[CO6](Analyse/HOCQ)]

(b) Construct a D flip-flop using J-K flip-flop.

[[CO6](Apply/IOCQ)]

(c) Develop the characteristic equation of T flip flop.

[[CO6](Create/HOCQ)]

4 + 5 + 3 = 12

9. (a) Explain with necessary logic diagram the working of a 3 bit parallel in serial out (PISO) shift register.

[[CO6](Remember/LOCQ)]

(b) Design and implement a Mod-6 synchronous up counter using JK flip flop.

[[CO6](Create/HOCQ)]

6 + 6 = 12

Cognition Level	LOCQ	IOCQ	HOCQ
Percentage distribution	18.75	53.13	28.12