

ANALOG VLSI IC DESIGN
(VLSI 5201)

Time Allotted : 2½ hrs

Full Marks : 60

Figures out of the right margin indicate full marks.

*Candidates are required to answer Group A and
any 4 (four) from Group B to E, taking one from each group.*

Candidates are required to give answer in their own words as far as practicable.

Group - A

1. Answer any twelve:

12 × 1 = 12

Choose the correct alternative for the following

- (i) Linear amplification can be obtained from common-source MOSFET amplifier when biased in
 - (a) Saturation region
 - (b) Linear region
 - (c) Subthreshold region
 - (d) only exactly at $V_{DS} = V_{DS(sat)}$
- (ii) Practical current mirror circuits deviate from ideal behaviour due to
 - (a) Channel-length modulation effect
 - (b) Threshold voltage offset between two transistors
 - (c) Imperfect geometrical matching
 - (d) All of the above
- (iii) The substrate of the NMOS transistor is connected to
 - (a) Most negative supply in the system
 - (b) ground
 - (c) threshold voltage
 - (d) most positive supply in the system
- (iv) Multiplication in the time domain corresponds to
 - (a) Multiplication in the frequency domain
 - (b) Convolution in the frequency domain
 - (c) Addition in the frequency domain
 - (d) Division in the frequency domain
- (v) For a good design of MOSFET, the relationship between the thermal noise arising from the gate resistance and the channel should satisfy
 - (a) $4kT \frac{R_G}{3} \ll \frac{4kT\gamma}{g_m}$
 - (b) $4kT \frac{R_G}{3} \gg \frac{4kT\gamma}{g_m}$
 - (c) $4kT \frac{R_G}{3} \ll 4kT\gamma g_m$
 - (d) $4kT \frac{R_G}{3} = \frac{4kT\gamma}{g_m}$
- (vi) The error tolerance at the output of S/H (Sample / Hold) depends on the amplifier's
 - (a) Offset
 - (b) Gain Error
 - (c) Linearity
 - (d) All of the above
- (vii) A 4-bit R-2R digital-to-analog converter has a reference of 5volts. What is the analog output for the input code 0101
 - (a) 0.3125V
 - (b) 3.125V
 - (c) 0.78125V
 - (d) -3.125V
- (viii) Considering VREF = 1V, as the digital word increases by 1 bit, the output of the ideal 3-bit DAC should jump by
 - (a) 0.25V
 - (b) 0.0625V
 - (c) 0.33V
 - (d) 0.125V
- (ix) The frequency of the signal applied to the switched-capacitor circuit should satisfy the the criteria
 - (a) $f_{signal} \ll f_{clock}$
 - (b) $f_{signal} \gg f_{clock}$
 - (c) $f_{signal} = 2f_{clock}$
 - (d) $f_{clock} = 2f_{signal}$
- (x) The number of inverter stages in a ring oscillator is given by
 - (a) 1
 - (b) 2
 - (c) 3
 - (d) Anyone of (a), (b), (c)

Fill in the blanks with the correct word

- (xi) An ideal differential amplifier should have common-mode voltage gain ____.
- (xii) A good current mirror should have ____ (high / low) output resistance.
- (xiii) Integral Nonlinearity (INL) is one important ____ (static / dynamic) characteristics of the DAC.
- (xiv) The full form of PLL is ____.
- (xv) Switched capacitors accumulate the _____ noise of the switches.

Group - B

2. (a) Briefly explain the voltage transfer characteristics of a basic resistive load differential amplifier circuit. *[(CO2)(Understand/LOCQ)]*
 (b) Deduce the ICMR of this type of circuit. *[(CO2)(Analyze/LOCQ)]*
 (c) Consider the circuit in Fig. 1 in which M2 is twice as wide as M1. Calculate the small-signal gain if the bias values of V_{in1} and V_{in2} are equal. *[(CO2)(Evaluate/HOCQ)]*

 


Fig. 1

4 + 5 + 3 = 12

3. (a) Briefly explain the current –voltage characteristics of a current sink and source. *[(CO1)(Apply/LOCQ)]*
 (b) Derive the small-signal voltage gain of a push-pull amplifier from its small-signal equivalent circuit. *[(CO2)(Analyze/LOCQ)]*
 (c) Consider a discrete common-source MOSFET amplifier shown in Fig. 2. Determine its small-signal voltage gain, its input resistance and the largest allowable input signal. The transistor has $V_{th} = 1.5V$, $k_n'(W/L) = 0.25mA/V^2$, and $V_A = 50V$. Assume the coupling capacitors to be sufficiently large so as to act as short circuits at the signal frequencies of interest. *[(CO1)(Evaluate/HOCQ)]*

 


Fig. 2

4 + 5 + 3 = 12

Group - C

4. (a) Briefly discuss the effects of nonlinearity in RF circuits. *[(CO3)(Understand/LOCQ)]*
 (b) An analog multiplier mixes its two inputs $x_1(t)$ and $x_2(t)$, ideally producing an output $y(t) = kx_1(t)x_2(t)$, where k is a constant. Assume, $x_1(t) = A_1\cos\omega_1 t$ and $x_2(t) = A_2\cos\omega_2 t$. (i) If the mixer is ideal, determine the frequency components, (ii) If the input port sensing $x_2(t)$ suffers from third-order nonlinearity, determine the output frequency components. *[(CO3)(Apply/LOCQ)]*
 (c) In most circuits, one terminal of the inductor(s) is at ac ground. Which terminal of the structure should be grounded in Fig. 3. *[(CO3)(Apply/LOCQ)]*

 


Fig. 3

4 + 5 + 3 = 12

5. (a) Briefly explain the phenomenon of cross-modulation. *[(CO3)(Understand/LOCQ)]*

(b) Suppose an interferer contains phase modulation but not amplitude modulation. Does cross modulation occur in this case? Justify. [(CO3)(Apply/IOCQ)]

(c) A Low-Noise amplifier senses a -80dBm signal at 2.410GHz and two -20dBm interferers at 2.420GHz and 2.430GHz . What IIP_3 is required if the InterModulation (IM) must remain 20dB below the signal? For simplicity, assume 50Ω interfaces at the input and output. [(CO3)(Evaluate/HOCQ)]

4 + 3 + 5 = 12

Group - D

6. (a) Explain the *INL* and *DNL* of a digital-to-analog converter graphically. [(CO4)(Understand/LOCQ)]

(b) Determine the *DNL* for the 3-bit nonideal DAC whose transfer curve is shown in the Fig. 4. Assume that $V_{REF} = 5V$. [(CO4)(Apply/IOCQ)]

 


Fig. 4

(c) Draw the *DNL* curve for the 3-bit nonideal DAC. [(CO4)(Evaluate/HOCQ)]

4 + 4 + 4 = 12

7. (a) Determine the resolution for a *DAC* if the output voltage is desired to change in 1mV increments while using a reference voltage of $5V$. [(CO4)(Apply/IOCQ)]

(b) Determine the *INL* for the *ADC* whose transfer curve is illustrated in Fig. 5. Assume that $V_{REF} = 5V$. [(CO4)(Apply/IOCQ)]

 


Fig. 5

(c) Draw the Quantization error (Q_e) in units of *LSBs*. [(CO4)(Evaluate/HOCQ)]

4 + 4 + 4 = 12

Group - E

8. (a) Mention the advantages of the switched-capacitor circuits. [(CO5)(Understand/LOCQ)]

(b) Emulate the resistor equivalent of the parallel switched capacitor circuit. [(CO5)(Apply/IOCQ)]

(c) Design a parallel switched capacitor circuit which will emulate $1\text{M}\Omega$ resistor and the clock frequency is 100KHz . Determine the value of capacitance. [(CO5)(Apply/LOCQ)]

4 + 5 + 3 = 12

9. (a) Explain the Barkhausen criteria for oscillation.

[(CO6)(Understand/LOCQ)]

(b) Analyze the stability of two-pole amplifier system with proper graphical illustration.

[(CO6)(Analyze/IOCQ)]

(c) Determine the minimum voltage required voltage gain per stage in the four-stage oscillator shown in Fig. 6. How many signal phases are provided by the circuit?

[(CO6)(Evaluate/HOCQ)]

 


Fig. 6

$$4 + 3 + 5 = 12$$

Cognition Level	LOCQ	IOCQ	HOCQ
Percentage distribution	36.46	38.54	25