

**ELECTRICAL & ELECTRONICS MEASUREMENTS
(AEI2103)**

Time Allotted : 2½ hrs

Full Marks : 60

Figures out of the right margin indicate full marks.

*Candidates are required to answer Group A and
any 4 (four) from Group B to E, taking one from each group.*

Candidates are required to give answer in their own words as far as practicable.

Group – A

1. Answer any twelve:

12 × 1 = 12

Choose the correct alternative for the following

- (i) The full scale deflection current of the basic moving coil of a PMMC type voltmeter is 1 mA. The sensitivity of it is given by,
(a) 500Ω/V (b) 1000Ω/V (c) 1500 Ω/V (d) 200 Ω/V
- (ii) A resistance of a moving coil ammeter is 30 Ω. To extend the range from 1mA to 10mA, the required value of shunt is
(a) 5.55 Ω (b) 7.25 Ω (c) 4.35 Ω (d) 3.33 Ω
- (iii) Which of the following is known as the transfer instrument among the following indicating instruments?
(a) Moving Iron (b) Electrodynamicometer
(c) Electrostatic (d) PMMC
- (iv) Unknown frequency is measured by using
(a) De Sauty's Bride (b) Wien's Bridge
(c) Wheatstone Bridge (d) Kelvin's Double Bridge
- (v) High resistance is measured by
(a) Megger (b) Ammeter-voltmeter method
(c) Substitution method (d) Kelvin's Bridge
- (vi) An impedance has magnitude 200 Ω and phase angle 80°. The reactance of the impedance is given by
(a) 197 Ω (b) 135 Ω (c) 183 Ω (d) 127 Ω
- (vii) In a CRO the brightness control is adjusted by adjusting the potential applied to the
(a) Cathode (b) First focussing anode
(c) Horizontal deflection amplifier (d) Grid

- (viii) A FET input stage is used in electronic voltmeters because
 (a) It provides high input impedance (b) It provides low input impedance
 (c) It is cheap (d) None of these
- (ix) A circuit which can be used to convert a sine waveform into a pulse waveform is
 (a) Non-inverting amplifier (b) Inverting amplifier
 (c) Summing amplifier (d) Schmitt Trigger
- (x) What will be the Hex code to display 'E' in the 7 segment display unit?
 (a) 3F (b) 67 (c) 06 (d) 79

Fill in the blanks with the correct word

- (xi) Expression of nominal ratio of a current transformer is _____.
- (xii) Precision of an instrument is expressed in terms of _____.
- (xiii) In a pure capacitance, voltage across it lags current by ____.
- (xiv) In spectrum analyzer the attenuation level of a given signal is expressed in _____.
- (xv) In ramp type DVM the stop pulse for conversion is produced by _____.

Group - B

2. (a) Show how the angular displacement of the moving system is proportional to the current through it for PMMC instrument. [[CO2](Analyse/IOCQ)]
- (b) What are the advantages of PMMC instrument? [[CO1](Remember/LOCQ)]
- (c) A PMMC instrument has a coil of dimensions 18mm x 13mm. The flux density in the air gap is 2×10^{-3} Wb/m² and the spring constant is 0.22×10^{-6} Nm/rad. Determine the number of turns required to produce an angular deflection of 90° when a current of 7 mA is flowing through the coil. [[CO2](Evaluate/HOCQ)]
5 + 3 + 4 = 12
3. (a) Derive the expression of deflecting torque of moving iron instrument and hence comment on the nature of the scale for spring controlled instrument. [[CO2](Analyse/IOCQ)]
- (b) The inductance of a moving iron ammeter with a full scale deflection of 90° at 1.5 A is given by
 $L = (300 + 50\theta - 4\theta^2 - \theta^3)$ μH, where θ is the deflection in radian from zero position. Find out the angular deflection of the pointer for a current of 1 A. [[CO2](Evaluate/HOCQ)]
- (c) With neat diagram show why the scale of an indicating instrument is non-linear when controlling torque is produced by gravity controlled scheme. [[CO1](Understand/LOCQ)]
6 + 3 + 3 = 12

Group - C

4. (a) Find the expression of self inductance along with internal resistance of an unknown coil by Maxwell's Inductance- Capacitance Bridge. How the balance of the bridge is achieved? [[CO3](Analyse/IOCQ)]

- (b) Draw the phasor diagram of Maxwell's Inductance- Capacitance Bridge. [[CO3](Understand/LOCQ)]
- (c) In an a.c. bridge 'abcd', between a & b an unknown coil along with its series resistance (r_1) is connected in series with a resistance R_1 . Pure resistance R_3 and R_4 are connected between b & c and c & d respectively. Between d & a, a standard variable inductance (L_2) with its series resistance (R_2) is connected. An a.c. supply is connected between a & c. At balance, $R_3 = R_4 = 110 \Omega$, $L_2 = 52.8 \text{ mH}$, $R_2 = 38.7 \Omega$ and $R_1 = 5.36 \Omega$. Find the self inductance of the unknown coil along with its resistance. [[CO3](Evaluate/HOCQ)]
(4 + 1) + 3 + 4 = 12
5. (a) Find the balance condition of an a.c. bridge having impedances Z_1, Z_2, Z_3 and Z_4 in its four arms. [[CO3](Analyse/IOCQ)]
- (b) An a.c. bridge 'abcd' has impedances $90 \Omega \angle 20^\circ$ in ab arm, 60Ω at bc arm, $20 \Omega \angle 10^\circ$ at cd arm and $30 \Omega \angle 30^\circ$ at da arm having supply voltage connected between a and c. Check whether the bridge is in balanced condition or not? [[CO3](Evaluate/HOCQ)]
- (c) Showing the circuit diagram of De Sauty's bridge draw the phasor diagram of it. [[CO3](Remember/LOCQ)]
5 + 3 + 4 = 12

Group - D

6. (a) Using a Schmitt Trigger and ramp generator design a time base circuit for CRO. Explain the operation of it. [[CO5](Analyse/IOCQ)]
- (b) What is the significance of the term 'TIMES/DIV' ? [[CO5](Remember/LOCQ)]
- (c) How brightness of display is controlled in a cathode ray tube? [[CO5](Understand/LOCQ)]
(3 + 4) + 2 + 3 = 12
7. (a) Name the different parts of the focussing section of a cathode ray tube. Explain the operation of the focussing section of it. [[CO5](Analyse/IOCQ)]
- (b) With a neat diagram show how the Lissajous pattern is formed on the CRO screen if two sine waves having same peak to peak voltage, same frequency but phase difference 0° and 90° between them is applied to the vertical and horizontal deflecting plates. [[CO5](Analyser/IOCQ)]
- (c) How phase difference between two sine waves is measured from the displayed Lissajous figure on the CRO screen? [[CO5](Understand/LOCQ)]
(1 + 3) + 4 + 4 = 12

Group - E

8. (a) Draw the block diagram of a digital frequency meter for the measurement of frequency of an ac signal. Hence show the timing diagram of it. [[CO6](Analyse/IOCQ)]
- (b) Explain the operation of digital frequency meter for the measurement of unknown frequency. [[CO6](Understand/LOCQ)]
- (c) Show the connection of time base and display unit for multiple ranges of the digital frequency meter. [[CO6](Remember/LOCQ)]
(2 + 2) + 6 + 2 = 12

9. (a) Design a circuit for 3 bit successive approximation type digital voltmeter .
[[CO6](Remember/LOCQ)]
- (b) Show the steps to convert 4.9V by 3 bit approximation type DVM using necessary calculations.
[[CO6](Analyse/IOCQ)]
- (c) What is the percentage error in the measurement of 4.9 V by this DVM?
[[CO6](Analyse/IOCQ)]
- 4 + 6 + 2 = 12**
-

Cognition Level	LOCQ	IOCQ	HOCQ
Percentage distribution	35.41	50	14.58