

**DIGITAL SYSTEMS DESIGN
(ECE2102)**

Time Allotted : 2½ hrs

Full Marks : 60

Figures out of the right margin indicate full marks.

*Candidates are required to answer Group A and
any 4 (four) from Group B to E, taking one from each group.*

Candidates are required to give answer in their own words as far as practicable.

Group – A

1. Answer any twelve:

12 × 1 = 12

Choose the correct alternative for the following

- (i) The expression $Y=(A+B)(B+C)(C+A)$ shows the _____ operation.
(a) AND (b) POS (c) SOP (d) NAND
- (ii) The simplified form of the Boolean expression $(X+Y+XY)(X+Z)$ is
(a) $X+Y+Z$ (b) $XY+YZ$ (c) $X+YZ$ (d) $XZ+Y$
- (iii) The code used for labelling cells of the K-map is
(a) natural BCD (b) Hexadecimal
(c) Gray (d) Octal
- (iv) The maxterm corresponding to decimal 9 is
(a) $AB'C'D$ (b) $A+B'+C'+D$
(c) $A'+B+C+D'$ (d) $A'BCD'$
- (v) How many NOT gates are required for the construction of a 4-to-1 multiplexer?
(a) 3 (b) 4 (c) 2 (d) 5
- (vi) Which of the following combinational circuits is used to convert a binary input into a unique output line based on the input code, and has n inputs and 2^n outputs?
(a) Multiplexer (b) Encoder
(c) Demultiplexer (d) Decoder
- (vii) A universal register
(a) accepts serial input (b) accepts parallel input
(c) give serial and parallel outputs (d) is capable of all of the above
- (viii) Which type of counter uses a single global clock signal that is connected to all flip-flops simultaneously?
(a) Asynchronous ripple counter (b) Synchronous counter
(c) Ring counter (d) Johnson counter

- (ix) Resolution of n-bit DAC is given by
 (a) $1/(2^n-1)$ (b) $1/2^n$
 (c) $1/(2^n+1)$ (d) $1/2^{-n}$
- (x) Which type of memory is volatile, meaning its stored data is lost when the power supply is removed?
 (a) ROM (Read-Only Memory) (b) EPROM (Erasable Programmable ROM)
 (c) RAM (Random-Access Memory) (d) EEROM (Electrically Erasable ROM)

Fill in the blanks with the correct word

- (xi) 2's complement of binary number 0101 is _____.
- (xii) Minimum number of 2-input NAND gates required to implement the function $F = (x + y)(Z + W)$ is _____.
- (xiii) Maxterm designation for $A + B + C$ is _____.
- (xiv) A logic circuit that can store one bit of information is a _____.
- (xv) In a positive logic system, the HIGH level is usually represented by _____.

Group - B

2. (a) Simplify the Boolean function by using K-map: $F = \prod M(2, 8, 9, 10, 11, 12, 14)$ and implement the real minimal expression in universal logic. [[CO1](Evaluate/HOCQ)]
- (b) Implement the following Boolean functions using only NAND or NOR gates.
 (i) $F(A, B, C) = AB + AC'(B+C)$
 (ii) $F(A, B, C) = (A+B) + (A+C')(B+C)$ [[CO1](Analyse/IOCQ)]
8 + (2 + 2) = 12
3. (a) (i) Convert the decimal number $(145)_{10}$ to its binary, octal, and hexadecimal equivalents.
 (ii) Using 2's complement arithmetic, perform the following subtraction: $(45)_{10} - (29)_{10}$. Show all steps and the final binary result. [[CO1](Evaluate/HOCQ)]
- (b) Simplify the following Boolean function in both Sum of Products (SOP) and Product of Sums (POS) forms using a 4-variable Karnaugh Map (K-map). The 'd' terms represent don't-care conditions.
 $F(A, B, C, D) = \sum m(0, 2, 4, 6, 8, 10, 12, 14) + d(5, 7, 13, 15)$ [[CO1](Apply/IOCQ)]
(3 + 3) + 6 = 12


Group - C

4. (a) Realize 3-input XOR gate with 4:1 Multiplexer. [[CO3](Apply/IOCQ)]
- (b) Design a 4-to-16 Decoder using Two 3-to-8 Decoders. [[CO3](Evaluate/HOCQ)]
- (c) With the help of a logic diagram and a truth table, explain an Octal to Binary encoder. [[CO2](Apply/IOCQ)]
4 + 4 + 4 = 12

5. (a) Explain the operation of a 4-bit binary ripple carry adder circuit with block schematic. [[CO3](Analyse/HOCQ)]
 (b) Design a 3-bit binary to Gray code converter circuit. [[CO3](Evaluate/HOCQ)]
6 + 6 = 12

Group - D

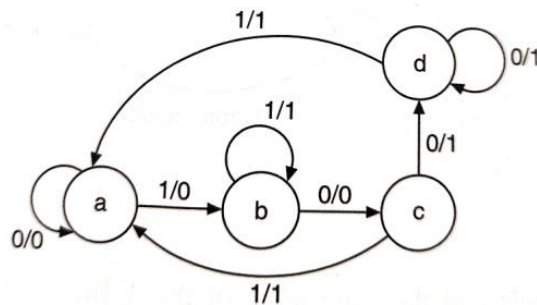6. (a) Draw the circuit diagram of a master-slave J-K flip-flop using all NAND gates and explain the circuit operation. [[CO4](Remember/LOCQ)]
 (b) Draw a neat diagram of a 4-bit Bi-directional shift register using mode control (M). When M is logic zero then left shift and right shift for M is logic one. [[CO5](Remember/LOCQ)]
6 + 6 = 12
7. (a) Define Mealy model of the state diagram of a memory element. [[CO5](Remember/LOCQ)]
 (b) Obtain a reduced state table and reduced state diagram for the sequential machine whose state diagram in given below. [[CO4](Create/HOCQ)]



- (c) How is the state of the memory element specified? [[CO5](Remember/LOCQ)]
2 + 8 + 2 = 12

Group - E

8. (a) Design a 2-input NAND gate using a CMOS inverter. [[CO6](Create/HOCQ)]
 (b) What are ROM and RAM? What are the basic differences between EPROM and EEROM? [[CO6](Remember, Analyze /LOCQ)]
 (c) Design a 3-input NOR gate using RTL logic family. [[CO6](Create/HOCQ)]
4 + 4 + 4 = 12
9. (a) Draw a static RAM cell and explain its operation. [[CO6](Remember/LOCQ)]
 (b) Explain the concepts of fan-in and fan-out for logic families. [[CO6](Remember/LOCQ)]
 (c) Design a basic 2 input TTL NAND gate and explain. [[CO6](Create/HOCQ)]
4 + 4 + 4 = 12

Cognition Level	LOCQ	IOCQ	HOCQ
Percentage distribution	29.17	18.75	52.08

