

NETWORK THEORY
(ECE2104)

Time Allotted : 2½ hrs

Full Marks : 60

Figures out of the right margin indicate full marks.

*Candidates are required to answer Group A and
any 4 (four) from Group B to E, taking one from each group.*

Candidates are required to give answer in their own words as far as practicable.

Group - A

1. Answer any twelve:

12 × 1 = 12

Choose the correct alternative for the following

- (i) If an impedance Z_L is connected across a voltage source V with source impedance Z_S , then for maximum power transfer the load impedance must be equal to
 (a) Source impedance Z_S (b) complex conjugate of Z_S
 (c) real part of Z_S (d) imaginary part of Z_S
- (ii) Quality factor Q of a series resonant circuit is given by
 (a) $(\Delta\omega)\omega_0$ (b) $(\Delta\omega) / \omega_0$
 (c) $\omega_0 / (\Delta\omega)$ (d) $\Delta\omega + \omega_0$
- (iii) A series RLC circuit is overdamped when
 (a) $R^2/4L^2 > 1/LC$ (b) $R^2/4L^2 = 1/LC$
 (c) $R^2/4L^2 < 1/LC$ (d) $R^2/4L^2 \geq 1/LC$
- (iv) Laplace transform of $f(t-a)$ is
 (a) $e^{-as} F(s)$ (b) $e^{as} F(s)$
 (c) $F(s-a)$ (d) $F(s+a)$
- (v) The transform impedance of an inductor is
 (a) L (b) $1/L$ (c) sL (d) $1/sL$
- (vi) The number of twigs in a tree of a graph with n nodes and b branches is
 (a) $n-1$ (b) n (c) $b-n+1$ (d) b
- (vii) Two two-port networks are connected in series. The z-matrix of the single equivalent network is obtained by
 (a) multiplying z-matrices of individual networks (b) adding z- matrices of individual networks
 (c) subtracting z- matrices of individual networks (d) multiplying y- matrices of individual networks
- (viii) Two two-port to be reciprocal (using z parameters), the condition is
 (a) $Z_{11}=Z_{22}$ (b) $Z_{12}=Z_{21}$
 (c) $Z_{11}Z_{22}=Z_{12}Z_{21}$ (d) $Z_{11}+Z_{22}=Z_{12}+Z_{21}$
- (ix) A low pass filter having cut-off frequency f_1 followed by a high pass filter having cut-off frequency f_2 ($f_2 < f_1$) results
 (a) band pass filter (b) low pass filter
 (c) high pass filter (d) band reject filter
- (x) In a source free RC circuit, when the switch is closed the current_____.
 (a) does not vary with time (b) decays with time
 (c) increases with time (d) first decreases and then increases with time


Fill in the blanks with the correct word

- (xi) The Laplace transform of $\delta(t)$ is _____.
- (xii) For a connected graph with 'n' number of nodes and 'b' number of branches, the number of tie-sets will be always _____.
- (xiii) The coefficient of coupling, k between the two coils is given by the formula _____.
- (xiv) The rank of a graph from a network of five nodes is _____.
- (xv) A long time after switching a circuit on with a step, the inductor behaves as a _____.

Group - B


2. (a) Find the value of R_L for maximum power transfer in the circuit. Evaluate the maximum power.

[[CO2](Analyse/IOCQ)]

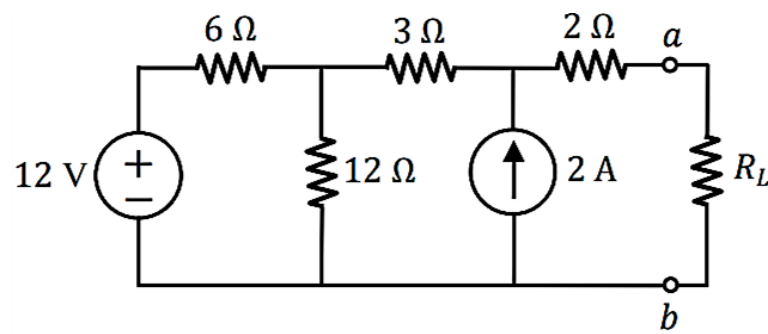


- (b) Determine the condition of maximum power transfer to a load having complex impedance by a voltage source having complex impedance. Consider independent tuning of load resistance and load reactance. [[CO2](Apply/IOCQ)]
8 + 4 = 12

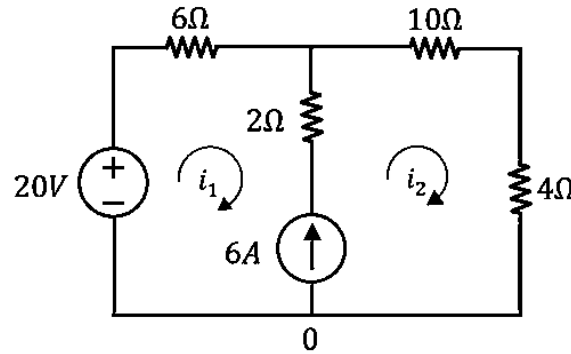3. (a) Find the mesh currents i_1 and i_2 for the given circuit using mesh analysis method. [[CO1](Apply/IOCQ)]



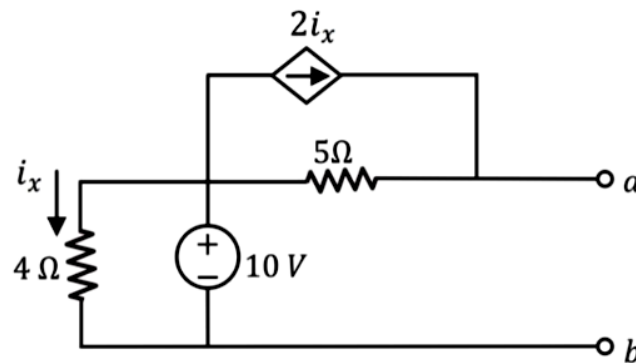
- (b) Find the Thevenin equivalent of the circuit shown in the figure, across the terminals a and b. [[CO2](Understand/LOCQ)]



6 + 6 = 12


Group - C

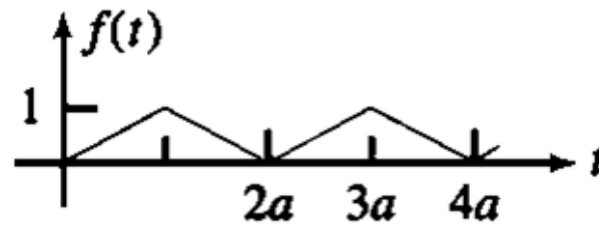4. (a) Define impulse function. Decipher the response if the impulse function is passed through an integrator circuit. Evaluate the Laplace transform of the response. [[CO3](Understand/LOCQ)]
 (b) Evaluate the Laplace transform of the following waveform. [[CO3](Understand/LOCQ)]




6 + 6 = 12

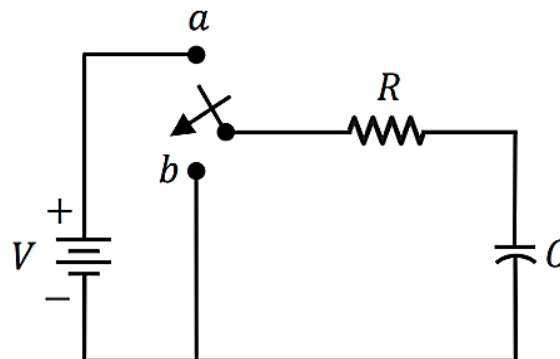5. (a) The circuit is in the steady state with switch in position a. The switch is moved from a to b at $t=0$. Find the current in the resistor. How much energy is dissipated in R during $t=0$ to $t=\infty$. [[CO3](Understand/LOCQ)]



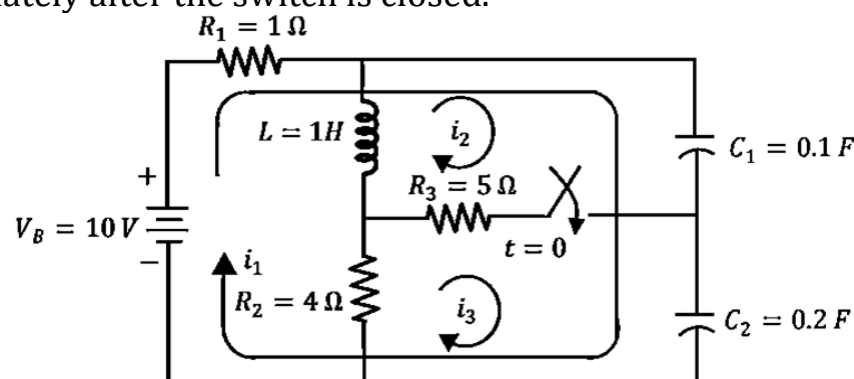- (b) The circuit is in the steady state before $t=0$ when the switch was open. The switch is now closed at $t=0$. Determine the mesh currents i_1 , i_2 and i_3 immediately after the switch is closed. [[CO3](Analyse/IOCQ)]




6 + 6 = 12

Group - D


6. (a) For the following 2-port network, calculate the z-parameters.

[[CO5](Apply/IOCQ)]

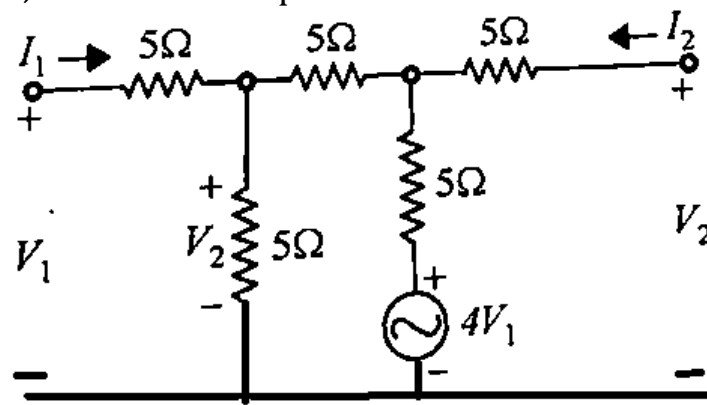

- (b) Find the y and z-matrices of the resistive network of the following figure.


[[CO5](Understand/LOCQ)]

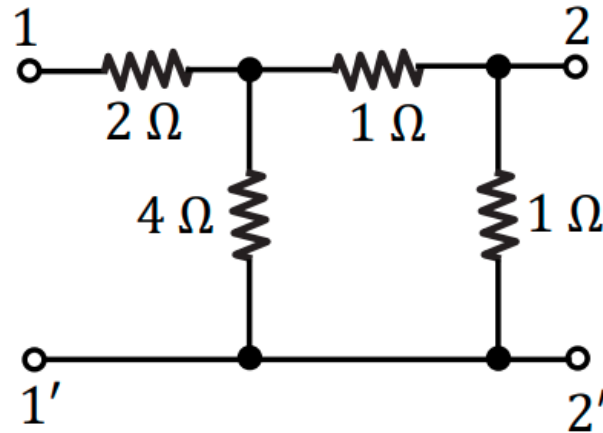

6 + 6 = 12


7. (a) In the following network, write the tie-set matrix and determine the KVL equations. Calculate the loop currents.

[[CO4](Analyse/IOCQ)]

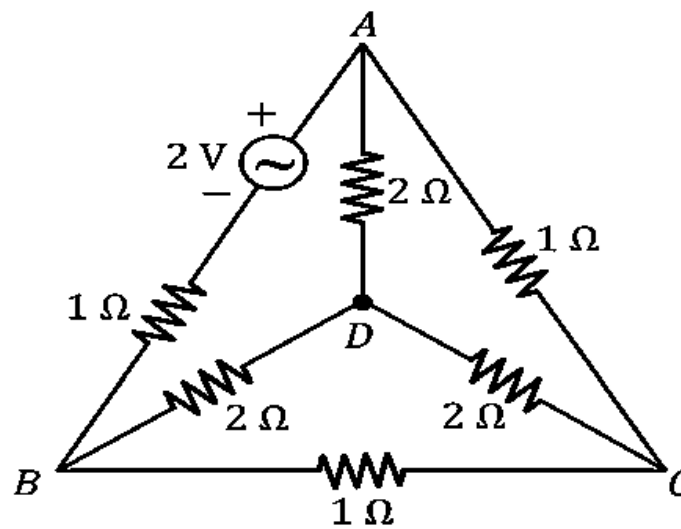

- (b) How many trees are possible for the graph of the network of the figure. Draw any two of them.

[[CO4](Apply/IOCQ)]

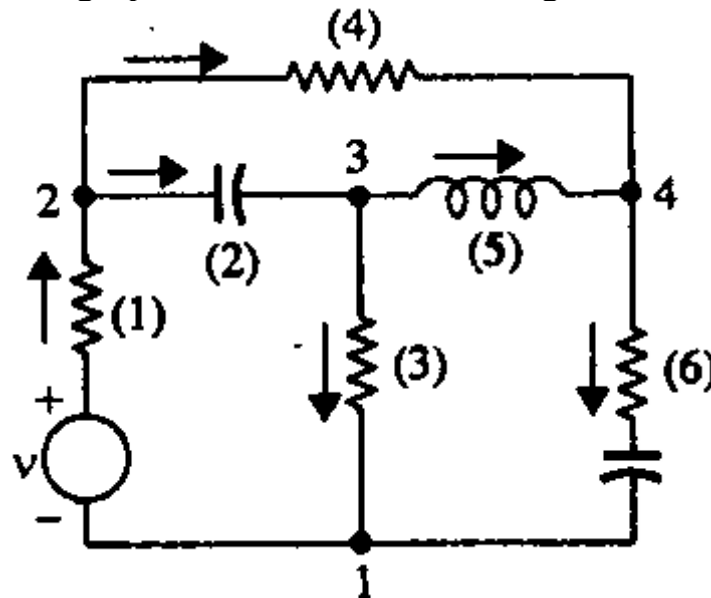

6 + 6 = 12

Group - E

8. (a) Design a 2nd order band pass filter that has a centre frequency of 1 KHz and a band-width of 100 Hz. Take the centre frequency gain to be 2.


[[CO6](Design/HOCQ)]

- (b) Derive the transfer function of a 1st order low pass active filter.


[[CO6](Remember/LOCQ)]

6 + 6 = 12

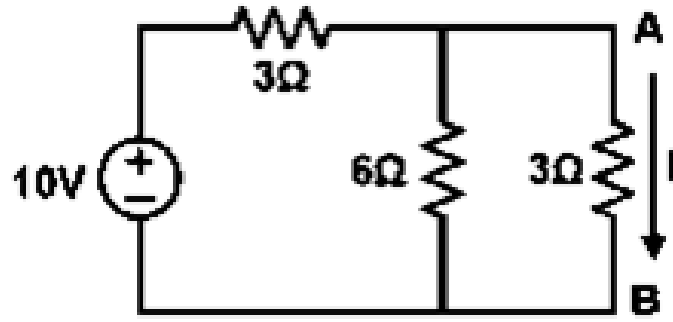9. (a) Prove the Compensation theorem by writing a SPICE code and taking a 20% change in the 3Ω resistance through which the current I is flowing. [[CO6](Remember/LOCQ)]



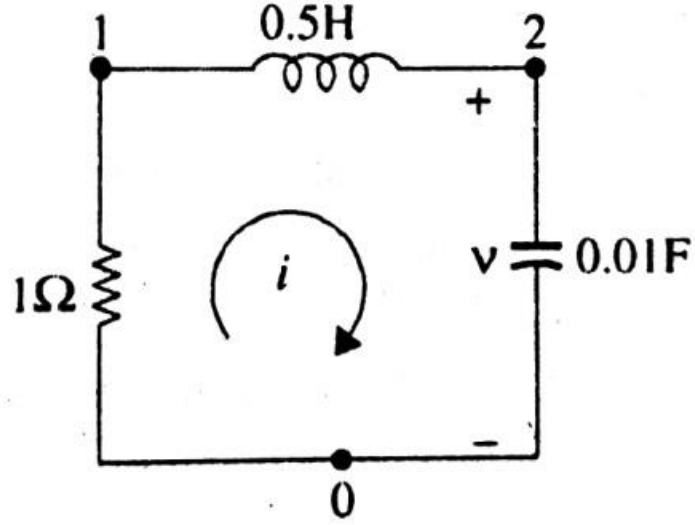- (b) Use SPICE to find $i(t)$ & $v(t)$ in the given circuit. Where, $i(0) = -0.5A$, $v(0) = 2.5V$. [[CO6](Apply/IOCQ)]



6 + 6 = 12

Cognition Level	LOCQ	IOCQ	HOCQ
Percentage distribution	43.75	50	6.25