

- (vii) Laplace Transform of unit step function is
  - (a)  $1/s$                       (b)  $s$                       (c)  $1/(s + 1)$                       (d)  $1/s^2$ .
- (viii) A two port network is reciprocal if
  - (a)  $Z_{11} = Z_{22}$                       (b)  $Y_{12} = Y_{21}$                       (c)  $Y_{12} = Y_{22}$                       (d)  $Y_{11} = Y_{21}$ .
- (ix) Short circuit forward transfer admittance is:
  - (a)  $Y_{11}$                       (b)  $Y_{12}$                       (c)  $Y_{22}$                       (d)  $Y_{21}$ .
- (x) Mesh analysis is based on
  - (a) KCL    (b) KVL
  - (c) KVL and KCL    (d) none of above.

**Group - B**

2. (a) Find the node voltages at nodes 1 & 2 of Fig.1.

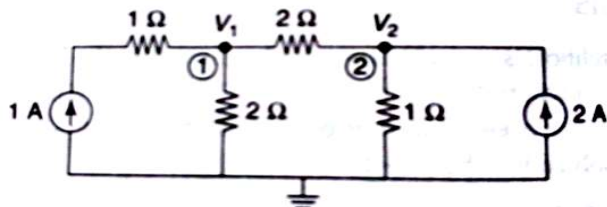


Fig.1

- (b) Find the current through 4 Ω resistance using mesh analysis of Fig.2.

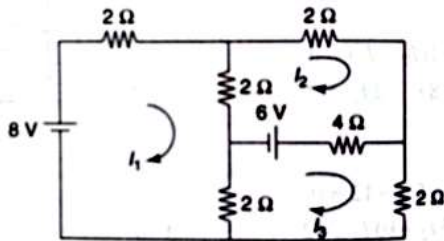


Fig.2

6 + 6 = 12

3. (a) Obtain current through 2 Ω resistance of Fig.3 using Thevenin's theorem.

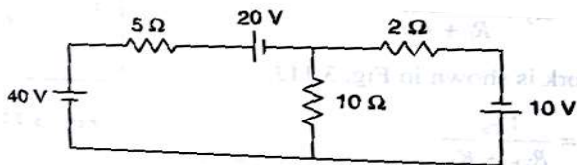


Fig.3

- (b) Find the current in 5Ω resistor of Fig.4 using Superposition Theorem

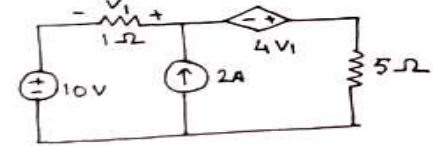


Fig.4

6 + 6

**Group - C**

- 4. (a) Define ramp signal and gate signal.
- (b) Find Laplace Transform of given signal shown in Fig.5.

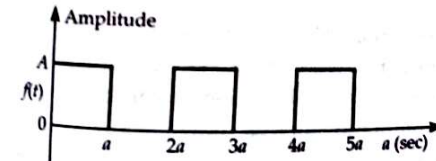


Fig.5

- (c) Find initial value and final value of the following function  $F(S) = \frac{5}{S(S+3)(S+8)}$

3 + 6 + 3

- 5. (a) In the following circuit voltage is 5Volts dc. Obtain Transient current  $i(t)$  through the circuit of Fig.6. Define time constant of a R-C circuit

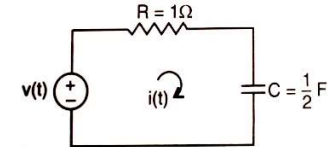


Fig.6

- (b) The switch  $S$  is in position 1 at a long time and moved to position 2 at  $t = 0$ . Find the current through the inductor  $i_L(t)$  of Fig.7.

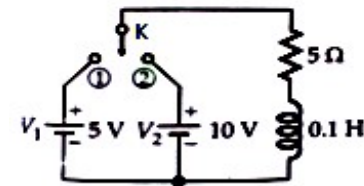


Fig.77 + 5 = 12

**Group - D**

6. (a) What is a tree? Write the properties of a tree.  
 (b) Explain how many branches are there in a co-tree?  
 (c) Consider the following incidence matrix and draw the graph.

$$\begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 \\ 0 & -1 & 1 & -1 & 0 & 0 \\ 0 & 0 & 0 & 1 & 1 & -1 \end{bmatrix}$$

(1 + 3) + 2 + 6 = 12

7. (a) Develop complete incidence matrix from the directed graph given in Fig.8.

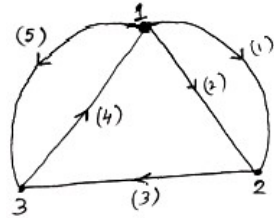


Fig.8

- (b) Select a tree of the above graph and compute tie-set matrix and fundamental cut-set matrix.  
 4 + (4 + 4) = 12

**Group - E**

8. (a) Define Y-parameters.  
 (b) Determine the ABCD-parameters for the circuit shown in Fig.9.

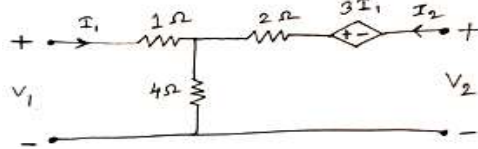


Fig.9

3 + 9 = 12

9. (a) Find Z parameters in terms of ABCD-parameters.  
 (b) Find Y parameters of the given network shown in Fig.10.

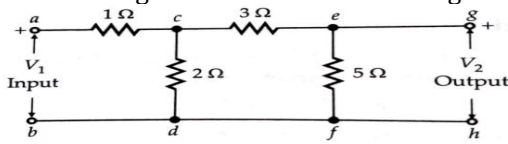


Fig.10

4 + 8 = 12

**CIRCUIT THEORY ANALYSIS  
 (ELEC 4182)**

**Time Allotted : 3 hrs**

**Full Mark**

*Figures out of the right margin indicate full marks.*

*Candidates are required to answer Group A and any 5 (five) from Group B to E, taking at least one from each group.*

*Candidates are required to give answer in their own words as far as practicable.*

**Group - A  
 (Multiple Choice Type Questions)**

1. Choose the correct alternative for the following: **10 × 1 :**
- (i) Superposition theorem is valid only for
    - (a) linear circuits
    - (b) non-linear circuit
    - (c) both (a) and (b)
    - (d) none of these.
  - (ii) Application of Norton's theorem to a circuit yields
    - (a) equivalent current source and impedance in series
    - (b) equivalent current source and impedance in parallel
    - (c) equivalent voltage source and impedance in series
    - (d) equivalent voltage source and impedance in parallel.
  - (iii) Time constant of a RC circuit is
    - (a) C/R
    - (b) R/C
    - (c) RC
    - (d)
  - (iv) Laplace Transform analysis gives
    - (a) time domain response only
    - (b) frequency domain response only
    - (c) both (a) and (b)
    - (d) neither (a) nor (b).
  - (v) Which among the statements given below is/are the proper 'Complete Incidence Matrix'?
    - (a) Determinant of a loop of a complete incidence matrix is always zero
    - (b) Addition of all entries in any column should be equal to zero
    - (c) Rank of connected or oriented graph is always 'n-1'
    - (d) All of the above.
  - (vi) The number of independent loops for a network with n nodes and b branches
    - (a) n + 1
    - (b) n - 1
    - (c) b - n + 1
    - (d) b + n - 1.