

- (vii) In a series RC circuit, if the output is measured across the capacitor, the circuit can be considered as a
 - (a) Band Pass Filter
 - (b) Band Reject Filter
 - (c) Low Pass Filter
 - (d) High Pass Filter.
- (viii) The dc gain of a system having transfer function $H(s) = \frac{12}{(s+2)(s+3)}$ is
 - (a) 12
 - (b) 6
 - (c) 3
 - (d) 2.
- (ix) '. TRAN' statement in SPICE is use to study the network in
 - (a) frequency domain
 - (b) time domain
 - (c) both frequency and time domain
 - (d) none of these.
- (x) Active filter consists of
 - (a) capacitor
 - (b) inductor
 - (c) op-amp and capacitor
 - (d) op-amp.

Group - B

2. (a) In the circuit of Fig.2(a), find Norton's equivalent circuit looking from terminal A-B.

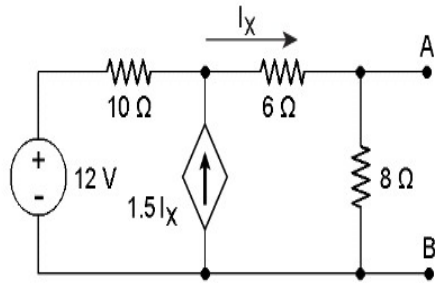


Fig.2(a)

- (b) Find mesh currents for the circuit of fig.2(b)

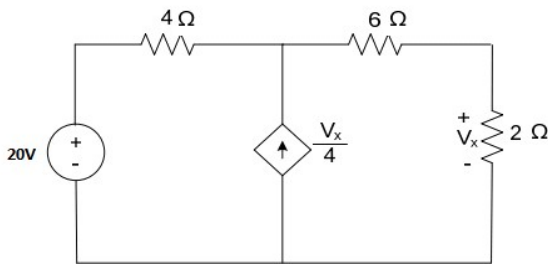


Fig.2(b)

7 + 5 = 12

- (c)

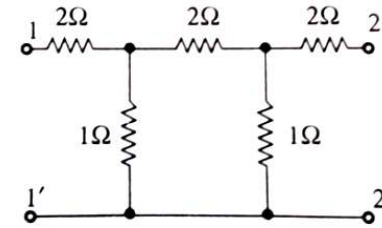


Fig.7(c)

Calculate the y parameters of the given circuit in Fig.7(c) and the equivalent π - circuit.

2 + 4 + 4

Group - E

8. (a) Find $\frac{V_{OUT}(s)}{V_{IN}(s)}$ for the circuits shown in Fig.8(a). Determine corner frequency and type of the filter.

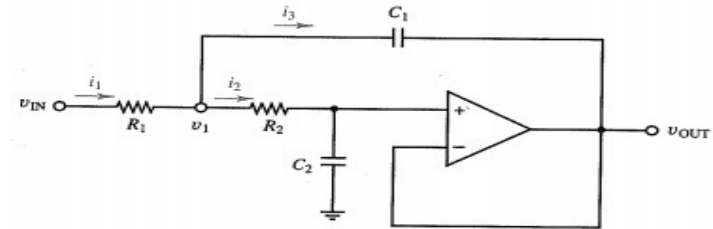


Fig. 8(a)

- (b) Design a 1st order active low pass filter with a dc gain of 4 corner frequency of 500Hz.

(6 + 1 + 1) + 4

9. (a) Write the input file in PSPICE for the circuit in Fig.9(a) to obtain node voltages.

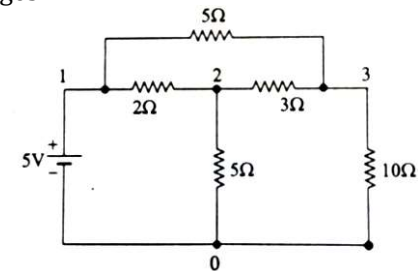


Fig.9(a)

- (b) An initially relaxed series RC circuit with $R=1k\Omega$ and $C=0.1\mu F$ is energized with a pulse source $v(t)$ as shown in fig.9(b) below. Write a SPICE input file to plot the voltage across resistor, voltage across capacitor and current response of the circuit.

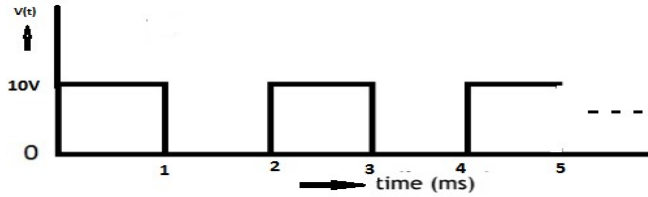


Fig. 9(b)

5 + 7 = 12

**CIRCUIT THEORY
(ELEC 2102)**

Time Allotted : 3 hrs

Full Marks : 70

Figures out of the right margin indicate full marks.

Candidates are required to answer Group A and any 5 (five) from Group B to E, taking at least one from each group.

Candidates are required to give answer in their own words as far as practicable.

**Group - A
(Multiple Choice Type Questions)**

1. Choose the correct alternative for the following: **10 × 1 = 10**
 - (i) Super mesh analysis is used in case of
 - (a) current source branch is common for two meshes
 - (b) ideal voltage source is connected between two non-reference nodes
 - (c) both (a) and (b)
 - (d) circuit containing only dependent source.
 - (ii) If two equal resistances connected in series across a certain supply are now connected in parallel across the same supply, the power produced will be _____ of series connection.
 - (a) one half
 - (b) one fourth
 - (c) two times
 - (d) four Times.
 - (iii) In a RLC series circuit $R=2\Omega$, $L=2mH$ and $C=1\mu F$ and applied voltage is 10V dc. Then what is steady state current value?
 - (a) 5A
 - (b) 2A
 - (c) 1A
 - (d) 0A.
 - (iv) The rank of f-cut-set matrix of a connected graph with n number of nodes is
 - (a) n-1
 - (b) n
 - (c) 2n+1
 - (d) n+1.
 - (v) If a circuit has n number of nodes and b number of branches then the number of mesh equations will be
 - (a) n-1
 - (b) b-1
 - (c) b-n+1
 - (d) b+n-1.
 - (vi) The condition for Reciprocity of any two port network is
 - (a) $Y_{11} = Y_{12}$
 - (b) $Y_{21} = Y_{12}$
 - (c) $Y_{11} = Y_{22}$
 - (d) $Y_{22} = Y_{12}$.

3. (a) A source $V_s(t) = V \cos(100\pi t)$ has an internal impedance of $(4+j3)\Omega$. If a purely resistive load connected to this source has to extract the maximum power out of the source, find its value.
- (b) Elaborate the statement of the Reciprocity theorem with a proper example.
- (c) For the circuit given in fig.3(c) find I_1 and I_2 . Assume $k=1$.

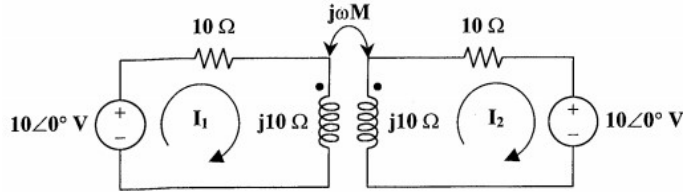


Fig. 3(c)

3 + 3 + 6 = 12

Group - C

4. (a) Find Laplace transform of the following function shown in Fig. 4(a).

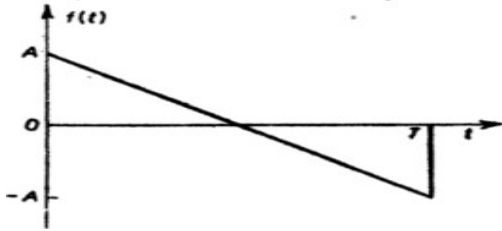


Fig.4(a)

- (b) Sketch the unit step response of an underdamped second order prototype system and mark all the time domain specifications on it.
- (c) In the circuit of fig. 4(b), the switch 's' is opened at $t=0$. Determine $i_1(t)$ and $i_2(t)$. Assume the circuit was at steady state condition before $t = 0$.

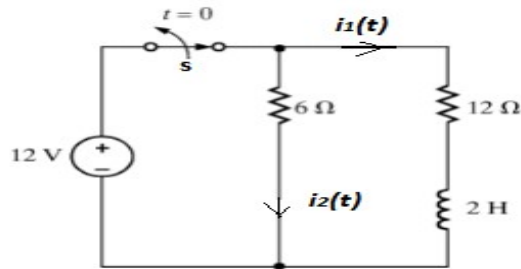


Fig. 4 (b)

4 + 3 + 5 = 12

3. (a) A source $V_s(t) = V \cos(100\pi t)$ has an internal impedance of $(4+j3)\Omega$. If a purely resistive load connected to this source has to extract the maximum power out of the source, find its value.
- (b) Elaborate the statement of the Reciprocity theorem with a proper example.
- (c) For the circuit given in fig.3(c) find I_1 and I_2 . Assume $k=1$.

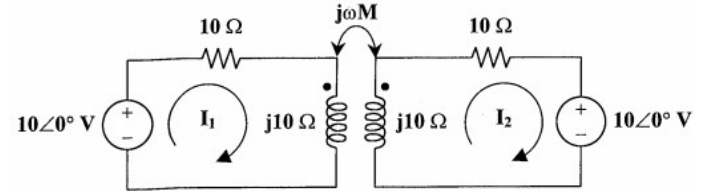


Fig. 3(c)

3 + 3 + 6 = 12

Group - C

4. (a) Find Laplace transform of the following function shown in Fig. 4(a).

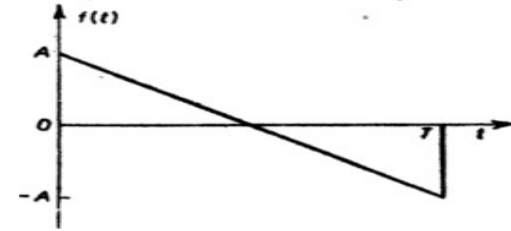


Fig.4(a)

- (b) Sketch the unit step response of an underdamped second order prototype system and mark all the time domain specifications on it.
- (c) In the circuit of fig. 4(b), the switch 's' is opened at $t=0$. Determine $i_1(t)$ and $i_2(t)$. Assume the circuit was at steady state condition before $t = 0$.

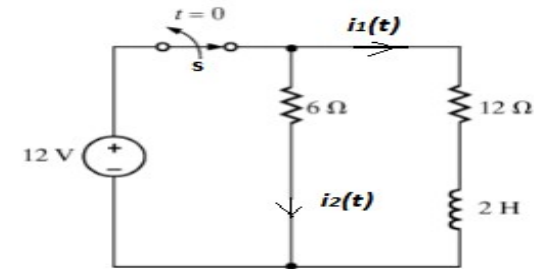


Fig. 4 (b)

4 + 3 + 5 = 12

5. (a) Given a pulse $f(t)$ in Fig.5(a), find its Laplace transform $F(s)$. Find inverse Laplace of $F^2(s)$ and hence draw its waveform.

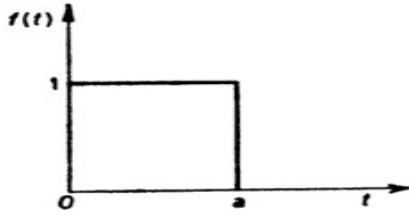


Fig.5(a)

- (b) Find the expressions of v and i for the given circuit in Fig. 5(b). for $t > 0$.

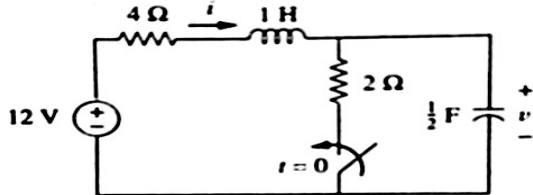


Fig. 5(b)

$(1 + 2 + 2) + 7 = 12$

Group - D

6. (a) What is 'tree'?
- (b) Draw the directed graph for the circuit shown in Fig.6(b1) below. Determine Tie-set matrix. Assume the sub-graph shown in Fig.6(b2) below as a tree. Find mesh equilibrium equations for the circuit using graph theory.

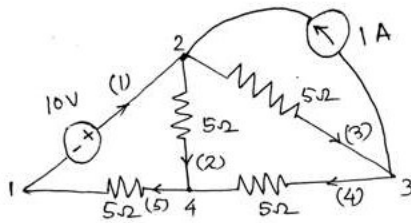


Fig. 6(b1)

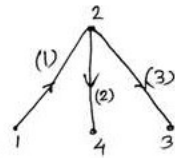


Fig.6(b2)

$2 + (2 + 2 + 6) = 12$

7. (a) Define 'Transmission' parameters.
- (b) Prove that for transmission parameters, condition of symmetrical network is $A=D$.

5. (a) Given a pulse $f(t)$ in Fig.5(a), find its Laplace transform $F(s)$. Find inverse Laplace of $F^2(s)$ and hence draw its waveform.

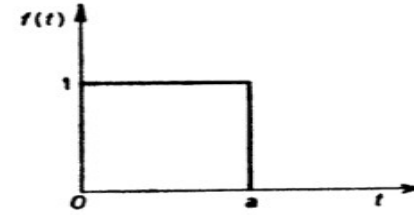


Fig.5(a)

- (b) Find the expressions of v and i for the given circuit in Fig. 5(b). for $t > 0$.

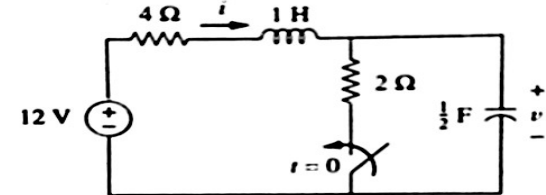


Fig. 5(b)

$(1 + 2 + 2) + 7 = 12$

Group - D

6. (a) What is 'tree'?
- (b) Draw the directed graph for the circuit shown in Fig.6(b1) below. Determine Tie-set matrix. Assume the sub-graph shown in Fig.6(b2) below as a tree. Find mesh equilibrium equations for the circuit using graph theory.

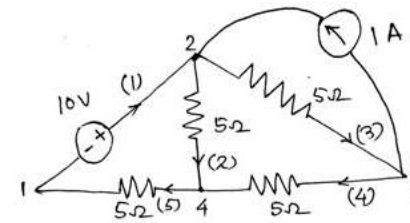


Fig. 6(b1)

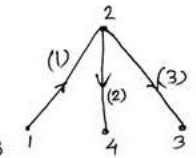


Fig.6(b2)

$2 + (2 + 2 + 6) = 12$

7. (a) Define 'Transmission' parameters.
- (b) Prove that for transmission parameters, condition of symmetrical network is $A=D$.