

B.Tech/ECE/3rd Sem/ECEN 2101/2015

2015

ANALOG ELECTRONICS CIRCUIT

(ECEN 2101)

Time Alloted : 3 Hours

Full Marks : 70

*Figures out of the right margin indicate full marks.**Candidates are required to answer Group A and any 5 (five) from Group B to E, taking at least one from each group.**Candidates are required to give answer in their own words as far as practicable***GROUP - A**

(Multiple Choice Type Questions)

1. Choose the correct alternatives for the following : [10×1=10]
- i) The input/output impedance of a transconductance amplifier, with negative feedback,
- (a) increases/decreases (b) increases/increases
(c) decreases/ increases (d) decreases/decreases
- ii) The voltage gain of differential-input-balanced-output amplifier is m times that of differential-input-unbalanced-output amplifier. Here m is
- (a) 2 (b) 0.5
(c) 1 (d) undefined

- iii) In which type of amplifier's operation is cross-over distortion observed?
- (a) Class A (b) Class B
(c) Class C (d) Class AB
- iv) The oscillating frequency of Colpitts oscillator can be found as

$$(a) f = \frac{1}{2\pi} \sqrt{\frac{1}{LC_1} \left(1 + \frac{C_1}{C_2}\right)^2}$$

$$(b) f = \frac{1}{2\pi} \sqrt{\frac{1}{LC_1} (1 + C_1 C_2)^2}$$

$$(c) f = \frac{1}{2\pi} \sqrt{\frac{1}{LC_1} (1 + C_1 + C_2)^2}$$


$$(d) f = \frac{1}{2\pi} \sqrt{\frac{1}{LC_1 C_2} \left(1 + \frac{C_1}{C_2}\right)^2}$$

- v) With respect to the feedback topologies a common emitter and common collector amplifier fall under the category of
- (a) Voltage-Series/Current-Series
(b) Current-Series/Voltage-Series
(c) Current-Shunt/Voltage-Series
(d) Current-Series/Voltage-Shunt
- vi) Placing a bypass capacitor, in common-emitter configuration, is necessary to
- (a) prevent the fall of mid-band voltage gain
(b) achieve a stable Q point
(c) prevent thermal runaway
(d) none of these

vii) A circuit that removes positive or negative parts of waveform is called

- (a) clamper (b) clipper
(c) diode clamp (d) limiter

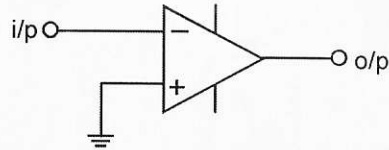viii) If the input to the circuit of figure is a sine wave the output will be



- (a) A half wave rectified sine wave
(b) A full wave rectified sine wave
(c) A triangular wave
(d) A square wave

ix) An ideal op-amp is an ideal

- (a) voltage controlled current source
(b) voltage controlled voltage source
(c) current controlled current source
(d) current controlled voltage source

x) In a bipolar junction transistor the base region is made very thin so that

- (a) recombination in base region is minimum
(b) electric field gradient in base is high
(c) base can be easily fabricated
(d) base can be easily biased

GROUP - B

2. (a) Draw the circuit of a transistor in CE configuration.
(b) What is a load line? Explain the concept of Q-point.
(c) For CE configuration prove that $I_C = \beta I_B + (1+\beta)I_{CO}$.

(d) In a collector to base bias circuit indicated in Fig.1., a transistor with $\beta = 50$ is used. Supply voltage $V_{CC} = 10V$, $V_{BE} = 0.7V$, collector resistor $R_C = 2k\Omega$. The bias is obtained by connecting $100k\Omega$ resistor from collector to base. Find the Q-point and stability factor.

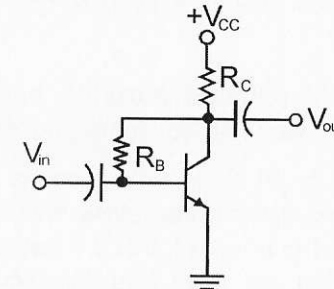


Fig.1

2+3+2+5 = 12

3. (a) The emitter resistance is inevitable to make a common emitter circuit stable. How this resistance affects the mid-band voltage gain? How can we handle this consequence?

- (b) Find the input and output impedance for the common-emitter circuit, shown in Fig.2, operated at mid frequency, with

$V_{CC} = +12V$, $R_1 = 2\text{ K}\Omega$, $R_2 = 4\text{ K}\Omega$, $R_S = 50\ \Omega$,
 $R_C = R_L = 10\text{ K}\Omega$, $R_E = 10\text{ K}\Omega$, and $h_{ie} = 1\text{ K}\Omega$, $h_{fe} = 150$.

Assume $\frac{1}{h_{oe}} \rightarrow \infty$,

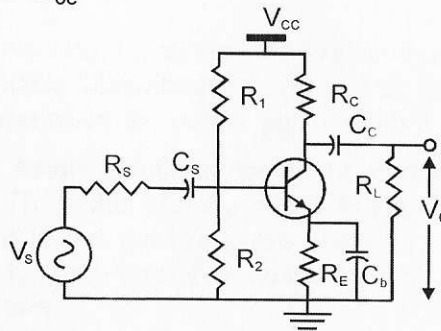


Fig.2

6+6 = 12

GROUP - C

4. (a) State Barkhausen criterion and explain the conditions that must be satisfied for a feedback amplifier to produce steady oscillations.
 - (b) Sketch the circuit of a phase-shift oscillator and explain its operation. Find an expression for the frequency of oscillations and the condition for sustained oscillation.
- 5+7 = 12
5. (a) List the merits and demerits of negative feedback.
 - (b) The open-loop gain $A_o = 99990$, of a high-gain amplifier, varies by 20%. Design a feedback path with feedback factor K such that the closed-loop gain varies only by 0.02%.

- (c) Derive an expression of output impedance for voltage-series type feedback amplifier.

(d) Draw the hybrid π model of BJT. 2+3+4+3 = 12

Group - D

6. (a) Discuss the advantages of differential amplifiers. Find the expression of differential voltage gain for a differential input balanced output type amplifier.
 - (b) Write the properties of instrumentation amplifier. Draw the circuit of an instrumentation amplifier.
 - (c) Draw a precision rectifier circuit with response curve.
- 4+5+3 = 12
7. (a) Describe the different building blocks of Op-Amp. Mention the properties of an ideal op amp.
 - (b) The circuit shown in the Fig.3, $R_1 = 100\Omega$, $R_2 = 56\text{ k}\Omega$, $v_{in} = 1V$ pp sine wave, and the op-amp is type 741 with supply voltages = $\pm 15V$. Determine the upper and lower threshold voltages and draw the output waveform.

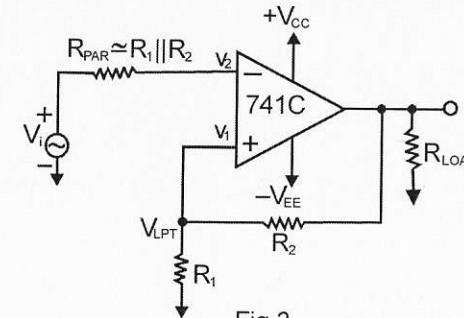


Fig.3

(3+3)+6 = 12

GROUP - E

8. (a) Derive the efficiency of transformer coupled class A power amplifier.
 (b) Explain the operation of a push pull amplifier circuit.
 (c) Write a short note on cross over distortion. How can it be overcome?
5+4+3 = 12
9. (a) Draw the circuit diagram and explain the operation of a Monostable Multivibrator using a 555 timer IC. Derive the expression for output pulse width.
 (b) In the Astable Multivibrator of the circuit shown in the Fig.4, $R_1 = 2.2 \text{ k}\Omega$, $R_2 = 3.9 \text{ k}\Omega$, and $C = 0.1 \text{ }\mu\text{F}$. Determine the positive pulse width T_1 , negative pulse width T_2 , free-running frequency f_0 and percentage of duty cycle.

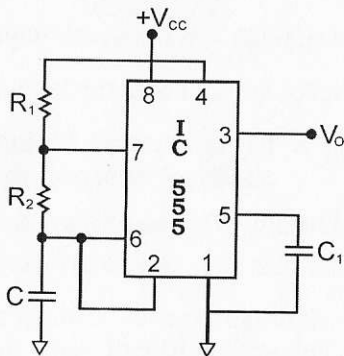


Fig.4

6+6 = 12