

**DIGITAL LOGIC DESIGN**  
**(MCAP 1101)**

Time Allotted: 3 hrs

Full Marks: 70

*Figures out of the right margin indicate full marks.*

*Candidates are required to answer Group A and*

*Any 5 (five) from Group B to E, taking at least one from each group.*

*Candidates are required to give answer in their own words as far as practicable.*

**Group - A**

**(Multiple Choice Type Questions)**

1. Choose the correct alternative for the following: **10 × 1 = 10**
  - (i) An OR gate has 6 inputs. The number of input words in it's truth table are  
(a) 6                      (b) 32                      (c) 64                      (d) 128.
  - (ii) The simplification of the Boolean expression  $(A'BC')' + (AB'C)'$  is  
(a) 0                      (b) 1                      (c) A                      (d) BC.
  - (iii) Find out the unknown base x when  $(123)_8 = (313)_x$ .  
(a) 6                      (b) 5                      (c) 7                      (d) 4.
  - (iv) What is the Grey code for the binary number  $(01001)_2$ ?  
(a) 01101                      (b) 010101  
(c) 101010                      (d) none of these.
  - (v) The number of control lines for a 8 - to - 1 multiplexer is  
(a) 2                      (b) 3                      (c) 4                      (d) 5.
  - (vi) One disadvantage of R-S flip-flop is,  
(a) it has only single output                      (b) it has no enable input  
(c) it has RACE condition                      (d) it has no clock input.
  - (vii) The Octal equivalent of  $(386)_{10}$  is  
(a) 606                      (b) 602                      (c) 620                      (d) 622.
  - (viii) Maximum no of inputs connected to gate is called  
(a) fan                      (b) fan in  
(c) fan out                      (d) out come.

- (ix) 2's complement representation of 1101 0110 is \_\_\_\_\_.  
(a) 0001 1001                      (b) 00101010  
(c) 1010 1001                      (d) none.
- (x) A Boolean expression  $\Sigma(1,3,6,7)$  is equivalent to  
(a)  $\Pi(0,2,4,5)$                       (b)  $\Pi(0,1,4,5)$   
(c)  $\Pi(0,2,4,6)$                       (d)  $\Pi(1,2,3,5)$ .

**Group - B**

2. (a) Perform the arithmetic operations  $(+42) + (-13)$  and  $(-42) - (-13)$  in binary signed 2's complement representation.
- (b) Add the following numbers using BCD number system  $(37) + (15)$ . Convert the following hexadecimal-number  $(13AC45.B3D)_{16}$  into it's octal equivalent.

**(3 + 3) + (3 + 3) = 12**

3. (a) Convert the Grey-code 1110111010101 into it's equivalent Binary Code.
- (b) Perform the following subtraction of two unsigned numbers using 1's complement:  
 $11001 - 10110$
- (c) Draw the block diagram of BCD adder and explain how it works.
- (d) Convert the octal number 7401 to its Binary equivalent.

**3 + 3 + 3 + 3 = 12**

**Group - C**

4. (a) What are universal gates? Construct a logic circuit using NAND gates only for the expression  $X = A.(B + C)$
  - (b) Convert the following Boolean-function into product of sum(POS) form:  
 $F(w, x, y, z) = \Sigma(2, 3, 10, 11, 12, 13, 14, 15)$ .
- (2 + 4) + 6 = 12**
5. (a) Simplify the following Boolean-function using K-map method and draw the circuit diagram using minimum number of NAND gates.  
 $F(w, x, y, z) = \Sigma(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$ .

- (b) Reduce the following Boolean expression into five literals:

$$ABC + A'B'C + A'BC + ABC' + A'B'C'$$

(where X' implies the complement of X)

$$(5 + 3) + 4 = 12$$

**Group - D**

6. (a) Implement the following function using 4-to-1 multiplexer.

$$F(A, B, C) = \sum(2, 3, 5, 6)$$

- (b) Implement a full-adder circuit with a Decoder and two OR gates.

$$6 + 6 = 12$$

7. (a) How many  $128 \times 8$  memory chips are needed to provide a memory capacity of  $4096 \times 16$ ? Also indicate the size of address bus and data bus for  $4096 \times 16$  bits memory.

- (b) Draw the logic diagram of a full subtractor using half subtractors and explain its working with the help of a truth table.

- (c) What are the two approaches to reduce the delay in the adders?

$$(1 + 1 + 1) + 6 + 3 = 12$$

**Group - E**

8. (a) What is the difference between a latch and a flip-flop?

- (b) Construct a shift register from S-R flip-flops. Explain its working.

- (c) Distinguish between synchronous sequential circuit and asynchronous sequential circuit.

$$2 + (2 + 2) + 3 = 12$$

9. (a) What is a shift register? Can a shift register be used as a counter? If yes, explain how?

- (b) What is race around condition in flip-flop?

- (c) Justify with diagram that T flip-flop is a single input version of JK flip.

$$(2 + 4) + 3 + 3 = 12$$