

Group - E

8. (a) Draw the ideal and practical characteristics of a band - pass and a stop-band filter.

(b) The driving point impedance of a circuit is given by

$$Z(s) = \frac{(s+1)}{s(s+2)}$$

Realize a circuit using Cauer form-I.

(2 + 2) + 8 = 12

9. (a) The driving point impedance of a circuit is given by

$$Z(s) = \frac{(s+1)}{s(s+2)}$$

Realize a circuit using Foster's form-II.

(b) A filter circuit, as shown in the Fig. 5, receives a signal from a rectifier having certain frequency. Analyse the circuit to know the type of the filter.

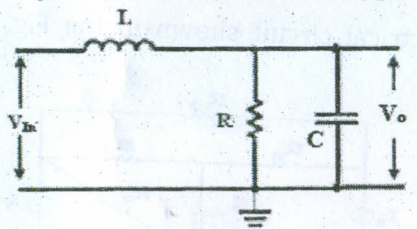


Fig. 5

8 + 4 = 12

**B.TECH/AEIE /3RD SEM/ AEIE 2102/2017
CIRCUIT THEORY AND NETWORKS
(AEIE 2102)**

Time Allotted : 3 hrs

Full Marks : 70

Figures out of the right margin indicate full marks.


Candidates are required to answer Group A and any 5 (five) from Group B to E, taking at least one from each group.

Candidates are required to give answer in their own words as far as practicable.

**Group - A
(Multiple Choice Type Questions)**

1. Choose the correct alternative for the following: 10 × 1 = 10
 - (i) When two inductive coils having self-inductance L₁, L₂ and mutual inductance M in between them are connected in series aiding, the equivalent inductance across the series combination will be
 (a) L₁+L₂+2M (b) L₁+L₂-2M (c) L₁+L₂+M (d) L₁+L₂-M.
 - (ii) A reciprocal circuit should have only
 (a) one independent source (b) at least two independent sources
 (c) dependent source (d) independent and dependent sources.
 - (iii) In an oriented graph, the reduced incidence matrix is used to find the number of
 (a) valid trees (b) KVL equations
 (c) KCL equations (d) all of the above.
 - (iv) Superposition theorem is not applicable for
 (a) voltage calculations (b) current calculations
 (c) power calculations (d) none of the above.
 - (v) A voltage dependent current source is realized using a/an
 (a) inductor (b) bipolar junction transistor
 (c) unity (d) zero.
 - (vi) In an RLC series circuit the power factor at resonance is
 (a) lagging (b) leading (c) unity (d) Not easy to predict.
 - (vii) A galvanic cell is used for the conversion of
 (a) (n - 1) (b) n (c) (b - n + 1) (d) (n + 1).

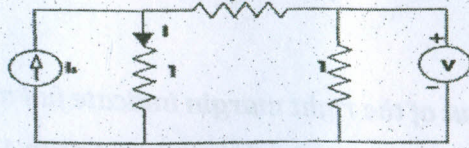
- (viii) In the circuit given, $I = 1$ A for $I_s = 0$ A. What is the value of I for $I_s = 2$ A?
 (a) 1A (b) 2A (c) 3A (d) 4A.



- (ix) A network, described by ABCD parameters, will be reciprocal if
 (a) $A = D$ (b) $(AD - BC) = 1$ (c) $(AC - BD) = 1$ (d) $(AD - BC) = 0$.
- (x) Laplace transform of $\sin \alpha t$ is
 (a) $\frac{\alpha}{s^2 + \alpha^2}$ (b) $\frac{s}{s^2 + \alpha^2}$
 (c) $\frac{\alpha}{s^2 - \alpha^2}$ (d) $\frac{s}{s^2 - \alpha^2}$.

Group - B

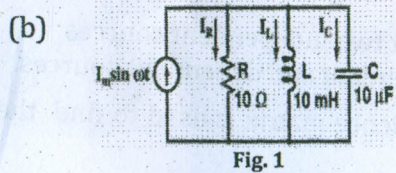- 2.(a) Derive the condition of resonance of a series RLC circuit. If the resistance in that circuit is doubled then what change in the resonating frequency will be observed?



The Fig. 1 shows an RLC circuit with a sinusoidal current source. Find the ratio of the magnitudes of the I_L and I_R at resonance.

(5 + 1) + 6 = 12

- 3.(a) Two identical coupled inductors are connected in series. The measured inductances for the two possible series connections are 380H and 240H. Find their mutual inductance.
- (b) What is the co-efficient of coupling in a magnetically coupled circuit? What is its practical range? Find the output voltage of the ideal transformer with the polarities and dots shown in the Fig. 2.

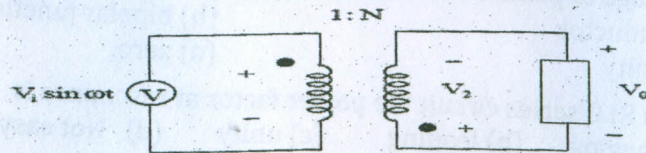


Fig. 2

6 + (1 + 1 + 4) = 12

Group - C

- 4.(a) An impulse voltage excites an RC circuit. Derive an expression of voltage across the capacitor using the concepts of Laplace transform. Assume that the circuit is initially relaxed.

- (b) In an RLC circuit, find the condition of the critically damped response.

6 + 6 = 12

- 5.(a) Find the inverse Laplace transform of the following function

$$F(s) = \frac{(s+2)}{s(s+1)(s+2)}$$

Using the initial value theorem, find the value of the above function at $t = 0$.

- (b) Write the Laplace transforms of the following time domain functions:
 (i) unit impulse (ii) unit step (iii) exponentially decaying and (iv) unit parabola.

(6 + 2) + 4 = 12

Group - D

6. (a) Consider the electrical circuit shown in the Fig. 3. Obtain the reduced incidence matrix.

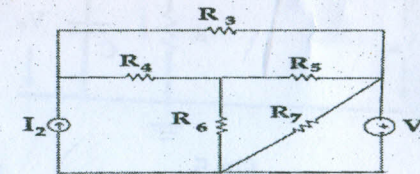


Fig. 3

- (b) Find the total number of valid trees that may be obtained from the above circuits.

6 + 6 = 12

7. (a) The elements in the Z-parameter matrix are: $Z_{11} = 1\Omega$, $Z_{12} = 2\Omega$, $Z_{21} = 2\Omega$, and $Z_{22} = 4\Omega$. Find Z_a , Z_b , and Z_c in the circuit of Fig. 4.

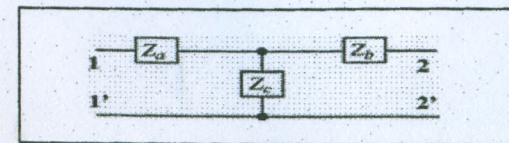


Fig. 4

- (b) Express ABCD parameters in terms of Z-parameters.

6 + 6 = 12