

7. (a) Obtain the expression for noise margin high (NM_H) for a CMOS inverter from the voltage transfer characteristics.
- (b) State how the Wilson MOS mirror can be modified to avoid the systematic current error. Derive an expression for output resistance in a Wilson MOS mirror.

7 + (2 + 3) = 12

Group - E

- 8 (a) Derive an expression for propagation delay in a CMOS inverter with capacitor load. Comment on the relation between propagation delay and capacitance of the load.
- (b) Draw the CMOS realization to implement the following logic expression, $y = \overline{A(B + CD)}$
- 9 (a) Derive the expression for noise margin high from voltage transfer characteristics of a pseudo-NMOS inverter.
- (b) Explain with detailed circuit diagram for a process of writing '0' in a 6T SRAM cell.

6 + 6 = 12

6 + 6 = 12

**MICRO ELECTRONIC DEVICES AND CIRCUITS
(AEIE 5101)**

Time Allotted: 3 hrs

Full Marks: 70


Figures out of the right margin indicate full marks.

*Candidates are required to answer Group A and **Any 5 (five)** from Group B to E, taking **at least one** from each group. Candidates are required to give answer in their own words as far as practicable.*

**Group - A
(Multiple Choice Type Questions)**

1. Choose the correct alternative for the following: **10 × 1=10**
- (i) The threshold voltage of an n-channel MOSFET can be increased by
 (a) increasing the channel dopant concentration
 (b) reducing the channel dopant concentration
 (c) reducing gate oxide thickness
 (d) reducing the channel length.
- (ii) In a CMOS inverter the upper MOSFET is
 (a) active load (b) passive load
 (c) complementary load (d) none of the above.
- (iii) What is the difference voltage output from an Op-Amp if the inputs are an ideal in-phase signal?
 (a) The differential gain times twice the input signal
 (b) The differential gain times the input signal
 (c) The common-mode gain times twice the input signal
 (d) The common-mode gain times the input signal.
- (iv) The primary function of the bias circuit is to
 (a) hold the circuit stable at V_{CC}
 (b) hold the circuit stable at V_{in}
 (c) ensure proper gain is achieved
 (d) hold the circuit stable at the designed Q-point.
- (v) What is the voltage gain of the unity follower?
 (a) 0 (b) 1 (c) -1 (d) infinity.

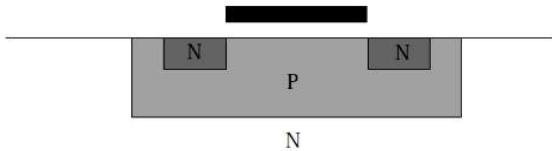- (vi) A MOSFET is
 - (a) a current-controlled device
 - (b) a voltage-controlled device
 - (c) always forward-biased
 - (d) reversed biased.
- (vii) Which components are hard to fabricate into ICs?
 - (a) diode
 - (b) resistor
 - (c) inductor
 - (d) transistor.
- (viii) What is the most common method used for the growth of single crystals for IC fabrication?
 - (a) epitaxial growth
 - (b) czochralsky pulling technique
 - (c) film deposition
 - (d) photolithography.
- (ix) Voltage follower is a special case of _____.
 - (a) inverting configuration
 - (b) non-inverting configuration
 - (c) difference configuration
 - (d) integrator configuration.
- (x) The MOSFET below



is labeled with the different types of silicon. The device is best described as

- (a) an n-MOSFET in an N-well
- (b) an n-MOSFET in a P-well
- (c) a p-MOSFET in an N-well
- (d) a p-MOSFET in a P-well.

Group - B


- 2. (a) What are the various steps involved in IC fabrication process? Briefly describe each step.
 - (b) Design an active resistor by using an n-channel MOSFET and derive the expression for resistance.
- 5 + 7 = 12**
- 3. (a) Derive the expression for current transfer ratio in a two transistor BJT Widlar current source.
 - (b) For $I_{ref} = 1 \text{ mA}$, find I_o when $V_o = 5V$. For a cascade MOS mirror utilizing devices with $V_t = 0.5V$, $\mu_n C_{ox} = 387 \mu A/V^2$, $V_a' = 5V/\mu m$, $W/L = 3.6 \mu m/0.36 \mu m$ and $I_{ref} = 100 \mu A$, find output resistance of the MOS mirror.
- 6 + 6 = 12**

Group - C

- 4. (a) An active-loaded MOS differential amplifier inside 741 Op-Amp has the following specification: $(W/L)_n = 100$, $(W/L)_p = 200$, $\mu_n C_{ox} = 2\mu_p C_{ox} = 0.2$, $V_{An} = |V_{Ap}| = 20V$, $I = 0.8 \text{ mA}$, $R_{SS} = 25 \text{ k}\Omega$. Calculate G_m , A_d , $|A_{CM}|$ and CMRR of MOS differential pair.
 - (b) Deduce the expression for the transconductance for the input stage of a 741 Op-Amp.
- 7 + 5**
- 5. (a) Derive the expression for output resistance in a 741 Op-Amp from small signal model of the output stage.
 - (b) Derive the relationship between unity-gain bandwidth (f_u) and rate (SR) in case of a 741 Op-Amp.
- 9 + 5**

Group - D

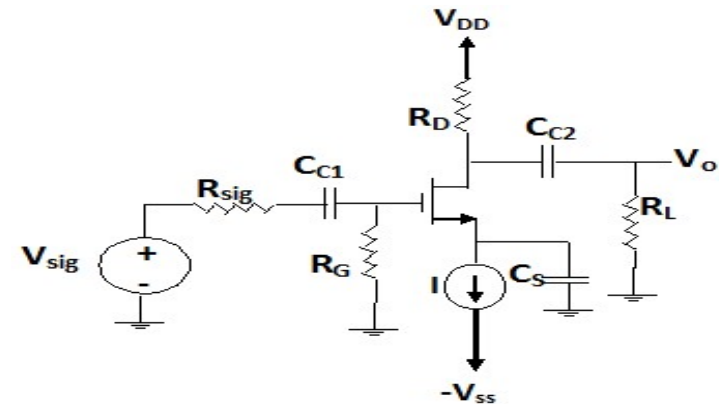- 6. (a) Derive the expression for CMRR of an active loaded MOS differential pair.
- (b) Perform small signal analysis on the given NMOS amplifier circuit shown in following figure. Find an expression for output impedance and voltage gain.



8 + 4