

**DIGITAL ELECTRONICS
(ECEN 2002)**

Time Allotted : 3 hrs

Full Marks : 70

Figures out of the right margin indicate full marks.

Candidates are required to answer Group A and any 5 (five) from Group B to E, taking at least one from each group.

Candidates are required to give answer in their own words as far as practicable.

**Group - A
(Multiple Choice Type Questions)**

1. Choose the correct alternative for the following: **10 × 1 = 10**
- (i) Conversion of $(11011.101)_2$ to decimal number is
 (a) 26.725 (b) 27.625
 (c) 25.675 (d) 22.657.
- (ii) A binary number with n bits all of which are 1 has the value
 (a) $n^2 - 1$ (b) 2^n
 (c) $2^{(n-1)}$ (d) $2^n - 1$.
- (iii) To construct a K-map, the order is crucial and is obtained by using
 (a) binary code progression (b) BCD code
 (c) gray code progression (d) excess-3 code.
- (iv) The OR operation can be produced with
 (a) two NOR gates (b) three NAND gates
 (c) four NAND gates (d) both answers (a) and (b).
- (v) Excess-3 code is
 (a) cyclic code (b) weighted code
 (c) self-complementing code (d) error-correcting code.
- (vi) If $(12x)_3 = (123)_x$, then the value of x is
 (a) 2 (b) 4 (c) 5 (d) none of the above.
- (vii) The fastest ADC is
 (a) successive approximation (b) flash type
 (c) dual slope (d) none of these.
- (viii) An n-stage ripple counter can count up to
 (a) 2^n (b) $2^n - 1$ (c) n (d) $2^{(n-1)}$.

- (ix) The number of J-K flip-flops that is required to design a mod-11 asynchronous up counter is
 (a) 3 (b) 4 (c) 5 (d) 6.
- (x) A combinational circuit
 (a) never contain memory element
 (b) may sometimes contain memory element
 (c) contain only memory element
 (d) always contain memory element.

Group - B

2. (a) Simplify the Boolean function using tabulation method:
 $F(A, B, C, D) = \sum m(0,2,3,6,7) + \sum d(8,10,11,15)$
 (b) Design a 3 bit odd parity generator **7 + 5 = 12**
3. (a) Minimize the Boolean function with K-map and realize using NAND gates only.
 $F(A, B, C, D) = \sum m(2,3,8,10,11,12,14,15) + \sum d(0,1)$
 (b) Represent
 (i) $(4578)_{10}$ in Gray code
 (ii) $(572.61)_8$ in common binary code. **7 + 5 = 12**

Group - C

4. (a) Design a full subtractor using half subtractor module and necessary logic gates.
 (b) Design a BCD to decimal decoder. **6 + 6 = 12**
5. (a) Realize 8:1 Multiplexer using 4:1 Multiplexer and necessary logic gates.
 (b) Implement a full subtractor using
 (i) decoder and necessary logic gates.
 (ii) 4:1 Multiplexer. **6 + 6 = 12**

Group - D

6. (a) Design an asynchronous counter that goes through the states 0-1-2-3-4-5-0.

- (b) Realize J-K flip-flop using D flip-flop.
- (c) Mention advantages of JK flip flop over SR flip flop.

6 + 4 + 2 = 12

7. (a) Design a synchronous MOD 3 UP/DOWN Counter using J-K flip-flops.
- (b) A clocked sequential circuit has four states A, B, C and D as show in the state diagram of Fig.1. Assume state assignments as A=00, B=01, C=10 and D=11. Prepare the state table and draw circuit using D flip-flops.

 


Fig. 1: State diagram of a clocked sequential circuit

6 + 6 = 12

Group - E

8. (a) Explain the operation of a Dual Slope ADC with the proper circuit diagram.
- (b) What are the advantage of R-2R ladder type DAC over counter type DAC?

7 + 5 = 12

9. (a) Implement the function $Y = (A+B)'$ using CMOS logic circuit.
- (b) Draw a NOR Gate using RTL logic circuit.
- (c) Draw the circuit of TTL NAND gate.

6 + 3 + 3 = 12