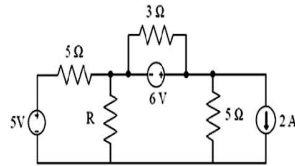
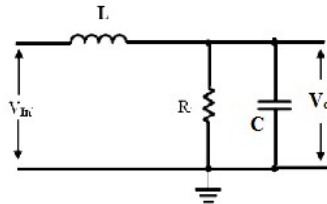


Group - E

8. (a) Find the maximum power transferred to the resistor R in the circuit of Fig. 6.


**Fig. 6**

- (b) Analyze the circuit in Fig. 7 to determine the type of the filter.

**Fig. 7**

$$4 + 8 = 12$$

9. (a) Design a low-pass active filter at a cut-off frequency of 1 KHz with a pass band gain of 2.
- (b) Find the Norton's equivalent resistance across the terminals a and b of the circuit in Fig. 8.

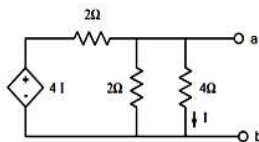**Fig. 8**

$$6 + 6 = 12$$

**CIRCUIT THEORY AND NETWORKS
(AEIE 2102)****Time Allotted : 3 hrs****Full Marks : 70***Figures out of the right margin indicate full marks.*

Candidates are required to answer Group A and any 5 (five) from Group B to E, taking at least one from each group.

Candidates are required to give answer in their own words as far as practicable.

**Group - A
(Multiple Choice Type Questions)**

1. Choose the correct alternative for the following: **10 × 1 = 10**
 - (i) When two inductive coils, having self-inductance L_1, L_2 and mutual inductance M in between them, are connected in series opposing, the equivalent inductance across the series combination will be
(a) $L_1 + L_2 + 2M$ (b) $L_1 + L_2 - 2M$ (c) $L_1 + L_2 + M$ (d) $L_1 + L_2 - M$.
 - (ii) Current division rule is valid for
(a) series circuit (b) parallel Circuit
(c) resonant circuit (d) all of these.
 - (iii) If the RMS value of current is 12.25 A, its peak value is
(a) 17.3A (b) 8.66 A (c) 12.25A (d) none of these.
 - (iv) In a parallel RLC circuit, the currents through the capacitor and the inductor are equal. What is the power factor of the circuit?
(a) lagging (b) leading (c) unity (d) 0.5.
 - (v) The property of an electrical circuit that dissipates electric energy is called
(a) resistance (b) reactance (c) conductance (d) inductance.
 - (vi) For a network with b branches and n nodes, the number of twigs for a selected tree and the number of links with respect to this tree are
(a) $(n+1)$ and $(b-1)$ (b) $(n-1)$ and $(b-n+1)$
(c) n and b (d) $(1/n)$ and $(b+1)$.
 - (vii) Which of the followings is correct for Z_{21} in a two-port network?
(a) $\frac{Y_{21}}{\det Y}$ (b) $\frac{Y_{12}}{\det Y}$ (c) $-\frac{Y_{21}}{\det Y}$ (d) $-\frac{Y_{12}}{\det Y}$.

- (viii) A current dependent current source is realized using a/an
 (a) inductor (b) bipolar junction transistor
 (c) field effect transistor (d) diode.
- (ix) The most elementary form of a loop which cannot be further divided into other loops is called
 (a) node (b) branch (c) loop (d) mesh.
- (x) Time constant of an RC series circuit is
 (a) RC (b) 1/RC (c) R/C (d) C/R.

Group - B

2. (a) Show that the resonating frequency of a series RLC circuit is independent of resistance(R).

- (b) Find the RMS value of the current $i(t)$ in the circuit shown in Fig. 1.

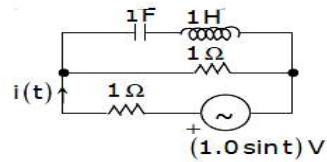


Fig. 1 6 + 6 = 12

3. (a) Derive an expression of the bandwidth (BW) of a series resonant circuit in terms of R, L and C showing the current frequency curve for the series RLC circuit.
- (b) Derive an expression of the quality factor (Q_0) of a series resonant circuit in terms of R, L and C. Express quality factor in terms of BW.

(5 + 1) + (5 + 1) = 12

Group - C

4. (a) Find the steady state values of the following functions.

(a) $F(s) = \frac{(s+1)}{s(s+1)}$

(b) $G(s) = \frac{e^{-st}}{s(s+1)}$

- (b) A current $i(t)$ flows through the circuit of Fig. 2, when the switch is closed at $t=0$ sec. Find the expressions of (a) current $i(t)$, and (b) rate of change of current ($di(t)/dt$) for $t>0$.

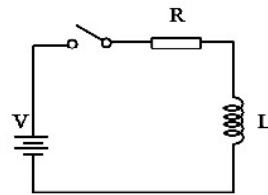


Fig.2

(3 + 3) + (4 + 2) = 12

5. (a) Find the inverse Laplace transform of the following function

$$F(s) = \frac{(s+2)}{s(s+1)(s+2)}$$

Using the initial value theorem, find the value of the above function at $t=0$.

- (b) Write the Laplace transforms of the following time domain functions:
 (i) unit impulse (ii) unit step
 (iii) exponentially decaying (iv) unit parabola.

(6 + 2) + 4 = 12

Group - D

6. (a) Derive z-parameters of the network shown in the Fig. 3.

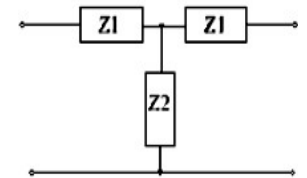


Fig. 3

where, $Z1 = (4+j3)\Omega$, and $Z2 = (3-j3)\Omega$. Is the network symmetrical and reciprocal?

- (b) Find the current through the resistor R in the circuit shown in Fig. 4.

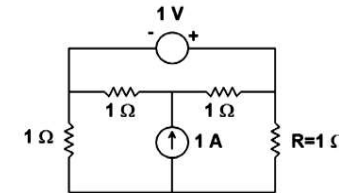


Fig. 4

(4 + 1 + 1) + 6 = 12

7. (a) Consider the electrical circuit shown in the Fig. 5. Obtain the incidence and tie-set matrices.

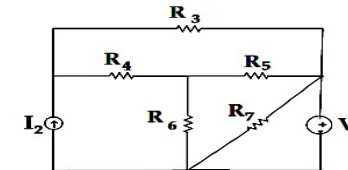


Fig. 5.

- (b) What is a reduced incidence matrix? How does one find the number of possible trees using a reduced incidence matrix? Explain with an example.

(4 + 4) + 4 = 12