

**BASIC ELECTRONICS
(ECEN 1011)**

Time Allotted : 3 hrs

Full Marks : 70

Figures out of the right margin indicate full marks.

*Candidates are required to answer Group A and
any 5 (five) from Group B to E, taking at least one from each group.*

Candidates are required to give answer in their own words as far as practicable.

**Group - A
(Multiple Choice Type Questions)**

1. Choose the correct alternative for the following: **10 × 1 = 10**
 - (i) JFET is a

(a) current controlled device	(b) voltage controlled device
(c) temperature controlled device	(d) none of these.
 - (ii) If the a.c. input to a half-wave rectifier is an r.m.s value of $400/\sqrt{2}$ volts, then diode PIV rating is

(a) $400/\sqrt{2}$ V	(b) 400 V
(c) $400 \times \sqrt{2}$ V	(d) none of the above.
 - (iii) In Enhancement n-channel MOSFET, an induced n-type channel can be produced between the source and the drain if

(a) $V_{GS} = 0$	(b) V_{GS} is positive
(c) V_{GS} is negative	(d) None of these.
 - (iv) Which of the following devices has the highest input impedance?

(a) JFET	(b) MOSFET
(c) Crystal diode	(d) ordinary transistor.
 - (v) The active components in an IC are

(a) Resistors	(b) Capacitors
(c) Transistors and diodes	(d) None of the above.
 - (vi) The ripple factor of a bridge rectifier is

(a) 0.482	(b) 0.812	(c) 1.11	(d) 1.21.
-----------	-----------	----------	-----------
 - (vii) The Slew rate of an ideal op-amp is

(a) zero	(b) infinity
(c) less than unity	(d) greater than unity.
 - (viii) The gain of an amplifier with feedback is known as

(a) Resonant gain	(b) Open loop gain
(c) Closed loop gain	(d) None of the above.

- (ix) In a Common Base BJT, for a fixed emitter base junction forward bias, increase in reverse bias across the collector base junction,

(a) increases emitter current	(b) decreases emitter current
(c) keeps emitter current constant	(d) makes emitter current zero.
- (x) If the temperature of an n-type semiconductor is increased then it becomes

(a) More n-type	(b) P-type
(c) Intrinsic	(d) None of the above.

Group - B

2. (a) Explain the mechanism of Zener breakdown in p-n junction and explain how it differs from avalanche breakdown.
 (b) Explain the drift and diffusion mechanism of charge carriers in a semiconductor.
 (c) Calculate the thermal equilibrium electron and hole concentration in a germanium sample for a given doping density. Assume that the germanium sample is at $T=300\text{k}$ in which $N_d = 5 \times 10^{13} \text{ cm}^{-3}$ and $N_a = 0$. Assume that $n_i = 2.4 \times 10^{13} \text{ cm}^{-3}$.
(3 + 2) + 4 + 3 = 12
3. (a) Plot the volt-ampere curve for a P-N junction diode and explain the nature of this curve.
 (b) What is ripple factor? Evaluate the ripple factor and efficiency of a half-wave rectifier.
 (c) AC voltage of 230 volt is applied to a half-wave rectifier through a transformer of turn ratio 10:1. The load resistance value is 1 K Ω and diode resistance is 20 Ω . Determine,
 - (i) I_m , I_{dc} , and I_{rms}
 - (ii) DC power output
 - (iii) AC power input
 - (iv) Efficiency of rectification**3 + (2 + 3) + 4 = 12**

Group - C

4. (a) Discuss the static characteristics of an n-p-n transistor in Common Base configuration.
 (b) Explain the circuit diagram for Fixed-biased configuration considering an n-p-n transistor in CE mode. Derive the expression for its stability factors.
6 + (3 + 3) = 12

5. (a) Derive the relationship between α and β in a BJT.

(b) Draw the collector to base bias BJT amplifier circuit


Derive

(i) B

(ii) C

(iii) S

What d

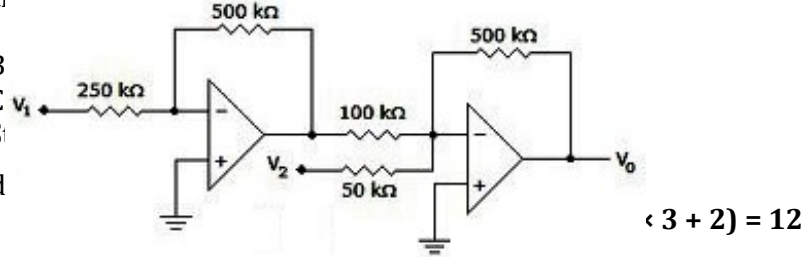

Group - D

6. (a) With the help of appropriate diagram explain the operation of an n-channel JFET.

(b) Draw and explain the drain and transfer characteristics of such n-channel JFETs.

6 + 6 = 12

7. (a) Why is FET called unipolar transistor? What do you mean by pinch-off voltage for n-channel JFET?

(b) What is the major physical difference between an enhancement-type and a depletion-type MOSFET? Draw the typical volt-ampere drain characteristics curve of a p-channel enhancement type MOSFET.

(c) In an n-channel JFET, I_{DSS} is 6 mA and $V_p = -6V$. Find the minimum value of V_{DS} for pinch-off operation. Determine drain current at $V_{GS} = -3V$.

(1 + 2) + (3 + 2) + 4 = 12

Group - E

8. Write short notes on any three of the followings:

(i) Light Emitting Diode (LED)

(ii) CMRR

(iii) Integrated Circuit

(iv) Virtual Ground.

4 + 4 + 4 = 12

9. (a) Describe the use of an op-amp as an integrator and derive its input-output relation. Draw its relevant input and output waveforms.

(b) In Fig.1. If $V_1=0.5V$ and $V_2=0.1V$, find V_o .

Fig.1

6 + 6 = 12