

**ELECTRONIC INSTRUMENTATION AND MEASUREMENT
(AEIE 3202)**

Time Allotted : 3 hrs**Full Marks : 70***Figures out of the right margin indicate full marks.*

*Candidates are required to answer Group A and
any 5 (five) from Group B to E, taking at least one from each group.*

Candidates are required to give answer in their own words as far as practicable.

**Group - A
(Multiple Choice Type Questions)**

1. Choose the correct alternative for the following: **10 × 1 = 10**
 - (i) The capture range of a PLL depends on
 - (a) phase detector
 - (b) cut off frequency of LPF
 - (c) amplifier gain
 - (d) none of these.
 - (ii) In a CRO the brightness control is adjusted by adjusting the potential applied to the
 - (a) cathode
 - (b) first focussing anode
 - (c) horizontal deflection amplifier
 - (d) grid.
 - (iii) For a digital voltmeter having 4-1/2 digit display, the input voltage of 0.8654V on 10V range will be displayed as
 - (a) 0.865 V
 - (b) 0.86 V
 - (c) 0.8654 V
 - (d) 0.8 V.
 - (iv) An OPamp based non inverting amplifier has biasing voltages +12V & -12V and gain 10. For the input of 2 volt the output voltage will be
 - (a) +20 V
 - (b) + V_{sat}
 - (c) +8 V
 - (d) - V_{sat}.
 - (v) The commercially available chip for VCO is
 - (a) NE505
 - (b) NE566
 - (c) NE565
 - (d) NE506.
 - (vi) The output frequency of VCO having external capacitance 500pF, external resistance 10Kohm, dc control voltage 10V and supply voltage V⁺ = 12 V is
 - (a) 50 KHz
 - (b) 20 KHz
 - (c) 66 KHz
 - (d) 80 KHz.
 - (vii) Deflection factor of a CRO is expressed in
 - (a) Ω/V
 - (b) cm/V
 - (c) V/cm
 - (d) V/Ω.

- (viii) If the phase difference between two same frequency signals applied to both vertical & horizontal plates is 180°, then the Lissajous figure will be
 - (a) a straight line
 - (b) a circle
 - (c) an ellipse
 - (d) a hyperbola.
- (ix) Post deflection acceleration system is provided in CRT to
 - (a) focus the electron beam
 - (b) reduce noise
 - (c) increase brightness of display
 - (d) reduce heat.
- (x) Charge amplifier is used in
 - (a) VCO
 - (b) Hall effect transducer
 - (c) piezoelectric transducer
 - (d) ramp type DVM.

Group - B

2. (a) Draw the circuit for a FET input voltmeter using dual emitter follower and an input attenuator. Hence show how the input voltage is measured by it.
- (b) What are the disadvantages of dc voltmeter while used for measurement of low voltage? How is it overcome by using chopper stabilized dc voltmeter?
(3 + 4) + (2 + 3) = 12
3. (a) What is the advantage of thermocouple type true r.m.s. voltmeter over other ac electronic voltmeter? With the circuit diagram of it show how it is advantageous.
- (b) Design a current mirror circuit and explain its operation. What is its use in electronic circuits?
(2 + 5) + (4 + 1) = 12

Group - C

4. (a) Using a Schmitt trigger and a ramp generator design a time base circuit for CRO. Explain the operation of it. What is the significance of the term TIMES/DIV regarding time-base of CRO?
- (b) Explain the operation of 10:1 attenuation probe used for CRO.
(3 + 4 + 2) + 3 = 12
5. (a) Draw the block diagram of sampling, storage and display unit of a digital storage oscilloscope. How is an input waveform sampled, stored and then recovered to display in a digital storage oscilloscope?

- (b) A 1V signal (V_s) with a source resistance of $R_s = 600\Omega$ is connected to an oscilloscope which has an input impedance of $R_i = 1\text{ M}\Omega$ in parallel with $C_i = 30\text{pF}$. The coaxial cable has a capacitance of $C_{cc} = 100\text{pF}$. Calculate the oscilloscope terminal voltage (V_i) when the signal frequency is 100Hz. Also determine the frequency at which V_i is 3dB below V_s .

$$(3 + 6) + 3 = 12$$

Group – D

6. (a) How is a time-base generation circuit giving a 100Hz clock signal made by using 1 MHz crystal oscillator and decade counters?
- (b) How is the unknown frequency of an ac signal measured by using a digital frequency meter? Calculate the percentage error in measuring the input signal frequency of 100MHz by digital frequency meter.

$$3 + (7 + 2) = 12$$

7. (a) Explain the operation of dual-slope integrating type DVM.
- (b) For an input voltage an 8-bit ADC having reference voltage 5volt gives digital output 11010010. Find the input voltage. What will be the display voltage if this input voltage is displayed in a 4 & ½ digit display unit for 100 volt range?

$$7 + 5 = 12$$

Group – E

8. (a) How parallel connection method of Q meter is used to find impure capacitance and inductance and their Q values.
- (b) What are the possible errors in measurement of Q value of unknown coil? What are the remedies to minimize these errors?

$$7 + (2 + 3) = 12$$

9. (a) Explain the operation of a swept superheterodyne spectrum analyzer. What is resolution bandwidth of spectrum analyzer?
- (b) What are the different modules of virtual instrumentation? Explain these by showing the architecture of it.

$$(5 + 1) + 6 = 12$$