B.TECH/AEIE/3RD SEM/AEIE 2102 (BACKLOG)/2019





6 + 6 = 12

Calculate z-parameters of the network shown in the Fig.8. (b)



where, $Z1 = 2 \Omega$, and $Z2 = 4 \Omega$. Is the network symmetrical and reciprocal?



Draw the oriented graph, one tree and its co-tree for an electrical 8. (a) circuit as shown in the Fig.9.



The driving point impedance of a circuit is given by (b)

$$Z(s) = \frac{(s+1)}{s(s+2)}$$

Realize a circuit using any one of the Foster's forms or any of the Cauer's forms. 4 + (4 + 4) = 12

- Design a low-pass active filter at a cut-off frequency of 1 kHz with a 9. (a) pass band gain of 2.
 - Propose the type of the filter circuit as shown in Fig.10. (b)



B.TECH/AEIE/3RD SEM/AEIE 2102 (BACKLOG)/2019

CIRCUIT THEORY AND NETWORKS (AEIE 2102)

Time Allotted : 3 hrs

Full Marks: 70

Figures out of the right margin indicate full marks.

Candidates are required to answer Group A and anv 5 (five) from Group B to E, taking at least one from each group.

Candidates are required to give answer in their own words as far as practicable.

Group – A (Multiple Choice Type Questions)

- 1. Choose the correct alternative for the following: $10 \times 1 = 10$
 - (i) Voltage divider rule is valid for (b) parallel circuit (a) series circuit (c) resonant circuit (d) all of these.
 - Two coils having self-inductances L1, L2 and mutual inductance M in (ii) between them are connected in series, adding the equivalent inductance across the series combination will be (b) L1 + L2 - 2M (a) L1 + L2 + 2M
 - (c) L1 + L2 + M (d) L1 + L2 - M. A voltage source is described by v(t) = 1. cost volts. The RMS value of (iii) v(t) in volts is

(a)
$$\sqrt{\frac{3}{2}}$$
 (b) $\sqrt{\frac{2}{3}}$ (c) 1 (d) $\sqrt{\frac{1}{2}}$

- The electrical component that dissipates electric energy (iv) (a) resistor (b) capacitor (d) all of the. (c) inductor
- If the number of nodes is n, then the number of twigs is t, (v) (a) (n + 1)(b) (n - 1) (c) n (d) (1/n).
- Time constant of an RC circuit is (vi) (a) RC (b) R/C (c) 1/RC (d) C/R.
- (vii) Which of the followings is correct for Z_{21} in a two-port network?

(a)
$$\frac{Y_{21}}{\det Y}$$
 (b) $\frac{Y_{12}}{\det Y}$ (c) $-\frac{Y_{21}}{\det Y}$ (d) $\frac{-Y_{12}}{\det Y}$
AEIE 2102 1

Fig. 10

6 + 6 = 12

4

B.TECH/AEIE/3RD SEM/AEIE 2102 (BACKLOG)/2019

- (viii) Thevenin's voltage of a circuit comprising of dependent source and resistive components is
 (a) finite value
 (b) 0A < V_{th} < 1V
 (c) 0 V
 (d) cannot be determined.
- (ix) The most elementary form of a loop which cannot be further divided into other loops is called
 (a) node
 (b) branch
 (c) loop
 (d) mesh.
- (x) In an RLC series circuit, the power factor at resonance is (a) lagging (b) leading (c) unity (d) zero.

Group – B

- 2. (a) What are the half power points of a series RLC circuit? Show the current versus frequency curve for the series RLC circuit. How does the resonating current relate with the cut-off frequencies?
 - (b) Two identical coupled inductors are connected in series. The measured inductances for the two possible series connections are 380 H and 240 H. Find their mutual inductance.
 - (2+2+2)+6=12
- 3. (a) Calculate the resonating frequency of a series RLC circuit.
 - (b) Find the RMS value of the current i(t) in the circuit shown in Fig.1.



Group – C

4. (a) In the circuit shown in the Fig.2 the initial charge on the capacitor is 0 (zero) coulomb. Find an expression of the current through the capacitor after the switch is closed at t = 0 second.



(b) Find the steady state values of the following functions.

B.TECH/AEIE/3RD SEM/AEIE 2102 (BACKLOG)/2019

(i)
$$F(s) = \frac{(s+2)}{s(s+3)}$$
 (ii) $G(s) = \frac{e^{-2st}}{s(s+4)}$





6 + (3 + 3) = 12

(b) Find the time-constant of the circuit across the terminals A and B as shown in Fig.4.



Group – D

6. (a) Draw the Thevenin's equivalent circuit across the load R_2 of the circuit shown in the Fig.5.



(b) Find the Maximum power transferred to the load resistor R_L in the circuit of Fig.6.



6 + 6 = 12

7. (a) Two 2-port networks N1 and N2 are connected as shown in Fig.7. The ABCD parameters are given as

AEIE 2102

2

AEIE 2102

3