

(b) Find the admittance parameters for a two port network in shown Fig. 9.

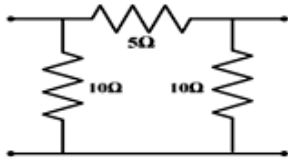


Fig. 9

Check the symmetry and reciprocity of the above network.

$(4 + 2) + 6 = 12$

7. (a) Fig. 10 represents a series RLC circuit. Find the value of capacitor C needed to have critically damped response for $i(t)$. The values of R and L are given as 40Ω and $4H$ respectively.

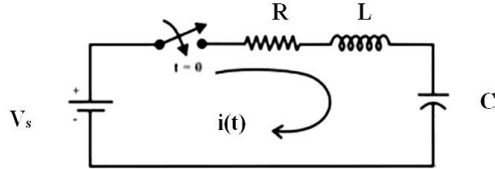


Fig. 10

(b) The capacitor, shown in Fig. 11, is initially charged to $+10V$. The switch closes at time $t=0$. Find the value of $V_c(t)$ at time $t=10ms$.

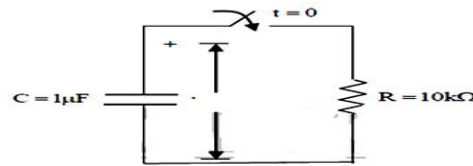


Fig. 11

$6 + 6 = 12$

Group – E

8. (a) Draw the frequency response of band pass and band reject filters.
 (b) Draw the circuit and explain the operation of 1st order HP Butterworth filter.

$(2 + 2) + 8 = 12$

9. (a) The driving point impedance of a circuit is given by $Z(s) = \frac{(s+1)}{s(s+2)}$. Draw a circuit showing the components and their values.

(b) Propose the type of the filter circuit as shown in Fig.12.

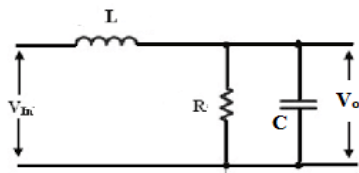


Fig. 12

$8 + 4 = 12$

**CIRCUIT THEORY AND NETWORK ANALYSIS
(AEIE 2103)**

Time Allotted : 3 hrs

Full Marks : 70

Figures out of the right margin indicate full marks.


Candidates are required to answer Group A and any 5 (five) from Group B to E, taking at least one from each group.

Candidates are required to give answer in their own words as far as practicable.

**Group – A
(Multiple Choice Type Questions)**

1. Choose the correct alternative for the following: $10 \times 1 = 10$

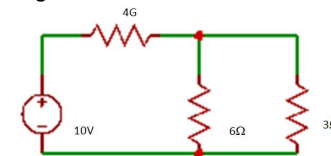- (i) In Superposition theorem, while considering a source, all other voltage sources are-----.
 (a) open circuited (b) short circuited
 (c) change its position (d) removed from the circuit
- (ii) In a parallel RLC circuit, the currents through the capacitor and inductor are equal. What is the power factor of the circuit?
 (a) lagging (b) leading (c) unity (d) 0.5.
- (iii) Find the current through 3Ω resistor in the circuit shown below.




- (a) 1 (b) 2 (c) 3 (d) 4.

- (iv) The most elementary form of a loop which cannot be further divided into other loops is called
 (a) node (b) branch (c) loop (d) mesh.
- (v) The impedance of an element is given by $(2 - j 3)\Omega$. The element comprises of
 (a) resistor and inductor (b) resistor and capacitor
 (c) capacitor and inductor (d) all of the above.
- (vi) Which of the followings is correct for Y_{21} in a two-port network?
 (a) $\frac{Z_{11}}{\det Z}$ (b) $-\frac{Z_{21}}{\det Z}$ (c) $\frac{Z_{21}}{\det Z}$ (d) $\frac{\det Z}{Z_{21}}$.
- (vii) A voltage dependent current source is realized using a/an
 (a) inductor (b) bipolar junction transistor
 (c) field effect transistor (d) diode.


- (viii) In a series RLC circuit, voltages across the resistor, inductor and capacitor are 3 V, 4 V and 4 V respectively, then the applied voltage is
 (a) 3 V (b) 4 V (c) 5 V (d) 7 V.
- (ix) A network, described by ABCD parameters, will be reciprocal if
 (a) $A=D$ (b) $(AD-BC)=1$ (c) $(AC-BD)=1$ (d) $(AD-BC)=0$.
- (x) In a pure inductive circuit if the supply frequency is reduced to $\frac{1}{2}$ (half), the current will be
 (a) reduced by half (b) doubled
 (c) reduced to one fourth (d) four times as high.

Group – B

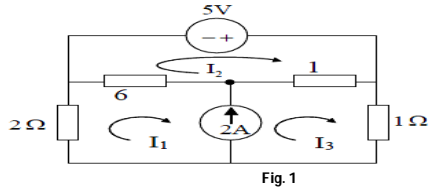2. (a) The circuit shown in Fig. 1, find the mesh currents I_1 , I_2 and I_3 .




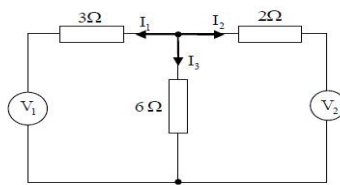- (b) In the circuit of Fig. 2, superposition is applied. When V_1 is set to 0 V, the current I_1 is +12A. When V_2 is set to 0V, the current is -12A. Find Current I_3 , when both sources are present in the circuit.



OR

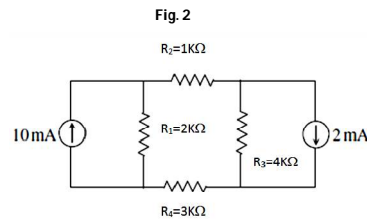Find the magnitude of current through the resistor R_2 shown in the Fig. 3.



6 + 6 = 12

3. (a) For the circuit shown in the Fig. 4, find the Thevenin's voltage and Thevenin's resistance.


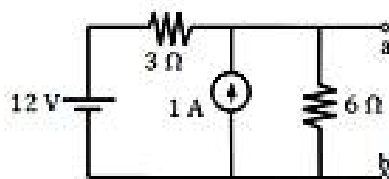


Fig. 4
2

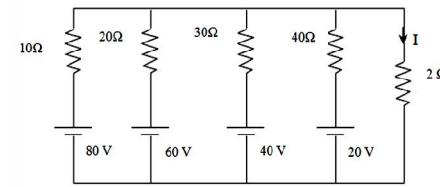- (b) Find the current I flowing through the 2Ω resistor in the circuit shown in Fig. 5.




Calculate the power dissipation through the 2Ω resistor.


(3 + 3) + (4 + 2) = 12

Group – C

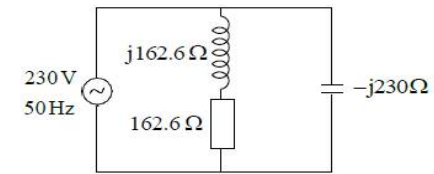4. (a) The circuit shown in fig. 6, a 230 V, 50 Hz single phase source is coupled to an RLC load. Find the magnitude of the active power (in VAR) supplied by the source.



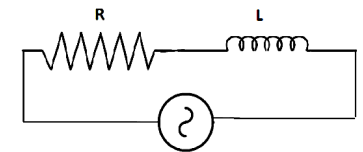
- (b) Determine the source voltage connected across an RL circuit (Fig. 7) if voltages across the resistor and inductor are 70 V and 20 V respectively. Show the associated phasor diagram.



(4 + 2) + 6 = 12

5. (a) The voltage across and the current through a load are expressed as follows:
 $v(t) = -20\sin(314t - 60^\circ)$ and $i(t) = 10\cos(314t + 60^\circ)$
 Find the average power consumed by the load.

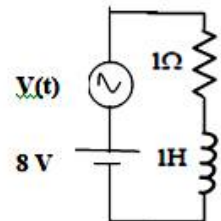- (b) Fig. 8 shows a circuit that has two sources connected in series. The instantaneous voltage of the AC source is given by $v(t) = 12\sin t$. If the circuit is in steady-state, then find the RMS value of the current flowing in the circuit.



6 + 6 = 12

Group – D

6. (a) Express Z parameters in terms of ABCD parameters.