

B.TECH/AEIE/7TH SEM/AEIE 4102/2019
POWER ELECTRONICS AND DRIVES
(AEIE 4102)

Time Allotted : 3 hrs

Full Marks : 70

Figures out of the right margin indicate full marks.

*Candidates are required to answer Group A and
any 5 (five) from Group B to E, taking at least one from each group.*

Candidates are required to give answer in their own words as far as practicable.

Group - A
(Multiple Choice Type Questions)

1. Choose the correct alternative for the following: **10 × 1 = 10**
- (i) In power electronics the solid state devices
(a) amplifiers (b) controlled resistors
(c) switches (d) none of these.
- (ii) Which of the following is not a current triggered device?
(a) thyristor (b) BJT
(c) triac (d) MOSFET.
- (iii) Power MOSFET is a
(a) voltage controlled device (b) current controlled device
(c) frequency controlled device (d) none of (a), (b) and (c).
- (iv) In forward blocking mode of SCR, the number of forward biased junction is
(a) 1 (b) 2
(c) 3 (d) 4.
- (v) The average output voltage is maximum when SCR is triggered at $\omega t =$
(a) π (b) 0
(c) $\pi/2$ (d) $\pi/4$.
- (vi) In a controlled rectifier a freewheeling diode is necessary if the load is
(a) inductive (b) resistive
(c) capacitive (d) all of (a), (b) and (c).
- (vii) For a full wave bridge inverter, the output voltage (V_o)
(a) $V_o = V_s/2$ for $0 < t < T/2$ (b) $V_o = V_s$ for $0 < t < T/2$
(c) $V_o = V_s$ for $T/2 < t < T$ (d) $V_o = -V_s$ for $T/2 < t < 3T/2$.
- (viii) A step-up chopper has V_s as the source voltage and k as the duty cycle. The output voltage for this chopper is given by
(a) $V_s (1 + k)$ (b) $V_s / (1 - k)$
(c) $V_s (1 - k)$ (d) $V_s / (1 + k)$.

B.TECH/AEIE/7TH SEM/AEIE 4102/2019

- (ix) A Schottky diode will have
(a) a low on state voltage and a small recovery time
(b) a low on state voltage and a high recovery time
(c) a high on state voltage and a low recovery time
(d) a high on state voltage and a high recovery time.
- (x) A cyclo-converter can be considered to be composed of two converters
(a) connected back to back (b) series connected
(c) parallel connected (d) series- parallel connected.

Group - B

2. Draw the V-I characteristics of TRIAC. State the different advantages and disadvantages of TRIAC. State and explain some of the application of TRIAC. **(4 + 4 + 4) = 12**
3. (a) What is an IGBT? Sketch the equivalent circuit and transfer characteristics of an IGBT.
(b) Compare the power MOSFETs with Power BJTs. **(4 + 4) + 4 = 12**

Group - C

4. (a) Draw and explain the different modes of operation using static V-I characteristic of thyristor. What is the effect of gate current on these characteristics?
(b) Define latching current and holding current. **(4 + 4) + 4 = 12**
5. (a) Explain the two-transistor analogy of thyristor. Derive an equation for anode current.
(b) How do you protect the thyristor from over voltages and currents? Explain the various protection schemes available now-a-days. **(4 + 2) + (2 + 4) = 12**

Group - D

6. (a) Explain the operation of a single- thyristor half- wave controlled rectifier and draw the input and output waveforms.
(b) Single phase half controlled rectifier is with resistive load where the delay angle is 45° . Find the (i) rectifier efficiency (ii) form factor and (iii) ripple factor. **6 + (2 + 2 + 2) = 12**

7. (a) What is current source inverter? Mention its merits and demerits compared to voltage source inverter.
- (b) A single-phase bridge inverter supplies bridge inverter supplies to series connected RLC load having $R=3\ \Omega$ and inductive reactance equal to $12\ \Omega$ at frequency of 5 kHz. The turn-off time of the thyristor is $14\ \mu\text{s}$. Assume 50% tolerance in circuit. Find the value of Capacitor for proper load commutation.
- (4 + 6) + 2 = 12**

Group - E

8. (a) With neat circuit diagram explain a step up chopper with resistive load. What is current limit control?
- (b) A step-up chopper operating at 20 kHz has non-conductive time of $20\ \mu\text{s}$. Calculate output voltage if the input voltage is 100 Volt DC.
- (4 + 4) + 4 = 12**
9. (a) Explain briefly the function of a Cycloconverter with proper circuit diagram.
- (b) A single -phase bridge type cyclo-converter has input voltage of 230 V, 50 Hz and load of $R = 10\ \Omega$. Output frequency is one-third of input frequency. For a triggering angle of 30° , calculate (i) rms value of output voltage (ii) rms current of each converter (iii) rms current of each thyristor and (iv) input power factor.
- 4 + (2 + 2 + 2 + 2) = 12**