

- (b) Explain in detail how can you construct a 16:1 MUX using 8:1 MUX and external gate.
- (c) Design a combinational circuit that converts a four bit binary number to a four bit Gray code number. Implement the circuit using suitable logic gates.

2 + 5 + 5 = 12

Group – E

8. (a) What is the difference between a latch and an edge triggered flip-flop?
- (b) Draw the circuit diagram of a clocked S-R flip-flop using NAND gates and explain its principle of operation.
- (c) Design a T flip flop using S-R flip-flop.
9. (a) What is the difference between an asynchronous and a synchronous counter?
- (b) Design a Mod-8 asynchronous up counter using J-K flip flop and explain its working principle. Draw the timing diagram.
- (c) Design a 4 bit shift register using D flip flop and explain its operation for right shift mode.

2 + 5 + 5 = 12

2 + 5 + 5 = 12

**ANALOG & DIGITAL ELECTRONICS
(ELEC 2102)**

Time Allotted : 3 hrs

Full Marks : 70

Figures out of the right margin indicate full marks.

Candidates are required to answer Group A and any 5 (five) from Group B to E, taking at least one from each group.

Candidates are required to give answer in their own words as far as practicable.

**Group – A
(Multiple Choice Type Questions)**

1. Choose the correct alternative for the following: **10 × 1 = 10**
- (i) The output of a differentiator circuit with square wave input is
 (a) triangular wave (b) impulse
 (c) parabola (d) step.
- (ii) Schmitt trigger is also known as
 (a) squaring circuit (b) blocking oscillator
 (c) sweep circuit (d) astable multivibrator.
- (iii) Let us consider an op-amp having a slew rate of 6 V/ μs. The undistorted peak-peak output voltage for an input sine wave of 2 MHz frequency is
 (a) 1.5 V (b) 0.95 V
 (c) 0.47 V (d) 3 V.
- (iv) Which of the following oscillators uses one inductor and two capacitors in the feedback circuit?
 (a) Hartley oscillator (b) Colpitts oscillator
 (c) Wien bridge oscillator (d) Phase shift oscillator.
- (v) The loop gain of an oscillator should be
 (a) zero (b) unity
 (c) 29 (d) 3.
- (vi) Which of the following is a weighted code?
 (a) 2421 (b) Excess-3
 (c) Gray (d) All of the above.
- (vii) The minimum number of NAND gates required to construct an XOR gate is
 (a) 3 (b) 4 (c) 5 (d) 8.

- (viii) The fundamental frequency of a crystal oscillator is
 - (a) directly proportional to the thickness of the crystal
 - (b) inversely proportional to the thickness of the crystal
 - (c) independent of the thickness of the crystal
 - (d) proportional to the temperature of the crystal.
- (ix) A latch is _____ sensitive
 - (a) both level and edge
 - (b) edge
 - (c) level
 - (d) neither level nor edge.
- (x) The number of flip-flops required to construct a Mod-32 binary counter is
 - (a) 3
 - (b) 4
 - (c) 5
 - (d) 8.

Group – B

- 2. (a) Realize the following linear differential equation using minimum number of OP-AMPs

$$2 \frac{d^2y}{dt^2} + 3 \frac{dy}{dt} + 2y = 10$$

- (b) Calculate the load voltage, I_1 , I_2 and I_z for the circuit shown in Fig. 1. Given that breakdown voltage of the zener diode is 5V, $R = 1k\Omega$ and $R_L = 1.2k\Omega$. Also determine the power consumed by the zener diode.

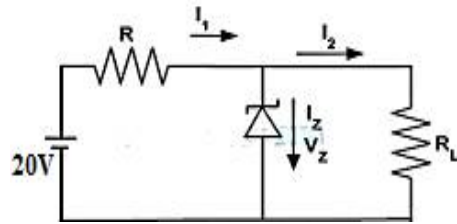


Fig. 1

- (c) Define input offset voltage of an OP-AMP.

6 + 5 + 1 = 12

- 3. (a) Determine the collector current I_c and collector-to-emitter voltage V_{CE} of the circuit shown in Fig. 2.

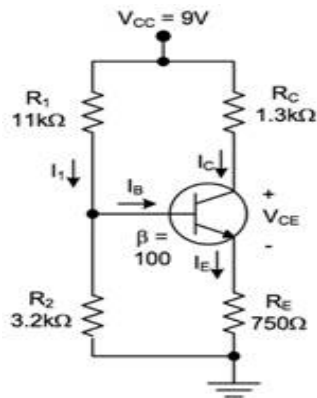


Fig. 2

- (b) For the circuit shown in Fig. 3, assuming diodes D_1 , D_2 and D_3 to be ideal, determine the DC components of voltages V_1 and V_2 .

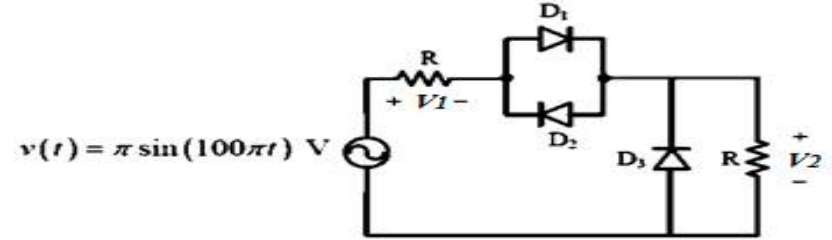


Fig. 3

6 + 6 = 12

Group – C

- 4. (a) Design an RC phase shift oscillator with oscillation frequency, $f_o = 200$ Hz.
- (b) State and explain Barkhausen criteria.
- (c) Draw a neat diagram of Hartley oscillator and derive the expression of oscillation frequency.

3 + 2 + 7 = 12

- 5. (a) Draw and explain the circuit of a triangular wave generator using two operational amplifiers where, one is used as a comparator and the other one is used as an integrator.
- (b) Draw a neat circuit diagram of a monostable multivibrator using op amp. Explain its principle of operation. Draw the output and capacitor voltage waveforms. Derive the expression of timing period.

4 + 8 = 12

Group – D

- 6. (a) What do you mean by a combinational circuit? Give two examples of combinational circuits.
- (b) Apply the knowledge of K map to simplify the following Boolean function and implement it using suitable logic gates:
 $F(A,B,C,D) = \sum_m (0,1,2,8,10,11,14,15) + \sum_d (3,13)$.
- (c) Design a full adder using NAND gate only.

2 + 5 + 5 = 12

- 7. (a) What is a decoder? What are its applications?