

- (b) Find the voltage drop equations for the oriented graph shown in the Fig.9.

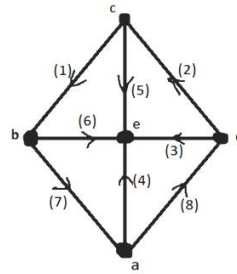


Fig. 9

$$6 + 6 = 12$$

7. (a) What are the impedance parameters and transmission parameters? Express impedance parameters in terms of transmission parameters.
- (b) Determine the y-parameters for the following two port network of the circuit shown in the Fig.10.

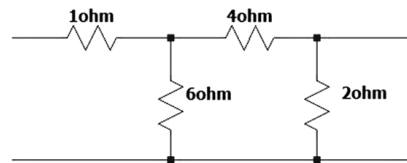


Fig.10

$$(2 + 4) + 6 = 12$$

Group – E

8. (a) Design a 1st order low pass filter having a dc gain of 4 and corner frequency of 1000Hz using ideal OPAMP.
- (b) Derive the transfer function of the following filter as shown in the Fig.11. Comment on the type of the filter.

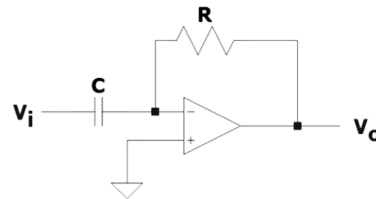


Fig.11

$$6 + 6 = 12$$

9. (a) Write a short note on ac analysis using PSPICE.
- (b) Write the source file for the following circuit shown in Fig.12 to find the voltage between the nodes (1, 2) and current through 1V source.

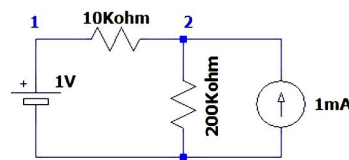


Fig.12

$$6 + 6 = 12$$

CIRCUIT THEORY & FILTERS (ECEN 2105)

Time Allotted : 3 hrs

Full Marks : 70

Figures out of the right margin indicate full marks.

Candidates are required to answer Group A and any 5 (five) from Group B to E, taking at least one from each group.

Candidates are required to give answer in their own words as far as practicable.

Group – A (Multiple Choice Type Questions)

1. Choose the correct alternative for the following: $10 \times 1 = 10$
- The reciprocity theorem is applicable for a network containing
 - independent sources only
 - dependent sources only
 - both dependent and independent sources
 - any one of dependent and independent sources.
 - Superposition theorem is not applicable for

(a) current calculation	(b) voltage calculation
(c) power calculation	(d) none of (a), (b) and (c).
 - In steady state inductor should behave as

(a) short circuit	(b) open circuit
(c) voltage source	(d) current source.
 - Time constant of series RL circuit is

(a) RL	(b) R/L	(c) L/R	(d) R+L.
--------	---------	---------	----------
 - For a network having N nodes and B branches, the number of links will be

(a) N	(b) N-1	(c) B-N+1	(d) B+N-1.
-------	---------	-----------	------------
 - In a series RC circuit, if the output is measured across the resistor, the circuit can be considered as a

(a) Band Pass Filter	(b) Band Reject Filter
(c) Low Pass Filter	(d) High Pass Filter.
 - The condition for reciprocity any two port network is

(a) $Z_{12} = Z_{21}$	(b) $Y_{22} = Y_{11}$	(c) $A - BC = 1$	(d) $Z_{12} = Y_{21}$.
-----------------------	-----------------------	------------------	-------------------------
 - Four capacitors each of 40 μF are connected in parallel, the equivalent capacitance of the system will be

(a) 40 μF	(b) 10 μF	(c) 20 μF	(d) 80 μF .
----------------------	----------------------	----------------------	------------------------

- (ix) If the Laplace transform of $f(t)$ is $F(s)$, then the Laplace transform of $e^{-at}f(t)$ is
 (a) $F(s+a)$ (b) $F(s-a)$ (c) $F(s/a)$ (d) $F(sa)$.
- (x) The 3dB frequency of a bandpass filter is calculated at
 (a) peak power point (b) half power point
 (c) quarter power point (d) none of (a), (b) and (c).

Group – B

2. (a) Determine the condition for the maximum power transfer to a resistive load in a resistive network.
 (b) Using superposition theorem find out the current I for the network shown in Fig.1.

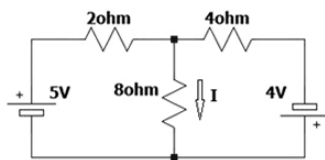


Fig.1

- (c) Find the equivalent resistance across the terminals a, b of the network shown in Fig. 2.

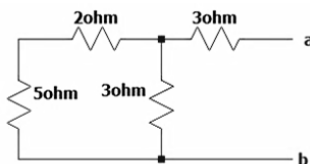


Fig.2

$$4 + 5 + 3 = 12$$

3. (a) Find the Thevenin equivalent of the circuit shown in the Fig.3 across the terminals a, b.

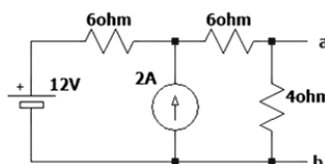


Fig.3

- (b) Find the value of i_o and v_o for the following circuit shown in the Fig.4.

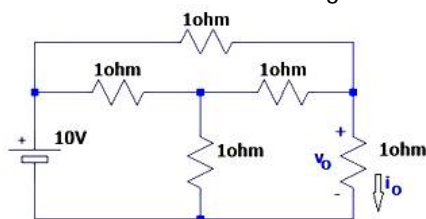


Fig.4

$$6 + 6 = 12$$

Group – C

4. (a) Derive the current expression for a series R-C network excited by a step voltage of height V considering zero initial condition. Also plot the current.
 (b) Determine the inductor current $i_L(t)$ for both $t < 0$ and $t > 0$ for the circuit shown in the Fig. 5.

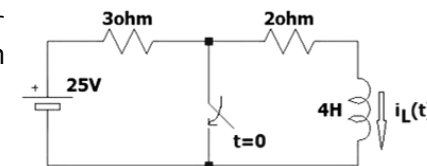


Fig.5

$$(5 + 1) + 6 = 12$$

5. (a) The switch S in the network shown in the Fig.6 is opened at $t = 0$. Calculate the current $i(t)$ for $t > 0$.

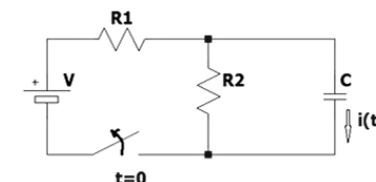


Fig.6

- (b) Calculate the Laplace transform of the given periodic function as shown in the Fig.7.
 $g(t) = \sin(\pi t)$, for $0 < t < 1$
 0 , for $1 < t < 2$.

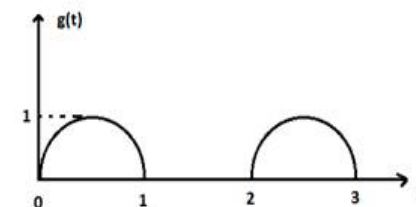


Fig.7

$$6 + 6 = 12$$

Group – D

6. (a) Derive the Tie-set matrix for the network shown in the Fig.8.

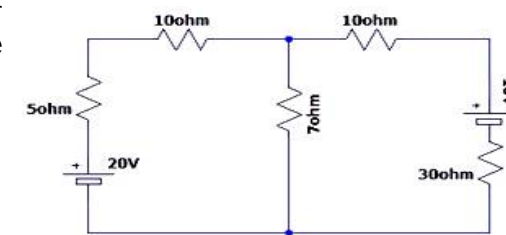


Fig.8