

## CIRCUIT AND NETWORK THEORY (ECEN 2102)

Time Allotted : 3 hrs

Full Marks : 70

*Figures out of the right margin indicate full marks.*

*Candidates are required to answer Group A and  
any 5 (five) from Group B to E, taking at least one from each group.*

*Candidates are required to give answer in their own words as far as  
practicable.*

### Group - A (Multiple Choice Type Questions)

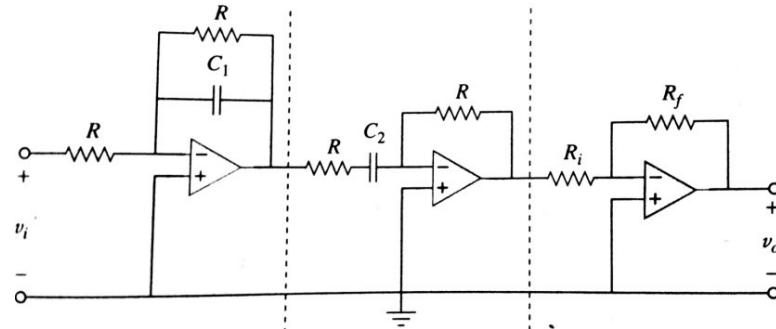


Figure 12

- (b) Design a second order band pass filter with a centre frequency of 1kHz and bandwidth of 200Hz. Take the centre frequency gain to be 2.  
6 + 6 = 12

1. Choose the correct alternative for the following: **10 × 1 = 10**

- (i) The open circuit voltage at the terminal of load  $R_L$  is 60V. Under the condition of the maximum power transfer the load voltage will be  
(a) 60V                      (b) 15V                      (c) 20V                      (d) 30V.
- (ii) Superposition theorem is not applicable to networks containing  
(a) Nonlinear elements                      (b) dependent voltage sources  
(c) transformers                              (d) dependent current sources.
- (iii) Two two-port networks are connected in cascade. The parameters of the single equivalent network are obtained by multiplying the individual  
(a) z-parameter matrices                      (b) h-parameter matrices  
(c) y-parameter matrices                      (d) ABCD-parameter matrices.
- (iv) The rank of f-cut-set matrix of a connected graph with n number of nodes is  
(a) n-1                      (b) n                      (c) 2n+1                      (d) n+1.
- (v) In a series RC circuit, if the output is measured across the capacitor, the circuit can be considered as a  
(a) Band Pass Filter                              (b) Band Reject Filter  
(c) Low Pass Filter                              (d) High Pass Filter.

- (vi) The reciprocity theorem is applicable for a network containing
  - (a) Independent sources only
  - (b) Dependent sources only
  - (c) Both dependent & independent sources
  - (d) Any one of dependent & independent sources.
- (vii) For steady state condition capacitor should behave as
  - (a) Short circuit
  - (b) Open Circuit
  - (c) Voltage Source
  - (d) Current Source.
- (viii) The condition for reciprocity of any two port network is
  - (a)  $Z_{12} = Z_{21}$
  - (b)  $Y_{12} = Y_{11}$
  - (c)  $AC - BD = 1$
  - (d)  $h_{11} = h_{22}$ .
- (ix) If the Laplace transform of  $f(t)$  is  $F(s)$ , then the Laplace transform of  $e^{-at}f(t)$  is
  - (a)  $e^{-sa}F(s)$
  - (b)  $e^{sa}F(s)$
  - (c)  $F(s+a)$
  - (d)  $F(s-a)$ .
- (x) The centre frequency of a bandpass filter is always equal to
  - (a) the bandwidth
  - (b) arithmetic average of the cut off frequencies
  - (c) 3dB frequency
  - (d) the product of bandwidth & quality factor

**Group - B**

- 2. (a) Find the open circuit voltage across the terminals a & b of the following circuit (Figure 1).

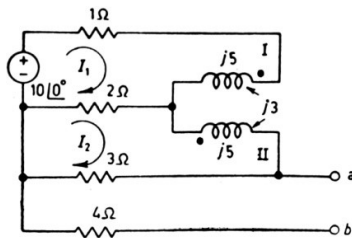


Figure 1

- (b) Find the reading of the voltmeter V in the given circuit. Interchange the current source and the voltmeter and verify the Reciprocity theorem (Figure 2).

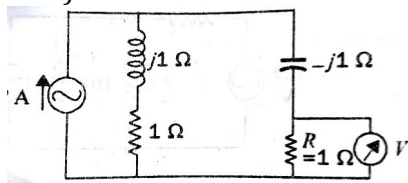


Figure 9

(3 + 3) + 6 = 12

- 7. (a) What do you mean by driving point impedance of a network? Two four terminal networks are connected in cascade, show that the ABCD matrix of the overall network is the product of the ABCD matrices of the individual network.
- (b) Determine the z-parameters for the following network of Figure 10.

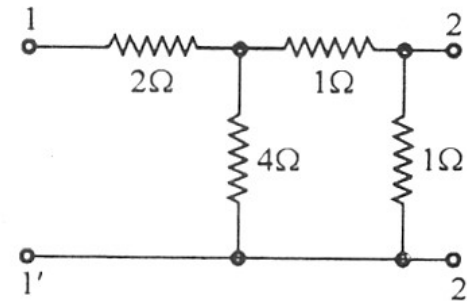


Figure 10

(2 + 4) + 6 = 12

**Group - E**

- 8. (a) Design a 1<sup>st</sup> order low pass filter having a dc gain of 10 and corner frequency of 2KHz using ideal OPAMP.
- (b) Derive the transfer function of the following filter of Figure 11. Comment on the type of the filter.

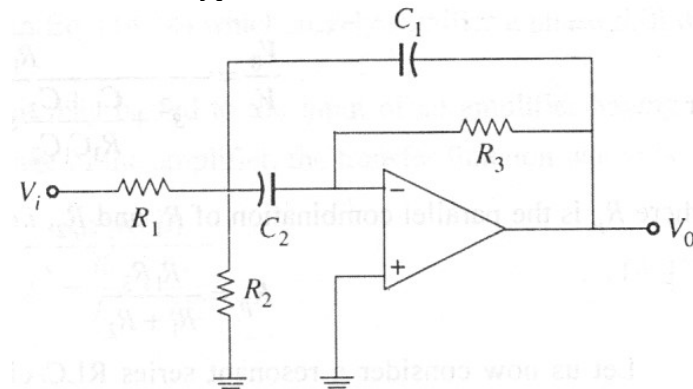


Figure 11

Figure 2

6 + 6 = 12

3. (a) Determine the value of R that will draw the maximum power from the rest of the circuit of Figure 3. Calculate the maximum power.

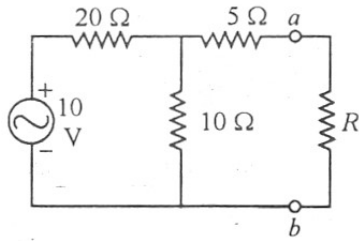


Figure 3

- (b) State the superposition theorem. Using any method find  $i_o$  in the circuit of Figure 4.

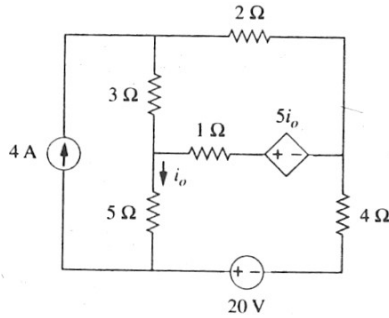


Figure 4

(5 + 1) + (1 + 5) = 12

**Group - C**

4. (a) A step input voltage of amplitude 'V' is applied to a series RLC circuit. Determine the current  $i(t)$  in the series circuit for  $t \geq 0$ . Explain the over, under and critical damping cases with proper plots.

- (b) The given circuit was in steady state before  $t=0$ . The switch is closed at  $t=0$ . Determine the mesh currents  $i_1$ ,  $i_2$  &  $i_3$  immediately after the switch closure at  $t=0^+$  (Figure 5).

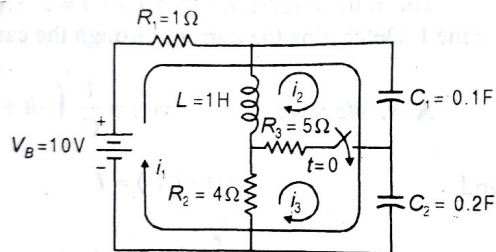


Figure 5

(4 + 3) + 5 = 12

- 5.(a) In the circuit of Figure 6, determine the voltage  $v(t)$  and the currents  $i_R(t)$  and  $i_L(t)$  for  $t > 0$ . The circulating current at  $t = 0^-$  in the RL loop is 1 amp clockwise.

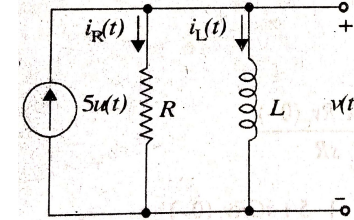


Figure 6

- Calculate the Laplace transform of the periodic function as shown in Figure 7.

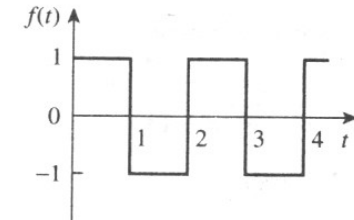


Figure 7

6 + 6 = 12

**Group - D**

6. (a) Find the tie-set and f-cut-set matrices using the given graph (Figure 8).

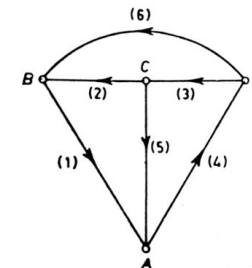


Figure 8

- (b) Form the fundamental cut-set matrix for the given network and hence find the matrix form of KCL equations (Figure 9).

