

**CIRCUIT THEORY & NETWORK ANALYSIS**  
**(AEIE 2103)**

**Time Allotted : 3 hrs**

**Full Marks : 70**

*Figures out of the right margin indicate full marks.*


*Candidates are required to answer Group A and  
any 5 (five) from Group B to E, taking at least one from each group.*

*Candidates are required to give answer in their own words as far as practicable.*

**Group – A**  
**(Multiple Choice Type Questions)**

1. Choose the correct alternative for the following: **10 × 1 = 10**

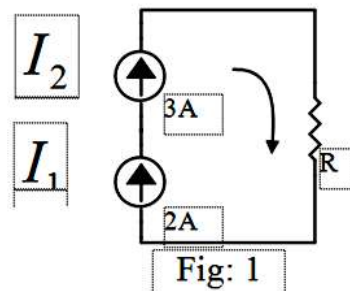- (i) A current dependent current source is realized using a/an  
(a) inductor (b) bipolar junction transistor  
(c) field effect transistor (d) diode
- (ii) A reciprocal circuit should have  
(a) only one independent source (b) at least two independent sources  
(c) one dependent source (d) independent and dependent sources
- (iii) Superposition theorem is not applicable for  
(a) voltage calculations (b) current calculations  
(c) power calculations (d) none of the above
- (iv) In a series RL circuit, voltages across the resistor and the inductor are 3 V and 4 V respectively, then the applied voltage is  
(a) 3V (b) 4V (c) 5V (d) 7V
- (v) Two ideal current sources of  $I_1 = 2A$  and  $I_2 = 3A$  are connected in series as show in the Fig.1.




The current through R will be

- (a) 2A (b) 3A (c)  $\sqrt{3^2 + 2^2}$  (d) cannot be determined

- (vi) Which of the followings is correct for  $Z_{21}$  in a two-port network?  
 (a)  $\frac{Y_{11}}{\det Y}$  (b)  $\frac{-Y_{21}}{\det Y}$  (c)  $-\frac{Y_{21}}{\det Y}$  (d)  $\frac{Y_{22}}{\det Y}$
- (vii) An active low pass filter with RC passive components has the cut-off frequency  
 (a)  $\frac{1}{2\pi RC}$  (b)  $2\pi RC$  (c)  $2\pi\sqrt{RC}$  (d)  $\frac{1}{2\pi\sqrt{RC}}$
- (viii) The function of an Inductor is to oppose any change in\_\_\_\_.  
 (a) current (b) voltage  
 (c) voltage and current. (d) neither voltage nor current.
- (ix) The voltage and current in a circuit are given by  $v(t) = 10\sin(t + 30^\circ)$  and  $i(t) = 10\sin(t - 30^\circ)$ . The power consumed in the circuit is  
 (a) 25 W (b) 50 W (c) 100 W (d) 12.5 W
- (x) If R and L are connected to a supply voltage (v) through an initially open toggle switch, the value of the currents at  $t=0$  and infinity through the inductor after the closure of the switch will be respectively  
 (a)  $V/R, 0$  (b)  $0, V/R$  (c)  $\infty, 0$  (d)  $0, \infty$


**Group - B**

2. (a) Find the current through the resistor R in the circuit shown in Fig. 2.

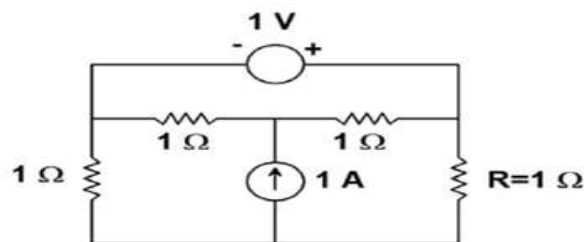

**Fig. 2**


- (b) Find the potential difference across the  $2\Omega$  resistor in the circuit of Fig.3.

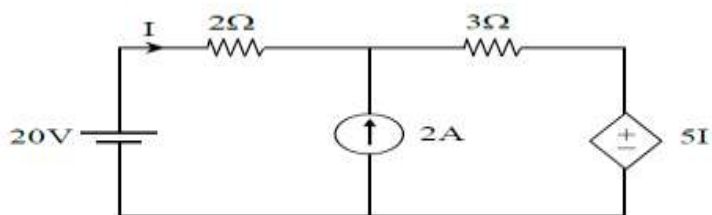

**Fig. 3**

**6 + 6 = 12**

3. (a) State and proof Maximum power transfer theorem for a DC circuit.
- (b) For the circuit shown in Fig.4, use superposition theorem to compute current I.

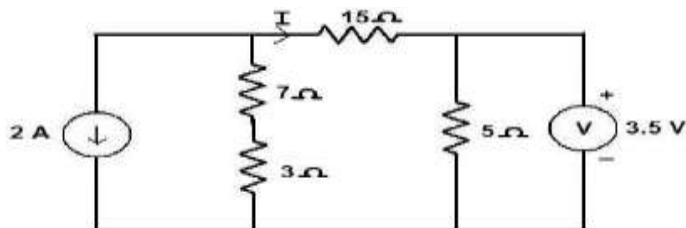


**Fig.4**

**6 + 6 = 12**

**Group – C**

4. (a) Derive the condition of resonance of a series RLC circuit. If the resistance in that circuit is doubled then what change in the resonating frequency will be observed? Justify.

- (b) An RLC circuit, connected to a sinusoidal current source as shown in the Fig. 5, is under resonance. Find the ratio of the magnitudes of the  $I_L$  and  $I_R$ .

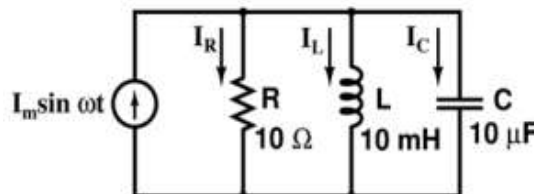**Fig.5****(4 + 2) + 6 = 12**

5. (a) What is the co-efficient of coupling in a magnetically coupled circuit? What is its practical range?

For the circuit in the Fig. 6, the following data are given:

(i) 45% of the primary flux gets linked with the secondary


(ii)  $i_1(t) = 4 \sin 2t$  A

(iii)  $i_2 = 0$  A.

Find

(A) the coefficient of coupling and


(B)  $v_2$ .

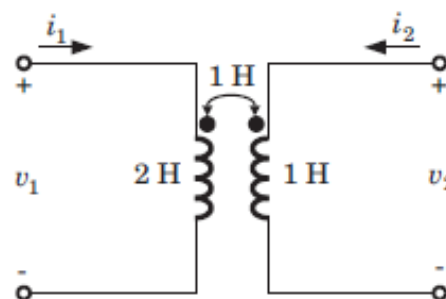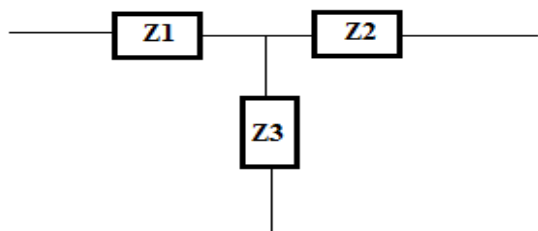**Fig. 6**

- (b) In a RLC Series resonance circuit,  $R = 10 \Omega$ ,  $L = 20 \text{ mH}$  and  $C = 0.5 \mu\text{F}$ . Find (i) Quality factor and (ii) Bandwidth

**(1 + 1 + 3 + 3) + (2 + 2) = 12****Group – D**

6. (a) Derive Z-parameters of the network shown in the Fig.7.

**Fig. 7**

Where,  $Z1 = (3 + j4) \Omega$ ,  $Z2 = 3 \Omega$  and  $Z3 = (3 - j4) \Omega$ .

Justify the symmetry and Reciprocity of the network.

- (b) Express Z- parameters in terms of h-parameters.

**(4 + 2) + 6 = 12**

7. (a) A 0.1 capacitor charged to 10 V is discharged through a  $1\text{K}\Omega$  resistor. Find the time required for the voltage across the capacitor to drop to 1V.

- (b) In the circuit shown in the Fig.8, the initial charge on the capacitor is 0 (zero) coulomb. Find an expression of the rate of change of current through the capacitor for  $t > 0$  after the switch is closed at  $t=0$  second.

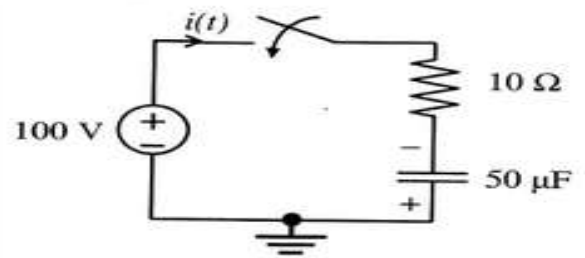


Fig. 8

5 + 7 = 12

### Group - E

8. (a) Draw the scheme of realizing a band pass filter.  
(b) Analyze the circuit in Fig. 9 to determine the type of the filter.

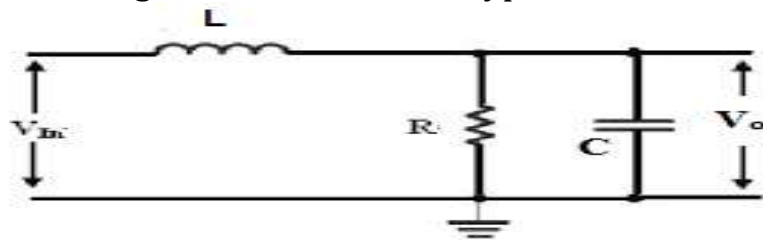


Fig. 9

If the components L and C in Fig. 9 are transposed then what type of filter may be realized?

4 + (4 + 4) = 12

9. (a) Find the Y-parameters for the circuit shown in Fig. 10.

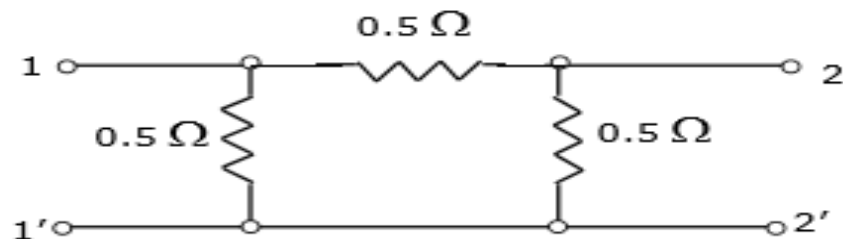


Fig. 10

- (b) Find the Thevenin's equivalent resistance across the terminals a and b of the circuit in Fig. 11.

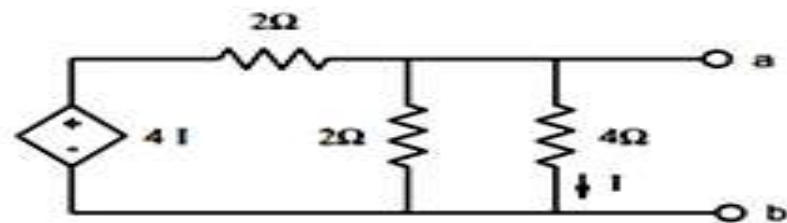


Fig. 11

6 + 6 = 12

Department & Section	Submission Link
AEIE	<a href="https://classroom.google.com/c/MTIxODk4ODA4NzY3/a/Mjc0MDY4MTQxNDg5/details">https://classroom.google.com/c/MTIxODk4ODA4NzY3/a/Mjc0MDY4MTQxNDg5/details</a>