

DIGITAL LOGIC
(ECEN 2104)

Time Allotted: 3 hrs

Full Marks : 70

Figures out of the right margin indicate full marks.

Candidates are required to answer Group A and any 5 (five) from Group B to E, taking at least one from each group.

Candidates are required to give answer in their own words as far as practicable.

Group – A
(Multiple Choice Type Questions)

1. Choose the correct alternative for the following: **10 × 1 = 10**
- (i) Which of the following is not a valid octal number?
(a) 1101 (b) 740 (c) 970 (d) 220.
- (ii) What is the Gray code word for the binary 101011?
(a) 101011 (b) 110101 (c) 011111 (d) 111110.
- (iii) A full adder can be made out of
(a) Two half adders
(b) Two half adders and a NOT gate
(c) Two half adders and a OR gate
(d) Two half adders and a AND gate.
- (iv) $(1111)_2$ in Grey code represents
(a) 9 (b) 15 (c) 10 (d) 16.
- (v) If $S=0, R=1$ in a SR flip flop
(a) $Q_{n+1} = \bar{Q}_n$ (b) $Q_{n+1} = Q_n$
(c) $Q_{n+1} = 0$ (d) $Q_{n+1} = 1$.
- (vi) The race around condition never occurs in Flip Flop
(a) J-K (b) T
(c) Master slave (d) None of these.

- (vii) A three variable Karnaugh map has
(a) 16 minterms (b) 8 minterms
(c) 24 minterms (d) 32 minterms.
- (viii) The hexadecimal equivalent of the decimal number 115 is
(a) 72 (b) 73 (c) 70 (d) None of these.
- (ix) 2's complement of binary number 0101 is
(a) 1011 (b) 1101 (c) 1110 (d) 1001.
- (x) A device which converts BCD to seven segment is called
(a) Encoder (b) Decoder
(c) Multiplexer (d) None of these.

Group - B


2. (a) Realise (i) $Y = A + B\bar{C}\bar{D}$ using NAND gates and
(ii) $Y = (A + C)(A + \bar{D})(A + B + \bar{C})$ using NOR gates only.
- (b) Apply DeMorgan's theorem to the given expression
$$\overline{AB(CD + EF)}$$
8 + 4 = 12
3. (a) Implement a 16-to-1 multiplexer using two 8-to-1 multiplexer.
12
- (b) Implement the logic function $F = \sum m(1,2,5,6,7,8,10,12,13,15)$
using 8 input data selector MUX.
6 + 6 = 12

Group - C

4. Design a combinational circuit that will take 3 bit binary number as input and produce its equivalent Grey code. Write the truth table and draw the complete circuit diagram.
12
5. (a) Design an asynchronous Modulo 8 down counter using J-K flip flops.
(b) Design a 3-bit even parity generator and the corresponding 4 bit even parity checker circuit.
8 + 4 = 12

Group - D

 6. (a) A flip flop has a 10 ns delay from the time its CLK input goes from 1 to 0 to the time its output is complemented. What is the maximum delay in a 10-bit binary ripple counter that uses these flip flops? What is the maximum frequency at which the counter can operate reliably?
- (b) How many flip-flops will be complemented in a 10-bit binary ripple counter to reach the next count after the following count: (i) 1001100111 (ii) 0011111111.
- (c) Draw the waveforms of a 10 flip flop ripple up counter.
- 4 + 4 + 4 = 12**
7. Design the clocked sequential circuit using JK flip flop, whose state diagram is given in the following figure.



12

Group - E

8. Construct a circuit using PROM type PLD that represents a function $Y=2X^2-X$, where X may vary from 0 to 7.
- 12**
9. (a) Design a two input NOR gate using CMOS logic. Draw the switching diagram for all the possible input combinations.
- (b) Draw and explain the general architecture of PLA structure.

6 + 6 = 12

Department & Section	Submission Link (for Backlog)
CSE	https://classroom.google.com/c/MjxxMzkxNTUzMTly?cjc=azj2z7w

