(c) h₁₁

B.TECH/ECE/3RD SEM/ECEN 2102/2021

CIRCUIT AND NETWORK THEORY (ECEN 2102)

Time Allotted : 3 hrs

Figures out of the right margin indicate full marks.

Candidates are required to answer Group A and <u>any 5 (five)</u> from Group B to E, taking <u>at least one</u> from each group.

Candidates are required to give answer in their own words as far as practicable.

Group – A (Multiple Choice Type Questions)

- 1. Choose the correct alternative for the following:
 - (i) The voltage can never be exactly in phase with the current in a circuit that contains (a) Only Capacitor (b) Only Resistor (c) Inductor & capacitor (d) Inductor, capacitor & resistor In a series RC circuit, if the output is measured across the resistor, then the (ii) circuit can be considered as a (a) Band Pass Filter (b) Band Reject Filter (d) High Pass Filter (c) Low Pass Filter If the Laplace transform of f(t) is F(s), then the Laplace transform of $f(t+\alpha)$ is (iii) (b) $e^{s\alpha} F(s)$ (a) $e^{-s\alpha} F(s)$ (c) $F(s-\alpha)$ (d) $F(s+\alpha)$ If three 9mH inductors are connected in parallel without mutual inductance, (iv) then the total inductance is (a) 3Mh (b) 9mH
 - (c) 18mH (d) 27mH
 - (v) Two port analysis is applicable for the network containing
 - (a) linear circuit element only
 - (b) non linear circuit element only
 - (c) both linear and non linear circuit elements
 - (d) both bilateral and non linear circuit elements.
 - (vi) A two-port network to be declared as symmetrical,
 - (a) $z_{11} = z_{22}$ (b) $y_{21} = y_{12}$ (c) $h_{11} = h_{22}$ (d) AD = BC

 $10 \times 1 = 10$

Full Marks: 70

- (vii) The initial rate of rise of current through a coil of inductance 10 H when suddenly connected to a D.C. supply of 200 V is
 (a) 50 A/s
 (b) 20 A/s
 (c) 0.05 A/s
 (d) 500 A/s
- (viii) Two perfectly coupled coils each of 1 H self inductance are connected in parallel so as to aid each other. The overall inductance in henry is
 (a) 2
 (b) 1
 (c) 0
 (d) 0.5
- (ix) The rank of fundamental cut-set matrix of a connected graph with n number of nodes is
 (a) n-1
 (b) n
 (c) 2n+1
 (d) n+1
- (x) A network has 5 nodes and 9 branches. The number of fundamental loops in the network is
 (a) 4 (b) 5 (c) 8 (d) 9

Group-B

- 2. (a) State the superposition theorem. [(CO1) (Remember/LOCQ)]
 - (b) Determine the current i_0 in the circuit of Fig:1 using superposition theorem.



Fig:1

[(CO2) (Apply/IOCQ)]

(c) In the circuit of Fig:2 find the reading of the voltmeter V_m . Interchange the position of the current source and the voltmeter, and again find the reading. Comment on your answers.



- 3. (a) Explain the Reciprocity theorem with a proper example. [(CO2) (Understand/LOCQ)]
 - (b) State the condition for maximum power transfer for a circuit having reactive elements. [(CO2) (Remember/LOCQ)]

(c) Find the equivalent inductance across the terminals a & b of the circuit in fig 3. [(CO1) (Analyse/IOCQ)]



(d) Evaluate the Thevenin's equivalent resistance R_{th}& voltage V_{th}for the circuit in the fig 4. [(CO2) (Evaluate/HOCQ)]



4 + 2 + 3 + 3 = 12

Group - C

- 4. (a) In a series RC network excited by a voltage source Vu(t), determine the time at which the voltage across the resistor and that across the capacitor are equal. Consider zero initial condition. [(CO3) (Analyze/IOCQ)]
 - (b) In the circuit of Fig:5, evaluate the voltage v(t) and the current $i_R(t)$ and $i_L(t)$ for t >0. The circulating current at t=0 in the RL loop is 1 A clockwise. [(CO3) (Evaluate/HOCQ)]



6 + 6 = 12

5. (a) The switch K in the network of Fig. 6 is closed at t = 0. Calculate the current i(t) for $t \ge 0$. [(CO3) (Analyze/IOCQ)]



(b) Determine the Laplace transform of the periodic function in Fig:7. [(CO3) (Apply/IOCQ)] $f(t) \neq f(t) \neq f(t)$



6 + 6 = 12

Group - D

- 6. (a) Define all the h-parameters for any two-port network. [(CO5) (Remember/LOCQ)]
 - (b) Derive the equivalent transmission line parameters of two cascaded two-port networks. [(CO5) (Apply/IOCQ)]
 - (c) Evaluate the Z parameters for the given network in fig 8. [(CO5) (Evaluate/HOCQ)] 1



4 + 4 + 4 = 12

7. (a) How many trees are possible for the graph of the network of Fig:9 ? Draw all the trees. [(CO4) (Understand/LOCQ, Create/HOCQ)]



(b) Obtain the incidence matrix of the graph of the network of Fig:10. Use it to obtain the node admittance matrix. Establish the KCL equation in matrix form and hence find the voltage at the node 2. [(CO4) (Analyze/IOCQ)]



(1+5)+6=12

Group - E

- 8. (a) What are the salient features of active filters? [(CO6) (Remember/LOCQ)]
 - (b) Draw the circuit diagram of first order low pass filter and find the transfer function of it. [(CO6) (Understand/LOCQ)]
 - (c) Design a second order band pass active filter that has a centre frequency of 1 KHz and a Band-width of 100 Hz. Take the centre frequency gain to be 2.
 [(CO6) (Create/HOCQ)]

3 + 3 + 6 = 12

9. (a) Write the input file of SPICE to determine the node voltages of the circuit in Fig 11. [(CO6) ((Apply/IOCQ)])]



(b) Design a 1st order active high pass filter with a dc gain of 10 and a corner frequency of 10KHz. [(CO6) (Create/HOCQ)]

6 + 6 = 12

Cognition Level	LOCQ	IOCQ	HOCQ
Percentage distribution	20%	48%	32%

Course Outcome (CO):

After the completion of the course students will be able to

- 1. Apply the previous knowledge gathered from Basic Electrical Engineering for understanding the basic concepts of this subject.
- 2. Solve problems in various electric circuits using Network Theorems.
- 3. Analyze complex circuits in Laplace domain.
- 4. Understand the application of Graph theory to solve various network behaviour.
- 5. Evaluate the output of various Two port network without going through the detailed configuration.
- 6. Design various types of filters using SPICE software.

*LOCQ: Lower Order Cognitive Question; IOCQ: Intermediate Order Cognitive Question; HOCQ: Higher Order Cognitive Question

Department & Section	Submission Link
ECE A	https://classroom.google.com/u/0/w/NDA0OTUzODA1ODk1/tc/NDY4Mjc5ODAxMzI3
ECE B	https://classroom.google.com/w/NDQyMjA3ODQzNjg1/tc/NDc3MzIyNzQ4OTQ4
ECE C	https://classroom.google.com/c/NDA1MTk5MTEwNDIx/a/NDc1MTUxMTIxMDQy/details