

**ANALOG & DIGITAL ELECTRONICS  
(ELEC 2102)**

**Time Allotted : 3 hrs**

**Full Marks : 70**

*Figures out of the right margin indicate full marks.*

*Candidates are required to answer Group A and  
any 5 (five) from Group B to E, taking at least one from each group.*

*Candidates are required to give answer in their own words as far as practicable.*

**Group - A  
(Multiple Choice Type Questions)**

1. Choose the correct alternative for the following: **10 × 1 = 10**
- (i) If a square wave is applied at the input of a differentiator, the output is  
(a) impulse waveform (b) square waveform  
(c) triangular waveform (d) sinusoidal waveform
- (ii) The output impedance of an operational amplifier should be  
(a) as low as possible (b) unity  
(c) as high as possible (d) infinite
- (iii) If the differential gain = 1000 and CMRR = 80dB, then the common mode gain of a differential amplifier is  
(a) 0.1 (b)  $10^8$  (c) 0.08 (d) 12.5
- (iv) A Schmitt trigger circuit generates  
(a) triangular waveform (b) sinusoidal waveform  
(c) square waveform (d) sawtooth waveform
- (v) The other name of voltage follower is  
(a) Inverting amplifier (b) Differential amplifier  
(c) Non-inverting amplifier (d) Unity gain amplifier
- (vi) Which of the following is a weighted code?  
(a) 2421 (b) Excess-3 (c) Gray (d) All of the above
- (vii) Which of the following is not a valid rule in Boolean algebra  
(a)  $A+1=1$  (b)  $A+0=0$  (c)  $A \cdot A = A$  (d)  $A \cdot 0 = 0$
- (viii) A 4-bit parallel adder can add  
(a) two 4-bit binary number (b) two 2-bit binary number  
(c) four bits at a time (d) four bits in sequence

- (ix) The minimum number of NAND gates required to construct an XOR gate is  
 (a) 3 (b) 4 (c) 5 (d) 8.
- (x) A feature that distinguishes the J-K flip-flop from the S-R flip flop is the  
 (a) toggle condition (b) preset input  
 (c) type of clock (d) clear input

**Group- B**

2. (a) Draw and explain the transfer characteristics of an inverting amplifier using an operational amplifier. [(CO1)(Remember/LOCQ)]
- (b) The transistor circuit shown in Fig. 1 uses a silicon transistor with  $V_{BE} = 0.7V$ ,  $I_C \approx I_E$  and a dc current gain of 100. Determine the value of  $V_o$ . [(CO1) (Analyze/LOCQ)]

 


Fig. 1

- (c) Design a circuit using one operational amplifier to obtain an output voltage  $V_{out} = V_1 - 3V_2$  where  $V_1$  and  $V_2$  are the input voltages. [(CO1)(Create/HOCQ)]  
 3 + 5 + 4 = 12

3. (a) Explain the working principle of a precision rectifier using an operational amplifier with the help of a neat circuit diagram and waveforms. [(CO2) (Remember/LOCQ)]
- (b) Model the linear differential equation using minimum number of operational amplifier:  $2 \frac{d^2y}{dt^2} + \frac{dy}{dt} + y = 1$ . [(CO2) (Apply/IOCQ)]
- (c) Determine the upper threshold voltage, lower threshold voltage and hysteresis voltage for the Schmitt trigger circuit shown in Fig. 2. Assume  $R_1 = R_2 = 10k\Omega$ ,  $V_{in}(p-p) = 20V$  sine wave,  $V_{sat} = \pm 12V$  and  $V_R = 5V$ . [(CO2) (Evaluate/HOCQ)]

 


Fig.2

3 + 5 + 4 = 12

**Group - C**

4. (a) Compare Hartley and Colpitts oscillator. [(CO3) (Remember/LOCQ)]  
(b) Derive the expression of oscillation frequency for the Wien bridge oscillator using an operational amplifier. [(CO3) (Apply/IOCQ)]  
(c) Justify the following statement : "RC phase shift oscillator using an operational amplifier cannot be realised with only two stages in the feedback circuit."  
[(CO3) (Evaluate/HOCQ)]  
**2 + 6 + 4 = 12**
5. (a) What is the nature of the trigger pulse applied in the circuit of a monostable multivibrator using an operational amplifier? [(CO3) (Understanding/LOCQ)]  
(b) Construct an astable multivibrator using a 555 timer having a duty cycle equal to 50%. [(CO3) (Apply/IOCQ)]  
(c) Design a triangular wave generator with frequency of oscillation = 2kHz and amplitude of the triangular wave  $V_o(p-p) = 7V$ . [(CO3) (Evaluate/HOCQ)]  
**2 + 6 + 4 = 12**

**Group - D**

6. (a) Define D Morgan's Theorem of boolean algebra. [(CO4) (Remember/LOCQ)]  
(b) Apply the knowledge of K map to simplify the following Boolean function and implement it using suitable logic gates:  
 $F(A,B,C,D) = \sum_m (0,1,2,8,10,11,14,15) + \sum_d (3,13)$ . [(CO4) (Apply/IOCQ)]  
(c) Realize EX-OR and EX-NOR gates using NAND gates only. [(CO4)(Create/HOCQ)]  
**3 + 5 + 4 = 12**
7. (a) Discuss briefly about 2 line to 4 line decoder. [(CO5) (Understand /LOCQ)]  
(b) Sketch and explain the functional diagram and write down the truth table of a 1:4 demultiplexer. [(CO5) (Apply/IOCQ)]  
(c) Design a single bit comparator, which can compare  $A=B$ ,  $A>B$  and  $A<B$ . [(CO5)(Create/IOCQ)]  
**4 + 5 + 3 = 12**

**Group - E**

8. (a) State the difference between asynchronous and synchronous counter. [(CO6) (Remember/LOCQ)]  
(b) Demonstrate how a JK flip flop can be used as a frequency divider circuit. [(CO6) (Apply/IOCQ)]  
(c) Design a SR flip flop using JK flip flop. [(CO6)(Create/HOCQ)]  
**4 + 5 + 3 = 12**
9. (a) Explain the working of a 4 bit asynchronous up counter with necessary diagrams. [(CO6) (Remember/LOCQ)]

- (b) Design a 4 bit SISO shift register and explain its working principle.  
 [(CO6)(Create/HOCQ)]

**6 + 6 = 12**

Cognition Level	LOCQ	IOCQ	HOCQ
Percentage distribution	28.13%	44.8%	27.08%

**Course Outcome (CO):**

After the completion of the course students will be able to

- Recall basic principles of diodes, transistors and OPAMPs.
- Understand basic principles of OPAMP based circuits for linear and nonlinear operations and analyze their implications.
- Acquire knowledge about different waveform generators, 555 timers, ADCs and DACs and their applications.
- Recall number systems and Boolean algebra.
- Understand Boolean algebra based realisation of logic gates and design of various arithmetic and combinational circuits.
- Design and analyze various sequential circuits like synchronous and asynchronous counters, shift registers using flip flops.

\*LOCQ: Lower Order Cognitive Question; IOCQ: Intermediate Order Cognitive Question; HOCQ: Higher Order Cognitive Question

Department & Section	Submission Link
EE	Joining Code: sywhhq3 Submission Link: <a href="https://classroom.google.com/c/NDA2NDE0NzI2MzEw/a/NDY0ODg0NTQwMzU5/details">https://classroom.google.com/c/NDA2NDE0NzI2MzEw/a/NDY0ODg0NTQwMzU5/details</a>