

**POWER ELECTRONICS
(ELEC 3104)**

Time Allotted : 3 hrs

Full Marks : 70

Figures out of the right margin indicate full marks.

Candidates are required to answer Group A and any 5 (five) from Group B to E, taking at least one from each group.

Candidates are required to give answer in their own words as far as practicable.

**Group – A
(Multiple Choice Type Questions)**

1. Choose the correct alternative for the following: **10 × 1 = 10**
- (i) Which of the following has the highest reverse recovery time?
(a) Schottky diode (b) Fast recovery diode
(c) GP diode (d) Normal diode.
- (ii) Rise time of SCR is the time taken by
(a) the anode current to rise from 10% to 90% of its final value
(b) the gate current to rise from 10% to 90% of its final value
(c) the anode current to rise from 10% to 50% of its final value
(d) the anode voltage to rise from 10% to 90% of its final value.
- (iii) Which power electronic device has the highest switching frequency?
(a) Power MOSFET (b) Power BJT
(c) SCR (d) IGBT.
- (iv) Power electronic device with poor turn off gain is
(a) GTO (b) Power MOSFET
(c) Power BJT (d) SCR.
- (v) In a single phase semi-converter, for continuous conduction, each SCR conducts for
(a) α (b) π
(c) $\pi + \alpha$ (d) $\pi - \alpha$.
- (vi) A single phase half wave controlled rectifier has $400 \sin 314t$ as the input voltage and R as the load. For a firing angle of 60° for the SCR, the average output voltage will be
(a) $400/\pi$ (b) $300/\pi$
(c) $240/\pi$ (d) $200/\pi$.

B.TECH/EE/5TH SEM/ELEC 3104/2020

- (vii) The input output voltage relationship for a boost chopper is
(a) $V_o = V_s$ (b) $V_o = \alpha V_s$ (c) $V_o = V_s / (1 - \alpha)$ (d) $V_o = \alpha V_s / (1 - \alpha)$.
- (viii) A single phase inverter with square wave output voltage will have its output waveform a fifth harmonic component equal to ____ percentage of fundamental
(a) 10% (b) 20% (c) 30% (d) 40%
- (ix) A single phase AC voltage controller feeds power to a resistance of 10Ω . The source voltage is 200V rms. For firing angle of 90° the rms value of Thyristor current in ampere is
(a) 20 A (b) 15 A (c) 10 A (d) 5 A.
- (x) The number of thyristors required in a three phase to three phase 3 pulse type cycloconverter is
(a) 6 (b) 12 (c) 18 (d) 36.

Group – B

2. (a) Draw and explain gate triggering circuit of SCR using UJT.
(b) Explain resonant pulse commutation of SCR with necessary waveforms.
(c) What are snubber circuits?
5 + 5 + 2 = 12
3. (a) Explain two transistor model of SCR with the help of a neat diagram. Hence derive an expression of anode current.
(b) The MOSFET cell embeds a parasitic BJT in its structure. Justify the statement.
(c) What is softness factor?
(4 + 4) + 3 + 1 = 12

Group – C

4. (a) Explain the operation of a full wave midpoint type controlled converter with RL load. Draw relevant waveforms.
(b) A single phase transformer with secondary voltage of 230V, 50Hz supplies a half wave rectifier circuit and delivers power to a load of 10Ω . For firing angle delay of 60° , calculate (i) Rectifier efficiency (ii) Form Factor (iii) Voltage ripple factor (iv) Transformer utilization factor and (v) PIV of thyristor.
5 + 7 = 12
5. (a) Define firing angle.
(b) An SCR is used to control the power of 1kW, 230V, 50Hz heater. Determine the heater power for firing angle of 45° .

- (c) Derive the average value and RMS value of output voltage for a three phase fully controlled bridge converter operating under continuous conduction mode.

2 + 4 + 6 = 12**Group – D**

6. (a) Explain the operation of a buck chopper with necessary equations. Also draw the inductor voltage and inductor current waveforms.
- (b) A boost regulator with an input voltage of 5V has an average output voltage of 15V and average load current of 0.5A. The switching frequency is 25kHz. If $L=150\mu\text{H}$ and $C=220\mu\text{F}$. Determine
- Duty cycle.
 - Ripple current of inductor.
 - Peak current of inductor.
 - Ripple voltage of filter capacitor.
 - Critical values of L and C.

6 + 6 = 12

7. (a) What are the uses of feedback diodes in an inverter?
- (b) A three phase bridge inverter delivers power to a resistive load from a 600V DC source. For a star connected load of 10Ω per phase determine for 180° mode,
- RMS value of load current. Also draw load current waveform.
 - RMS value of thyristor current. Also draw thyristor current waveform.
 - Load power.
- (c) Write short notes on current source inverters.

3 + (2 + 2 + 1) + 4 = 12**Group – E**

8. (a) Explain the operation of single phase half wave ac voltage controller for R load along with necessary waveforms.
- (b) Derive the average and rms values of output voltage for the above case.
- (c) Write any two typical application of AC voltage controller.
9. (a) Explain in detail the operation of a single phase to single phase step up bridge type cycloconverter.
- (b) Write short note on static circuit breakers.

5 + 5 + 2 = 12**6 + 6 = 12**

Department & Section	Submission Link
EE	https://classroom.google.com/c/MTIyMDQxNjg5Njkz/a/MjcxNjA2NTUzODk0/details