

## CIRCUIT THEORY (ELEC 2101)

Time Allotted : 3 hrs

Full Marks : 70


*Figures out of the right margin indicate full marks.*

*Candidates are required to answer Group A and  
any 5 (five) from Group B to E, taking at least one from each group.*

*Candidates are required to give answer in their own words as far as practicable.*

### Group – A (Multiple Choice Type Questions)

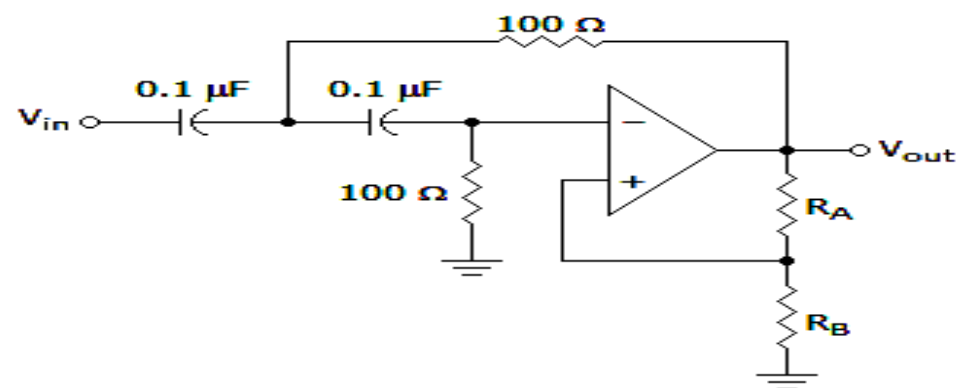1. Choose the correct alternative for the following: **10 × 1 = 10**
- (i) The critical frequency is the frequency at which the response drops from the passband by  
 (a) 20 dB                      (b) 3 dB                      (c) 6 dB                      (d) 40 dB
- (ii) Refer to the given figure. This circuit is known as a \_\_\_\_\_ filter, and the  $f_c$  is \_\_\_\_\_.  
 (a) high-pass, 1.59 kHz  
 (b) high-pass, 15.9 kHz  
 (c) low-pass, 15.9 kHz  
 (d) band-pass, 15.9 kHz
- (iii) For super node analysis technique we apply  
 (a) KVL only                      (b) KCL only  
 (c) both KVL and KCL                      (d) source transformation only.
- (iv) For perfect or ideal coupling, the value of the coefficient of coupling of two magnetically coupled coils is  
 (a) 1                      (b) 2                      (c) 0.1                      (d) 0.2.
- (v) Integration of ramp signal gives  
 (a) step signal                      (b) ramp signal                      (c) sinusoidal signal                      (d) parabolic signal.
- (vi) For  $F(s) = \frac{(s+2)}{s(s+1)}$ , the initial value of  $f(t)$  will be  
 (a) 0                      (b) 1                      (c) 2                      (d)  $\infty$ .
- (vii) Laplace transform of unitstep signal is  
 (a) 0                      (b) 1                      (c)  $1/s$                       (d)  $1/s^2$ .
- (viii) If a graph has  $n$  number of nodes and  $b$  number of branches then the number of fundamental cut-set of the graph is equal to  
 (a)  $b - n$                       (b)  $b + n + 1$                       (c)  $b - n + 1$                       (d)  $n - 1$ .



- (ix) The condition of symmetry for h-parameters is  
 (a)  $h_{11}=h_{22}$                       (b)  $h_{12}= -h_{21}$                       (c)  $h_{11} h_{22}- h_{12} h_{21} =1$                       (d)  $h_{12}= h_{21}$
- (x) Two 'two-port' networks are connected in series. The combination is to be represented as a single two -port network  
 (a) by adding individual Z parameter matrices  
 (b) by multiplying individual Z parameter matrices  
 (c) by subtracting individual Z parameter matrices  
 (d) by dividing individual Z parameter matrices.

**Group – B**

2. (a) Solve for the mesh currents  $i_1$  and  $i_2$  for the network given in Fig. 2(a).  
 [(CO1)(Apply/IOCQ)]

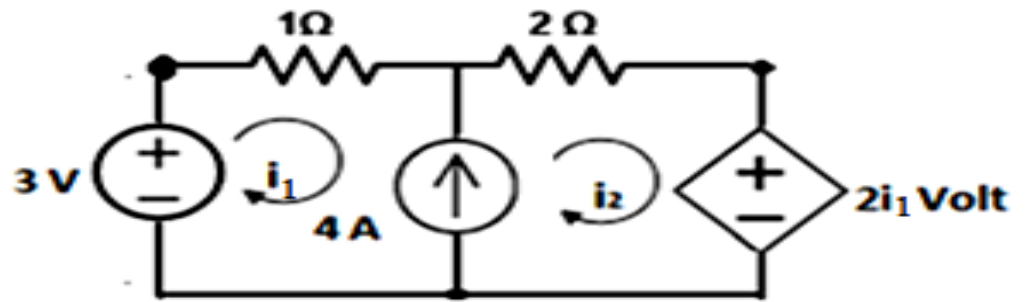


Fig. 2(a)

- (b) For the circuit of Fig. 2(b), solve for the value of current passing through load resistance  $R_L$  using Thevenin's theorem.  
 [(CO1)(Apply/IOCQ)]

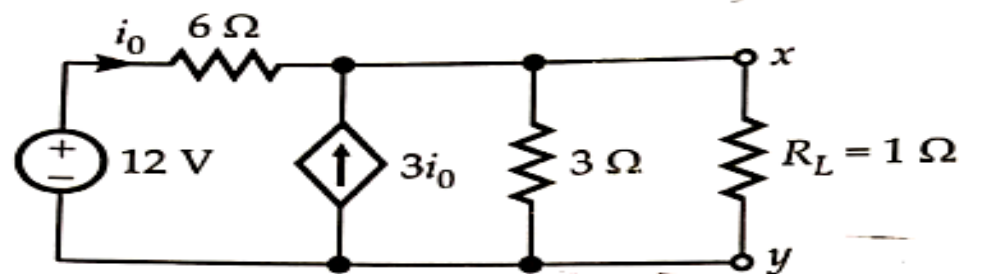


Fig. 2(b)

5 + 7 = 12

3. (a) Make use of superposition theorem to solve  $i$  and  $i_0$  for the network given in Fig.3(a).  
 [(CO1)(Apply/IOCQ)]

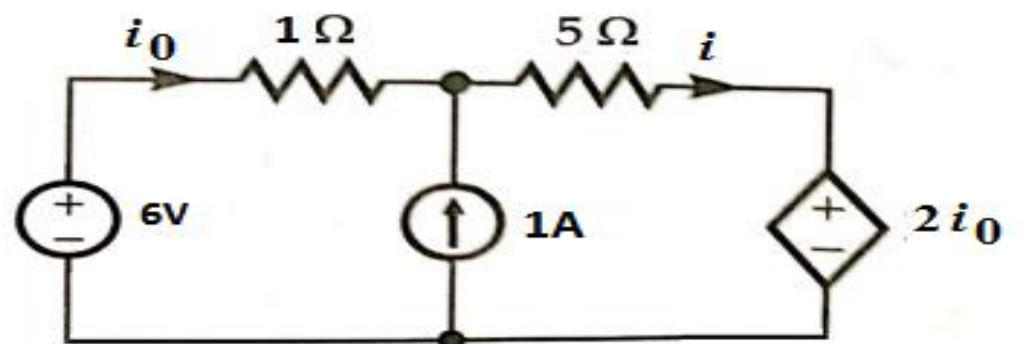


Fig. 3(a)

- (b) Construct the dotted equivalent circuit and determine the total inductance of the three series connected coupled coils as shown in Fig. 3(b). [(CO2)(Apply/IOCQ)]

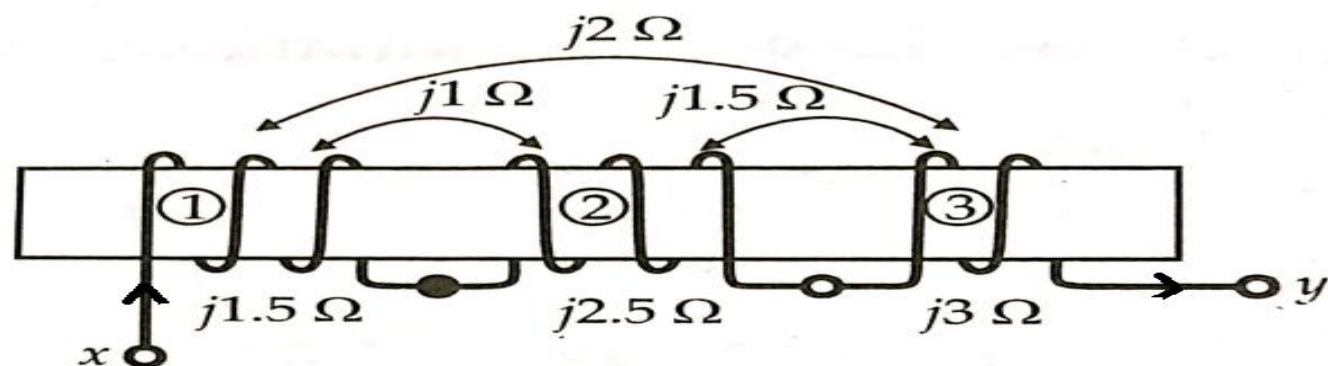


Fig. 3(b)

7 + 5 = 12

**Group – C**

4. (a) Define unit Step signal. [(CO3)(Remember/LOCQ)]

(b) Determine Laplace transform of the waveform shown in fig. 4(b).

[[CO3](Evaluate/HOCQ)]

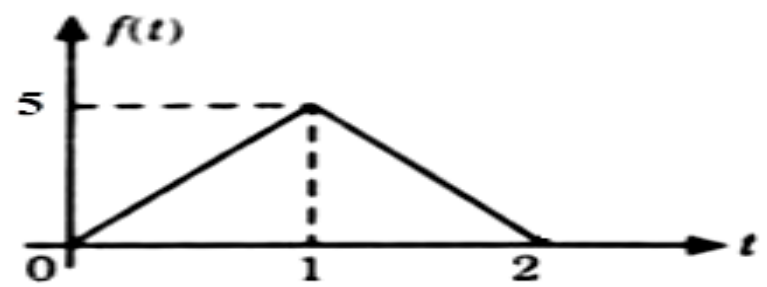


Fig. 4(b)

(c) In the circuit shown in Fig. 4(c), the switch 'K' is at position 1 for a long time. Develop the expression for the current through the inductor when the switch is moved from position 1 to 2 at  $t=0$ . [[CO3](Apply/IOCQ)]

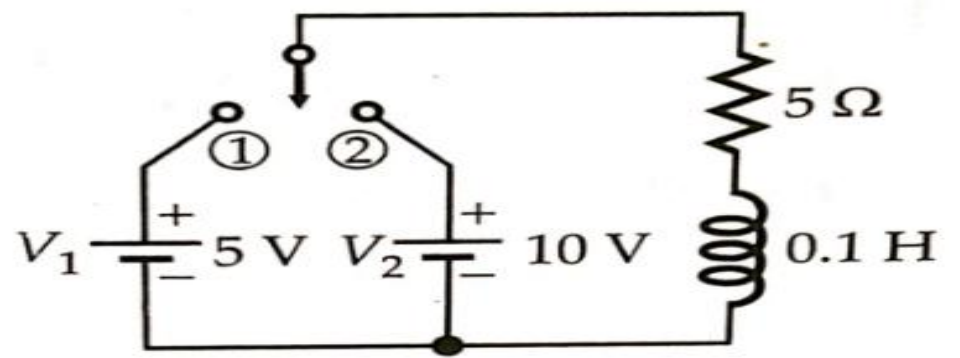


Fig. 4(c)

2 + 4 + 6 = 12

5. (a) Determine the signal  $x(t)$ , whose first derivative is as shown in fig.5(a). [[CO3](Evaluating/HOCQ)]

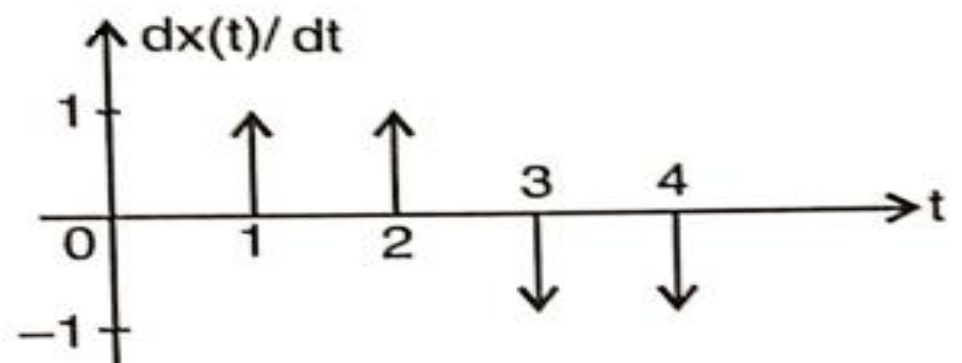


Fig. 5(a)

(b) In the series R-L-C circuit shown in fig. 5(b), there is no initial charge on the capacitor. If the switch 'S' is closed at  $t = 0$ , solve for the resulting current for  $t > 0$ . What will be the final current flowing through the circuit? Also state the nature of response.

[[CO3](Apply/IOCQ)]

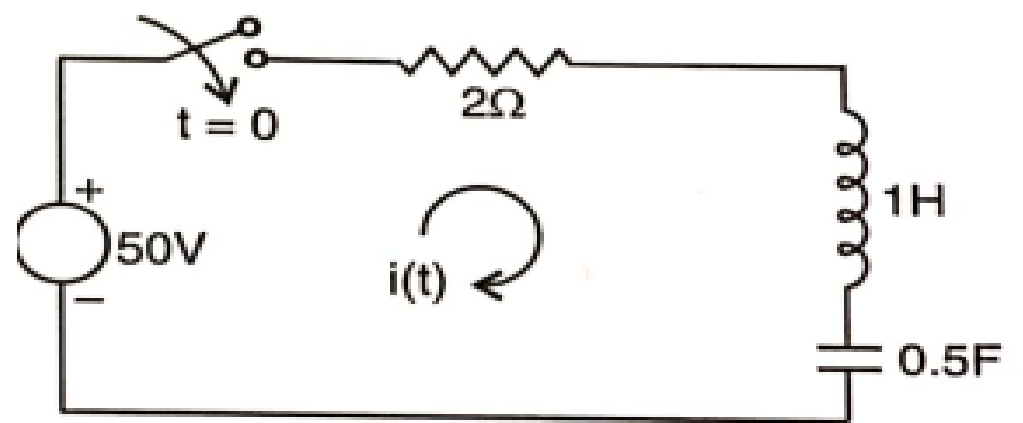


Fig. 5(b)

(c) Define unit Ramp signal. What is its Laplace transform? [[CO3](Remember/LOCQ)]

4 + 6 + 2 = 12

### Group - D

6. (a) What is co-tree of a graph ?

[[CO4](Remember/LOCQ)]

(b) (i) Develop Complete Incidence matrix of the directed graph shown in Fig. 6(b(i)).

(ii) Assume the sub-graph shown in Fig. 6(b(ii)) as a tree and develop fundamental Cut-set matrix and Tie-set matrix.

[[CO4](Apply/IOCQ)]

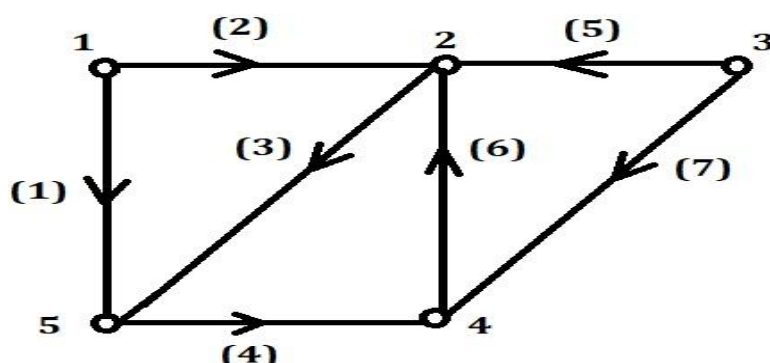


Fig. 6 (b(i))

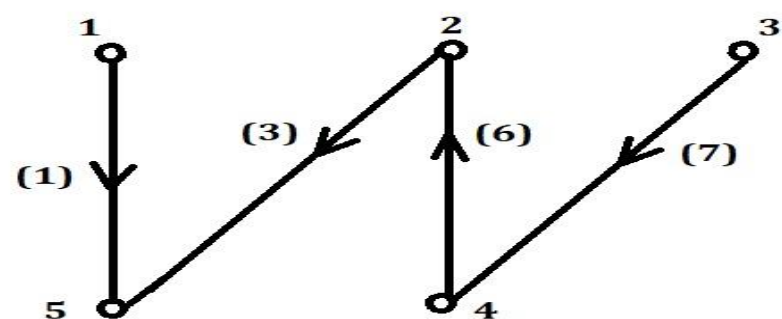


Fig. 6 (b(ii))

- (c) Prove that, in graph theory, the relation between branch voltage and node voltage is  $V_b = A^T V_n$ , where  $A$  = Reduced Incidence Matrix,  $V_b$  = branch voltage matrix and  $V_n$  = node voltage matrix. [(CO4) (Evaluate/HOCQ)]  
**1 + (3 + 3 + 3) + 2 = 12**

7. (a) Define Y-parameters and transmission parameters. Express Y-parameters in terms of hybrid parameters. [(CO5)(Remember/LOCQ)]

- (b) For transmission parameter, develop the condition of reciprocity. [(CO5)(Create/HOCQ)]

- (c) Analyse the circuit shown in Fig.7(c) and find ABCD parameters. [(CO5)( Analyze/IOCQ)]

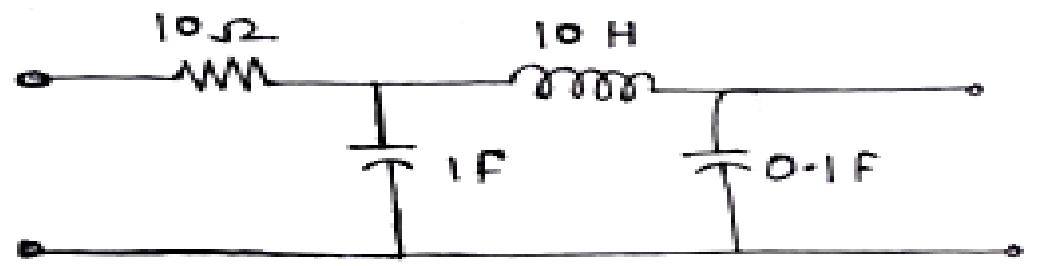


Fig. 7(c)

**(1 + 1 + 2) + 2 + 6 = 12**

**Group - E**

8. (a) Define Filter. [(CO6)(Remember/LOCQ)]  
 (b) Show the derivation of the transfer function of a 2<sup>nd</sup> order active Sallen & Key Low Pass Filter. [(CO6)(Understand/LOCQ)]

- (c) Design a 2<sup>nd</sup> order Butterworth low pass filter of cut-off frequency 2 kHz. [(CO6)(Create/HOCQ)]  
**2 + 5 + 5 = 12**

9. (a) Draw the circuit diagram of a Narrow Band Pass Filter. [(CO5)(Remember/LOCQ)]  
 (b) Derive the transfer function of a Notch Filter along with its Gain vs Frequency response. [(CO5)(Analyse/IOCQ)]

- (c) Determine the poles of lowpass Butterworth filter for N=4, where N is the order of the filter along with their location of poles on s-plane. [(CO6)(Evaluate/HOCQ)]  
**3 + 6 + 3 = 12**

| Cognition Level         | LOCQ  | IOCQ  | HOCQ  |
|-------------------------|-------|-------|-------|
| Percentage distribution | 19.79 | 59.38 | 20.83 |

**Course Outcome (CO):**

After the completion of the course students will be able to

C01: apply network theorems to solve electrical circuits having both dependent and independent sources.

C02: analyze magnetically coupled circuits.

C03: apply Laplace transform technique in solving transient problems of electrical circuits.

C04: apply the concept of graph theory to electrical circuits.

C05: obtain the equivalent representation of electrical circuits using two- port parameter representation.

C06: analyze and synthesize filters.

\*LOCQ: Lower Order Cognitive Question; IOCQ: Intermediate Order Cognitive Question; HOCQ: Higher Order Cognitive Question.