

DIGITAL VLSI DESIGN
(ECEN 3201)

Time Allotted : 3 hrs

Full Marks : 70

Figures out of the right margin indicate full marks.

*Candidates are required to answer Group A and
any 5 (five) from Group B to E, taking at least one from each group.*

Candidates are required to give answer in their own words as far as practicable.

Group – A
(Multiple Choice Type Questions)

1. Choose the correct alternative for the following: **10 × 1 = 10**
- (i) The time taken by a square wave to go from 10% to 90% of its final voltage level is called
 - (a) fan-out
 - (b) rise time
 - (c) fall time
 - (d) propagation delay.
 - (ii) The fan-out of a digital circuit means
 - (a) amount of cooling required by the gate
 - (b) the number of other gates that can be connected to one of the gate's input
 - (c) the physical distance between the output pins of the circuit
 - (d) the number of other gates that can be connected to one of the gate's output.
 - (iii) Which of the following is true for a NMOS operating in the linear region?
 - (a) $V_{DS} < (V_{GS} - V_t)$
 - (b) $V_{DS} > (V_{GS} - V_t)$
 - (c) $V_{GS} < V_t$
 - (d) $V_{GS} = 0$.
 - (iv) Dynamic power dissipation of a CMOS depends on
 - (a) Channel width of the MOSFETS
 - (b) MOSFET characteristics
 - (c) Switching frequency
 - (d) Input voltage.
 - (v) The body or the substrate terminal of a PMOS device is tied to the
 - (a) negative most supply of the system
 - (b) positive most supply of the system
 - (c) generally remains as a dangling terminal
 - (d) none of the above.
 - (vi) In a CMOS inverter, the direct current path exists from supply voltage (VDD) to ground when both _____ and _____ are turned ON.
 - (a) NPN and NMOS
 - (b) PMOS and NMOS
 - (c) PNP and NPN
 - (d) none of these


- (vii) What is the logical effort of “R” number of inputs in a NOR logic gate?
(a) $2R/3$ (b) $(R+1)/3$
(c) $(2R+1)/3$ (d) None of these.
- (viii) Most Manual Effort is needed in which of the below VLSI Methodology?
(a) FPGA (b) Gate Array
(c) Std Cell Based Semi Custom (d) Full Custom.
- (ix) Which of the following is considered as an electrical fault?
(a) Excessive steady state current (b) Delay fault
(c) Bridging fault (d) Logical Stuck-at-0 or Stuck-at-1.
- (x) The equivalent (W/L) of two nMOS transistors with (W_1/L) and (W_2/L) connected in parallel is
(a) $(W_1/L) + (W_2/L)$ (b) $(W_1/L) \times (W_2/L)$
(c) $[1/(W_1/L) + 1/(W_2/L)]^{-1}$ (d) $(W_1/L) / (W_2/L)$.

Group - B

2. (a) Draw the Voltage Transfer Characteristics of a CMOS inverter for (i) $k_n=k_p$ (ii) $k_n>k_p$, (iii) $k_n<k_p$. Draw the 3VTCs in the same axes frame to clearly indicate the variations. Give proper justification for the graphs. *[[CO1](Understand/LOCQ)]*
(b) Consider the Boolean form $f=\Sigma m(0,1,2,5,6)$. Realize this with the help of PLA logic design. *[[CO1](Apply/IOCQ)]*
(4 + 3) + 5 = 12
3. (a) A 64-bit off-chip bus operating at 1 V and 100 MHz clock rate is driving 25 pF/bit capacitance. Each bit is estimated to have a toggling probability of 0.25 at each clock cycle. Calculate the dynamic power dissipation in operating the bus. *[[CO2](Evaluate/HOCQ)]*
(b) Design a CMOS gate for the logic function $f(a,b,c)=\Sigma m(0,1,3,5,6)$. Mention the widths of NMOS and PMOS for the above design so that the current driving capability remains same as that of the basic CMOS inverter. *[[CO1](Apply/IOCQ)]*
(c) Briefly discuss about VLSI design flow with the help of a Y-Chart. *[[CO2](Remember/LOCQ)]*
4 + 6 + 2 = 12

Group - C

 4. (a) Draw the stick diagram of the function $Y = \overline{AD + E + BC}$ using Euler Path Algorithm. *[[CO4](Apply/IOCQ)]*
(b) Explain the Write-1 operation of a 3-Transistor DRAM cell with the help of the circuit diagram. *[[CO4](Understand/LOCQ)]*
6 + 6 = 12
5. (a) Considering the given CMOS topology, implement the Boolean expression available at the OUT1 node.



[[C03](Apply/IOCQ)]

- (b) Draw the circuit and timing diagram of a D-latch using Transmission Gate. Briefly state set-up time and hold-time. [[C03](Understand/LOCQ)]

- (c) Realise a 2-input X-NOR gate using transmission gate. [[C03](Apply/IOCQ)]

3 + 6 + 3 = 12

Group - D

6. (a) Implement the Data Flow Graph of the following function,
 $x = a * b$;
 $y = a - c$;
 $z = x + d$;
 $x = x * c$;

Using Data Flow Graph, realize the data path logic. [[C05](Remember/LOCQ)]

- (b) Write the Verilog code for the structural modelling of a 4:1 multiplexer using three 2:1 multiplexer modules. Draw the complete block diagram of the model.

[[C05](Apply/IOCQ)]

6 + 6 = 12

7. (a) Write the verilog code for designing a sequence counter which will count the following sequence: 0,1,2,5,6,8,10,3,0..... [[C05](Apply/IOCQ)]

- (b) Discuss the significance of Modularity in VLSI Design Methodology. [[C02](Understand/LOCQ)]


- (c) Write a Verilog code for designing a positive edge triggered Mod-16 counter. [[C05](Apply/IOCQ)]

5 + 3 + 4 = 12

Group - E

8. (a) Explain the different kinds of physical faults that can occur on a CMOS chip and relate them to typical circuit failures. [[CO6](Analyze/IOCQ)]
 (b) Explain the different types of Bridging Faults with the help of suitable diagrams. [[CO6](Understand/LOCQ)]
6 + 6 = 12

9. (a) Find the test vector for the following circuit which has got a Stuck-at-0 fault at 'g'

 

[[CO6](Evaluate/HOCQ)]

- (b) Discuss the 3 types of Delay Faults. Briefly state the nature of these faults. [[CO6](Analyze/IOCQ)]
7 + 5 = 12

<i>Cognition Level</i>	<i>LOCQ</i>	<i>IOCQ</i>	<i>HOCQ</i>
<i>Percentage distribution</i>	<i>37.5</i>	<i>51.04</i>	<i>11.46</i>

Course Outcome (CO):

After the completion of the course students will be able to

- Students will be able to relate to different MOS structures and functions in order to apply the knowledge in building CMOS circuits
- Students will learn VLSI Design Cycle, Style and Methodology.
- Students will be able to determine logic and performance of CMOS combinational and Sequential Circuit including Memory Array Design.
- Students will be able to construct Physical Layout Design and Stick Diagram of Digital Gates.
- Students will be able to make use of various synthesis flow and HDL modeling in ASIC Semi Custom Design.
- Students will be able to interpret Si Testing and Debug related algorithms and Fault Modeling.

**LOCQ: Lower Order Cognitive Question; IOCQ: Intermediate Order Cognitive Question; HOCQ: Higher Order Cognitive Question.*