

CIRCUIT THEORY
(ELEC 2101)

Time Allotted : 2½ hrs

Full Marks : 60

Figures out of the right margin indicate full marks.

Candidates are required to answer Group A and any 4 (four) from Group B to E, taking one from each group.

Candidates are required to give answer in their own words as far as practicable.


Group - A

1. Answer any twelve:

12 × 1 = 12



Choose the correct alternative for the following

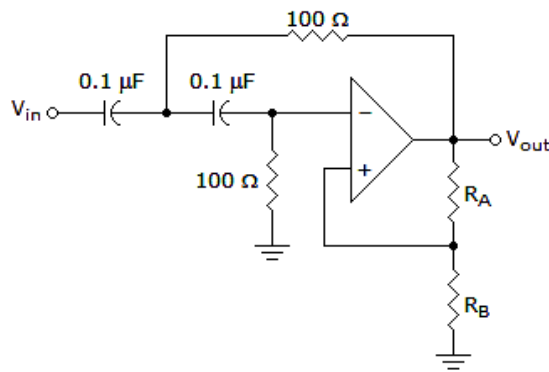- (i) As order of a filter increases cut-off rate of a low pass filter circuit
 (a) increases (b) decreases
 (c) remains same (d) none of these.
- (ii) Refer to the given figure. This circuit is known as a _____ filter, and the f_c is _____.




- (a) high-pass, 1.59 kHz
 (b) high-pass, 15.9 kHz
 (c) low-pass, 15.9 kHz
 (d) band-pass, 15.9 kHz

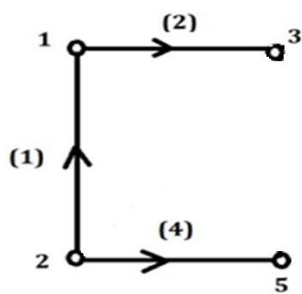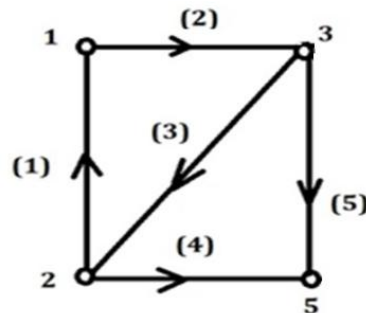
- (iii) In a certain low-pass filter, $f_c = 4.5$ kHz. Its pass band is
 (a) 0 Hz (b) 0 Hz to 4.5 kHz (c) 9 kHz (d) 4.5 kHz.
- (iv) Which of the given options is not a tree of the following graph?




(a)

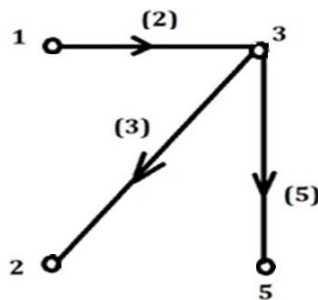

(b)

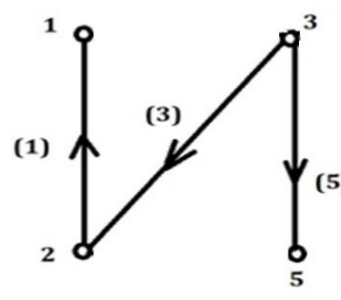

(c)

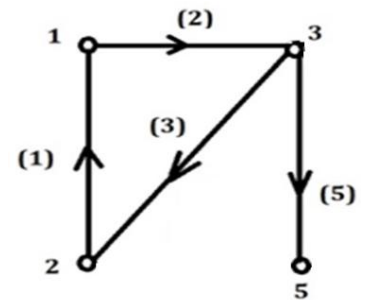

(d)

- (v) Short circuit reverse transfer admittance is
 (a) Y_{11} (b) Y_{12} (c) Y_{21} (d) Y_{22} .
- (vi) If the number of branches in a network is B, the number of nodes is N then the number of mesh equations will be
 (a) $B - N - 1$ (b) $B - N + 1$ (c) $N - 1$ (d) $N + 1$.
- (vii) Two coils having self-inductance 2 H and 8 H and with mutual inductance of 2 H between them, the coupling coefficient is
 (a) 0.5 (b) 20 (c) 2 (d) 8.
- (viii) The Laplace transform of a function is $F(s) = \frac{s+2}{s(s+1)}$. Its final value is
 (a) 1 (b) 2 (c) 0 (d) -1
- (ix) A 10 Ω resistor, a 1 H inductor and 1 F capacitor are connected in parallel. The combination is driven by a unit step current. Under steady state condition, the source current flow through
 (a) Resistor only (b) Inductor only (c) Capacitor only (d) all of the three elements.

- (x) For super mesh analysis we apply
 (a) KVL only (b) KCL only (c) both KVL and KCL (d) Lenz's Law

Fill in the blanks with the correct word

- (xi) The number of poles in a 2nd order low pass filter is _____.
- (xii) The cut-off rate in a 2nd order filter is _____.
- (xiii) The relation between branch current matrix and loop current matrix is _____.
- (xiv) Derivative of a unit ramp function will lead to _____ function.
- (xv) A 10 Ω resistor, a 2 H inductor and 3 F capacitor are connected in series. The combination is driven by a unit step voltage. The current flowing through the circuit under steady state condition is _____ A.

Group - B

2. (a) Calculate v_0 and i_0 for the circuit of Fig.1.

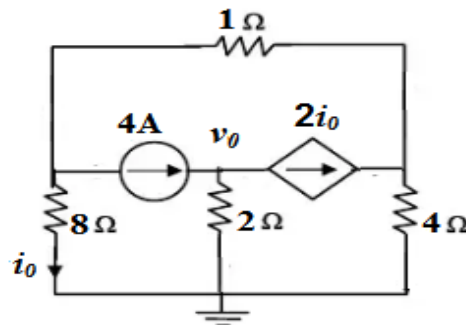


Fig. 1

[[CO1](Apply/IOCQ)]

- (b) Calculate current through 5Ω resistance of Fig.2 using Thevenin's theorem.

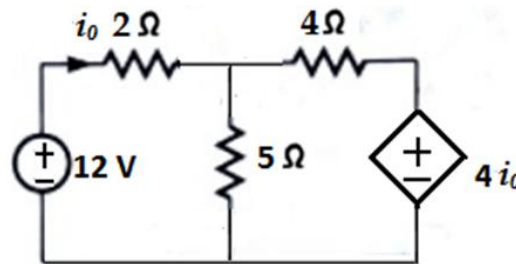


Fig. 2

[[CO1] (Apply/IOCQ)]
6 + 6 = 12

3. (a) Select the value of R_L to be connected across AB in Fig.3 for maximum power transfer. Also calculate the amount of maximum power absorbed by the R_L .

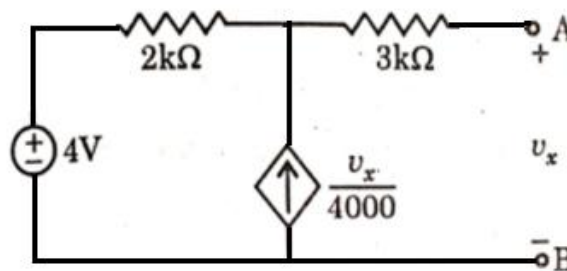


Fig. 3

[[CO1](Apply/IOCQ)]

- (b) Evaluate the value of I_1 and I_2 in the magnetically coupled circuit of Fig. 4.

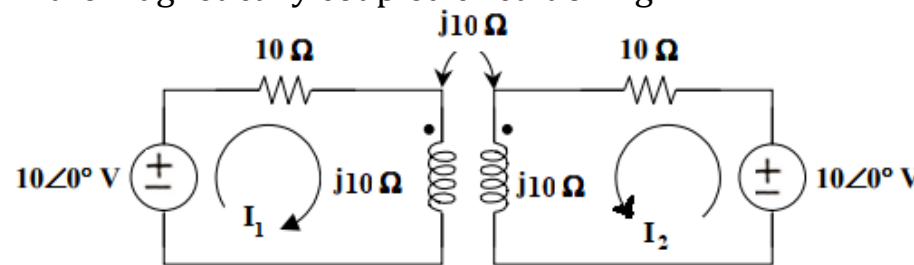


Fig. 4

[[CO2](Evaluate/HOCQ)]
6 + 6 = 12

Group - C

4. (a) Find the Laplace transform for the saw-tooth waveform shown in Fig. 5.

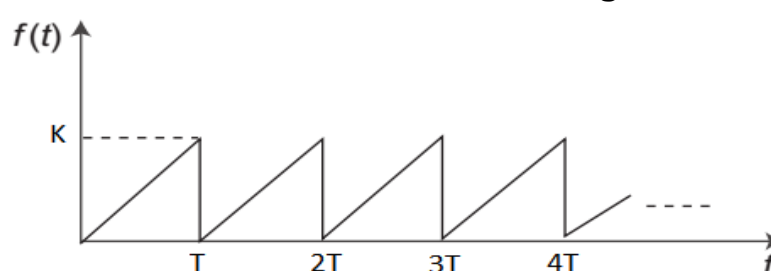


Fig. 5

[[CO3](Understand/LOCQ)]

- (b) In the network of Fig.6, switch 'S' is closed at $t = 0$. Determine the expression of current given by the source for $t > 0$. Assume zero initial condition.

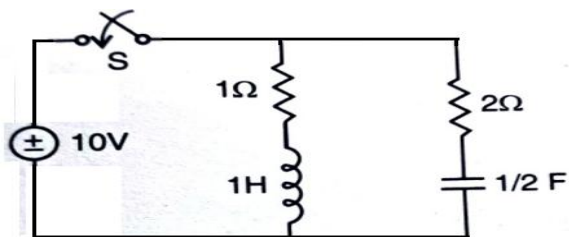


Fig. 6

[[CO4](Apply/IOCQ)]
6 + 6 = 12

5. (a) Determine the Laplace transform for the staircase waveform as shown in Fig. 7.

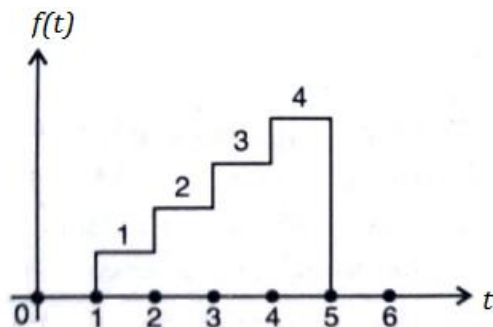


Fig.7

[[CO3](Evaluate/HOCQ)]

- (b) In the circuit shown in Fig. 8, the switch 'S' is closed at $t=0$. Develop the expression of voltage across the capacitor for $t > 0$ assuming zero initial voltage across the capacitor.

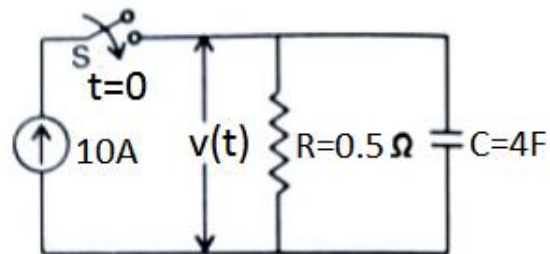


Fig. 8

[[CO3](Apply/IOCQ)]
6 + 6 = 12

Group - D

6. (a) Develop Complete Incidence matrix of the directed graph shown in Fig. 9.
(b) Assume the sub-graph shown in Fig. 10 as a tree and develop fundamental Cut-set matrix and Tie-set matrix.

[[CO4] (Create/HOCQ)]

[[CO4] (Apply/IOCQ)]

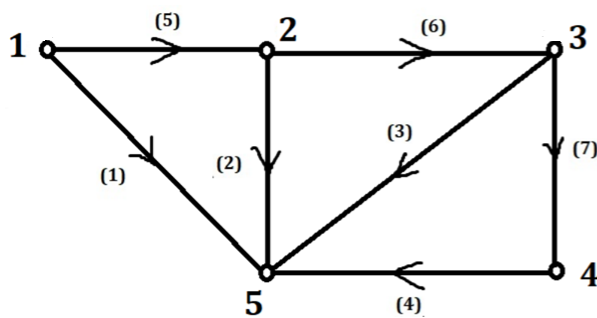


Fig. 9

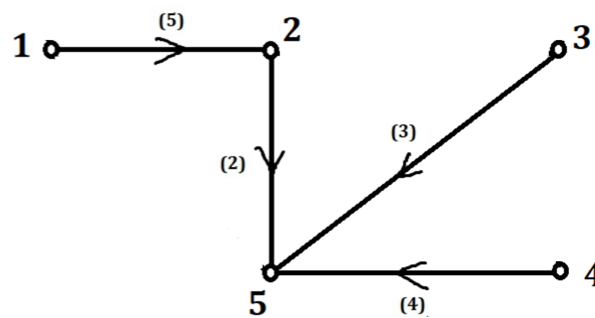


Fig. 10

4 + (4 + 4) = 12

7. (a) Define Z-parameters and transmission (ABCD) parameters. Express Z- Parameters in terms of hybrid parameters.
(b) For Y parameter, develop the condition of Symmetry.
(c) Analyse the circuit shown in Fig. 11 and find its Z-parameters and Y-parameters.

[[CO5](Remember/LOCQ)]

[[CO5](Create/HOCQ)]

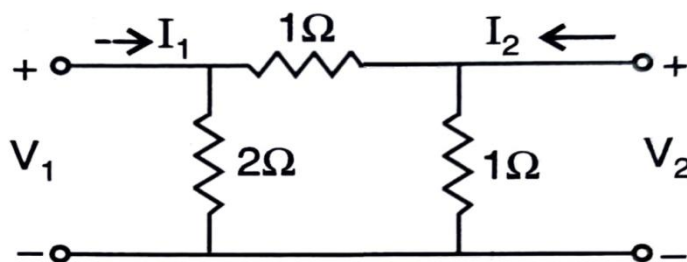


Fig. 11

[[CO5](Analyze/IOCQ)]
(1 + 1 + 2) + 2 + 6 = 12

Group - E

8. (a) Sketch the circuit diagram of 2nd order high pass active filter.
(b) Show that the cut-off rate of a first order active high pass filter is +20dB/Decade.

[[CO6](Apply/IOCQ)]

[[CO6](Understand/LOCQ)]

- (c) Sketch the Gain (dB) vs. Frequency plot of First order active high pass filter.
- (d) What is the nature of poles for different damping conditions?
- (e) Show that the maximum gain reduces by 3dB at the cut-off frequency.

[[CO6](Apply/IOCQ)]
 [[CO6](Remember/LOCQ)]
 [[CO6](Apply/IOCQ)]
2 + 4 + 1 + 2 + 3 = 12

9. (a) Sketch the circuit diagram of a 2nd order active low pass Sallen-Key filter.
 (b) Design a Notch Filter with a centre frequency of 60 Hz.
 (c) Sketch the Gain vs Frequency plot of Notch Filter.
 (d) Design a 2nd order Sallen-Key Filter whose cut-off frequency is 2 kHz with Quality Factor = 1.
 (e) What is the nature of poles for different damping conditions?
 (f) Define cut-off or Roll-off Rate of a filter.

[[CO6](Apply/IOCQ)]
 [[CO6](Create/HOCQ)]
 [[CO6](Apply/IOCQ)]
 [[CO6](Create/HOCQ)]
 [[CO6](Remember/LOCQ)]
 [[CO6](Remember/LOCQ)]
2 + 3 + 1 + 3 + 2 + 1 = 12

Cognition Level	LOCQ	IOCQ	HOCQ
Percentage distribution	19.79	55.21	25

Course Outcome (CO):

After the completion of the course students will be able to

- apply network theorems to solve electrical circuits having both dependent and independent sources.
- analyze magnetically coupled circuits.
- apply Laplace transform technique in solving transient problems of electrical circuits.
- apply the concept of graph theory to electrical circuits.
- obtain the equivalent representation of electrical circuits using two- port parameter representation.
- analyze and synthesize filters.

**LOCQ: Lower Order Cognitive Question; IOCQ: Intermediate Order Cognitive Question; HOCQ: Higher Order Cognitive Question.*