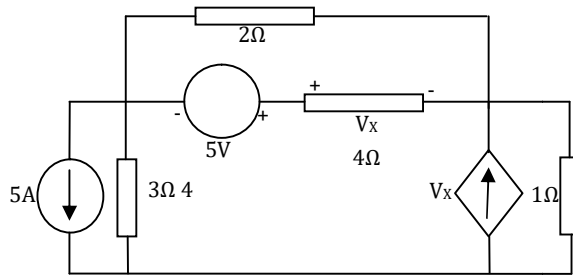


- (vii) A function that repeats itself after fixed intervals is said to be
 - (a) a phasor
 - (b) harmonic
 - (c) periodic
 - (d) reactive.
- (viii) The imaginary part of impedance is called
 - (a) resistance
 - (b) admittance
 - (c) reactance
 - (d) conductance.
- (ix) The coefficient of coupling for two coils having $L_1 = 2H$, $L_2 = 8H$ and $M = 3H$ is
 - (a) 0.1875
 - (b) 0.75
 - (c) 1.333
 - (d) 5.333.
- (x) A transformer is used in stepping down or stepping up
 - (a) dc voltage
 - (b) ac voltage
 - (c) both dc and ac voltage
 - (d) direct current.

Group - B

2. (a)



Find the voltage across 4Ω using Nodal analysis.

- (b) In a transformer the primary coil have a leakage flux (ϕ_{11}) of 0.5 mWb and they have mutual flux (ϕ_{12}) of 0.3 mWb. If the number of turns are 100 and 500 respectively in primary and secondary and if current flow through primary is 1 amp, then find (i) K, the coefficient of coupling, (ii) the inductances L_1 and L_2 , and (iii) M, the mutual inductance.


6 + 6 = 12

- 3. (a) Establish a relation between Q-factor, bandwidth and resonant frequency of a series RLC circuit.
- (b) A series RLC circuit has $R = 4 \Omega$, $L = 6 \text{ mH}$ and $C = 8 \mu\text{F}$. Calculate (i) the Q-factor, (ii) the bandwidth, (iii) the resonant frequency, (iv) the half-power frequencies and also (v) find the frequency at which V_c (voltage across capacitor) is maximum.

4 + 8 = 12

Group - C

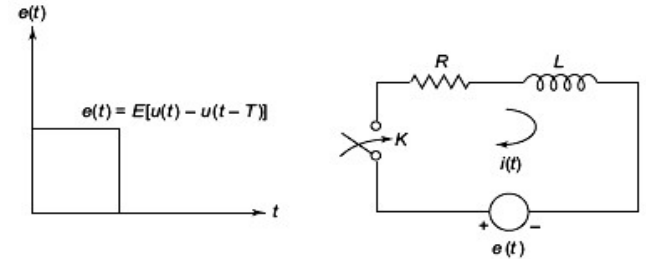
- 4. (a) Obtain the pulse response for the series RL circuit, shown i below. Find transient as well as steady state current in the circ




- (b) A transfer function is given by $F(s) = \frac{s^2+10s+}{(s+1)(s+2)(s+3)}$; find $F(t)$ steady state value of $F(t)$.
- (c) Find the final value of current using final value theorem in a RL circuit following step response.

6 + 3 + 3 = 12

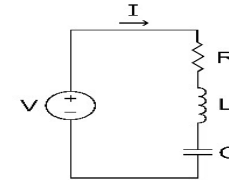- 5. (a) Derive the step response of the series RLC circuit as shown i below. Then define the following terms from the derived equ (i) neper frequency, (ii) angular resonance frequency (iii) damping factor.



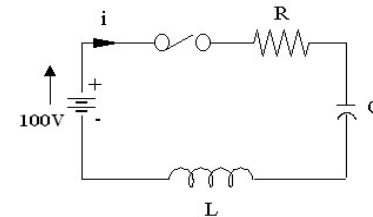
- (b) The circuit shown consists of R, L and C in series with a constant source when the switch is closed at $t = 0$. Find (transient and steady state current, (ii) damping factor and a resonance frequency.



(2 + 3 + 3) + (2 + 2) = 12

Group - D

6. (a)

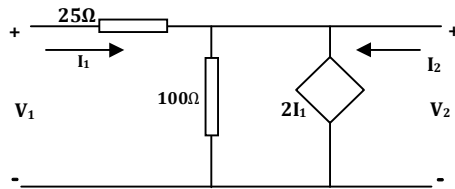

Find the short circuit parameters of the circuit shown in the above figure. Does it satisfy the condition of symmetry or reciprocity?

(b) Find the symmetry condition for the h parameters.


(6 + 2) + 4 = 12

7. (a) Reduced incident matrix of a graph is given by

Nodes ↓	Branches →					
		0	1	0	-1	-1
	0	-1	1	0	1	0
	1	0	-1	0	0	0

Draw the oriented graph. Select a tree and find the cut set matrix.

(b)

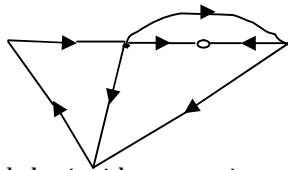

Find the incident matrix and tie-set matrix of the graph as shown in figure above.

(2 + 4) + (3 + 3) = 12

Group - E

8. (a) Design an active band pass filter with bandwidth 10kHz and pass band gain 3.

(b) Explain with proper diagram how all pass filter can be used as delay unit.

6 + 6 = 12

9. An impedance is given by

$$Z(S) = \frac{8(S^2 + 1)(S^2 + 3)}{S(S^2 + 2)(S^2 + 4)}$$

Realize the network in FOSTER form I and CAUER form II.

(6 + 6) = 12

**CIRCUIT THEORY & NETWORKS
(AEIE 2102)**

Time Allotted : 3 hrs

Full Marks : 70

Figures out of the right margin indicate full marks.

Candidates are required to answer Group A and any 5 (five) from Group B to E, taking at least one from each group.

Candidates are required to give answer in their own words as far as practicable.


Group - A

(Multiple Choice Type Questions)

1. Choose the correct alternative for the following:

10 × 1 = 10

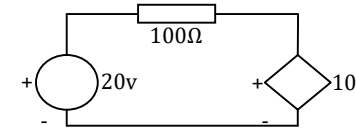(i) Find the value of i form the circuit diagram



- (a) 0.18A (b) -0.81^a (c) 1.81A (d) 18.18A.

(ii) To design an active band pass filter, the LPF and HPF are connected in

- (a) parallel (b) series
(c) both series and parallel (d) none of these.

(iii) If A = 8, B = 5, C = 11, D = 7, then it will satisfy:

- (a) symmetry condition (b) reciprocity condition
(c) dual condition (d) none of these.

(iv) If $Z_L = R_L + jX_L$ and $Z = R + jX$, where X_L is fixed then the condition of maximum power transfer will be

- (a) $R_L^2 = R^2 + X^2$ (b) $R_L^2 = R^2 + (X + X_L)^2$
(c) $R_L^2 = R^2 + X_L^2$ (d) none of these.

(v) The condition of reciprocity for h parameter is

- (a) $h_{11} = h_{22}$ (b) $h_{12} = h_{21}$
(c) $h_{12} = -h_{21}$ (d) none of these.

(vi) In a series RLC circuit, setting $R = 0$ will produce

- (a) an overdamped response (b) a critically damped response
(c) an underdamped response (d) an undamped response.