 



- (v) What has been considered as the industry standard of linear ICs?
 (a) 555 timer (b) 741 op amp
 (c) LM 340 (d) LM 317.
- (vi) What is the typical input bias current of a 741 operational amplifier?
 (a) 70 nA (b) 80 nA
 (c) 90 nA (d) 100 nA.
- (vii) What is the most common method used for the growth of single crystals for IC fabrication?
 (a) Epitaxial growth (b) Czochralsky pulling technique
 (c) Film deposition (d) Photolithography.
- (viii) In the figure below, assuming that the resistance R is very large, what is the best approximation for V_{out} ?



- (a) $-V_{tp}$ (b) V_{DD} (c) $V_{DD}-V_{tp}$ (d) 0.

- (ix) Basic building block in digital circuit is/are
 (a) NAND (b) NOR
 (c) AND (d) both (a) and (b).

(x) The MOSFET below

 

is labeled with the different types of silicon. The device is best described as

- (a) an NFET in an N-well (b) an NFET in a P-well
 (c) a PFET in an N-well (d) a PFET in a P-well.

Group - B

- 2. (a) Briefly describe the steps associated in IC processing, fabrication and packaging.
- (b) Write short note on MOS based active resistor circuit.

8 + 4 = 12

- 3. (a) Derive an expression for propagation delay in a CMOS inverter with a capacitor load. Comment on the relation between propagation delay and capacitance of the load.
- (b) For a $0.25\mu\text{m}$ process characterized by $V_{DD}=2.5\text{V}$, $V_{tn} = -V_{tp}$, $k'_n=3.5k'_p=115 \mu\text{A}/\text{V}^2$, find t_{PLH} , t_{PHL} and t_p for an inverter with $(W/L)_n=1.5$, $(W/L)_p=3$ and $C=10\text{fF}$.

6 +

Group - C

- 4. (a) Derive the expression of dominant pole frequency (f_p), unity gain bandwidth (f_c) and slew rate (SR) of 741 op-amp. How are they related to each other?
- (b) What is the use of 741 op-amp output short circuit protection circuit?

(6 + 2) + 4

- 5. (a) Perform small signal analysis on a MOS cascode amplifier with a load circuit and derive an expression for voltage gain and output resistance.
- (b) It is required to connect a transducer having an open-circuit voltage of 1V and source resistance of $1\text{M}\Omega$ to a load of $1\text{k}\Omega$ resistance. Calculate the load voltage if the connection is done (i) directly and (ii) through a unity gain voltage follower.

6 + 4


Group - D

- 6. (a) Briefly explain the operation of charge-redistribution Analog-to-Digital Converter.
- (b) Consider a 5-bit charge redistribution A/D converter with V_{REF} . What is the full scale voltage of this converter?
- 7. (a) Obtain the expressions for common mode gain and CMRR of an active loaded MOS differential pair.
- (b) An active loaded MOS differential amplifier has the following specifications: $(W/L)_n=100$, $(W/L)_p=200$, $\mu_n C_{ox}=2\mu_p C_{ox}=0.2\text{mA}/\text{V}^2$, $V_{An}=|V_{Ap}|$, $I_0=0.8\text{mA}$, $R_{ss}=25\text{k}\Omega$. Calculate G_m , R_o , A_d , $|A_{cm}|$, and CMRR.

7 + 5

Group - E

 8. (a) Briefly explain the CMOS realization of AOI gate and explain with truth table.
 (b) Implement $F = \overline{AB + \overline{AB}}$ using the AOI logic gate. **8 + 4 = 12**
9. (a) Perform small signal analysis on the given NMOS amplifier circuit, shown in the following figure. Find an expression for output impedance and voltage gain.



- (b) Compare a bipolar current mirror with MOS mirror. What is bias compensation in a bipolar mirror and how does it improve current transfer ratio. **4 + 8 = 12**

**MICRO ELECTRONIC DEVICES AND CIRCUITS
(AEIE 5101)**

Time Allotted : 3 hrs


Full Marks :

Figures out of the right margin indicate full marks.

Candidates are required to answer Group A and any 5 (five) from Group B to E, taking at least one from each group. Candidates are required to give answer in their own words as far as practicable.

**Group - A
(Multiple Choice Type Questions)**

 1. Choose the correct alternative for the following: **10 × 1 :**
- (i) The threshold voltage of an n-channel MOSFET can be increase
 (a) increasing the channel dopant concentration
 (b) reducing the channel dopant concentration
 (c) reducing gate oxide thickness
 (d) reducing the channel length.
- (ii) In a CMOS inverter the upper MOSFET is
 (a) active load (b) passive load
 (c) complementary load (d) none of the above
- (iii) The extremely high input impedance of a MOSFET is primarily due to
 (a) absence of its channel
 (b) negative gate-source voltage
 (c) depletion of current carriers
 (d) extremely small leakage current of its gate capacitor.
- (iv)



- If $R_1 = 10 \text{ k}\Omega$, and $R_2 = 30 \text{ k}\Omega$, the input impedance of the circuit
 (a) $10 \text{ k}\Omega$ (b) $40 \text{ k}\Omega$
 (c) infinity (d) none of the above