

2016

**BASIC ELECTRONICS ENGINEERING**

**(ECEN 1001)**

**Time Allotted : 3 hrs**

**Full Marks : 70**

**Figures out of the right margin indicate full marks.**

**Candidates are required to answer Group A and any 5 (five) from Group B to E, taking at least one from each group.**

**Candidates are required to give answer in their own words as far as practicable.**

**GROUP - A**

**(Multiple Choice Type Questions)**

**1. Choose the correct alternative for the following:**

**[10 x 1=10]**

i) Relation between  $\alpha$  and  $\beta$  of BJT is

a)  $\alpha = \frac{(\beta+1)}{\beta}$     b)  $\beta = \frac{\alpha}{(1-\alpha)}$     c)  $\beta = \frac{\alpha}{(1+\alpha)}$     d)  $\alpha = \frac{\beta}{1-\beta}$

ii) The built-in-potential of a silicon diode is about

a) 2.4V    b) 3V    c) 3.1V    d) 0.7V

iii) The maximum efficiency of a half-wave rectifier is

a) 40.6%    b) 56.6%    c) 81.2%    d) 50%

iv) On increasing temperature the Fermi level moves

a) in n-type semiconductor towards the centre of the band gap

b) in p-type semiconductor towards the centre of the band gap

c) in both n and p type semiconductor towards the centre of the band gap

d) for n-type semiconductor towards conduction band and for p-type semiconductor towards valence band

- v) The leakage current across a p-n junction is due to
- a) minority carriers
  - b) majority carriers
  - c) junction capacitance
  - d) none of these
- vi) In a transistor, signal is transferred from a \_\_\_\_\_ resistance to \_\_\_\_\_ resistance circuit
- a) high, low
  - b) low, high
  - c) high, high
  - d) low, low
- vii) Operating point represents
- a) values of  $V_{CE}$  and  $I_C$  when ac signal is applied
  - b) values of  $I_B$  and  $V_{BE}$
  - c) the magnitude of the external signal
  - d) values of  $V_{CE}$  and  $I_C$  before the application of ac signal
- viii) An inverting op-amp has  $R_1 = 1K\Omega$  and  $R_f = 100K\Omega$ ; the input impedance is
- a)  $1K\Omega$
  - b)  $100K\Omega$
  - c)  $101K\Omega$
  - d) infinite
- ix) In an oscillator
- a) negative feedback is used
  - b) positive feedback is used
  - c) ac input signal is applied
  - d) amplification occurs
- x) The effective channel length of a MOSFET in saturation, decreases with increase in
- a) gate voltage
  - b) drain voltage
  - c) source voltage
  - d) body voltage

**GROUP - B**

- 2 a) For an unbiased p-n junction, sketch the variation of the space charge, electric field, electrostatic potential and electron energy as a function of distance across the junction.

- b) 'Zener breakdown voltage has a negative temperature co-efficient whereas avalanche break-down voltage has a positive temperature co-efficient'. Explain
- c) "The dynamic resistance of an ideal Zener diode is zero but the dc resistance is not so". Explain the reason.
- d) A silicon diode has a reverse saturation current of 0.1 nA at room temperature. Find its current when it is biased in the forward direction by 0.55V.

**4+2+3+3=12**

- 3 a) Giving relevant defining equations, explain the phenomenon of drift and diffusion associated with carrier movement in semiconductors.
- b) State mass-action law. Explain its meaning.
- c) Calculate the thermal-equilibrium electron and hole concentrations in a germanium sample for a given doping density. Consider a germanium sample at  $T = 300\text{K}$  in which  $N_d = 5 \times 10^{13} \text{ cm}^{-3}$  and  $N_a = 0$ . Assume that  $n_i = 2.4 \times 10^{13} \text{ cm}^{-3}$ .

**5+3+4=12**

**GROUP - C**

- 4 a) Name the three possible transistor connections. Explain the operation of transistor as an amplifier.
- b) Define  $\beta$ . Show that  $\beta = \frac{\alpha}{(1-\alpha)}$ .
- c) A transistor has  $I_B = 105 \mu\text{A}$  and  $I_C = 2.05 \text{ mA}$ . Find the following:  
i)  $\beta$  of transistor      ii)  $\alpha$  of transistor      iii) emitter current  $I_E$ .

**(1+4)+(1+3)+3=12**

- 5 a) What do you mean by the quiescent point of a transistor amplifier?
- b) What is load line of a BJT? Explain its significance.

- c) A CE mode amplifier is biased by a potential divider circuit. Here  $R_1 = 60\text{k}\Omega$ ;  $R_2 = 10\text{k}\Omega$ ,  $\beta = 60$ . Find the value of the stability factor when  $R_E = 1\text{k}\Omega$  and  $3\text{k}\Omega$ .

**2+4+6=12**

**GROUP - D**

- 6 a) When is channel of a JFET said to be pinched off? Define the pinch-off voltage. Give the relationship between the pinch-off voltage, the saturation voltage and the gate source voltage. What is pinch-off current?
- b) BJT is characterized by current gain but FET is characterized by trans-conductance gain-- Explain.

**(2+2+3+1)+4=12**

- 7 a) Why is the field-effect transistor called a unipolar transistor? Draw schematically the structure of an n-channel MOSFET and explain the terms source, drain, gate and substrate. What is the significance of the terms field-effect?
- b) What is the major physical difference between an enhancement-type and a depletion-type MOSFET?
- c) Draw the typical volt-ampere drain characteristics curve of a p-channel enhancement mode MOSFET?

**(1+4+2)+3+2=12**

**GROUP - E**

8. a) Explain with the help of a block diagram the working principle of a feedback amplifier. Find out an expression for the voltage gain with feedback.
- b) Write down the condition of oscillation.
- c) A feedback amplifier is designed with closed loop gain of 100. The maximum allowable variation in closed loop gain is 1% whereas that in open-loop gain is 10%. Determine the open loop voltage gain and the feedback factor for the amplifier.

**(3+2)+3+4=12**

- 9 a) Define the following parameters in respect of OP AMP:  
i) CMRR            ii) Slew Rate            iii) Offset voltage
- b) In an OP AMP, when the voltage applied to the inverting input terminal is  $v_1 = 50\mu V$  and that applied to the non-inverting input terminal is  $v_2 = -50\mu V$ , what is the output voltage, if the voltage gain for the difference signal is  $A_d$ ? If the Common Mode Rejection Ratio is 1000, calculate the percentage difference of the output voltage obtained with  $v_1 = 500\mu V$  and  $v_2 = 400\mu V$ .

**(2+2+2)+(4+2)=12**

---