

ANALOG ELECTRONICS
(AEI2101)

Time Allotted : 2½ hrs

Full Marks : 60

Figures out of the right margin indicate full marks.

*Candidates are required to answer Group A and
any 4 (four) from Group B to E, taking one from each group.*

Candidates are required to give answer in their own words as far as practicable.

Group – A

1. Answer any twelve:

12 × 1 = 12

Choose the correct alternative for the following

- (i) BJT can be made to operate as an amplifier by operating it in the
 - (a) active region
 - (b) active and cut-off region
 - (c) active and saturation region
 - (d) cut-off and saturation region
- (ii) An ideal operational amplifier has
 - (a) zero output impedance
 - (b) infinite input impedance
 - (c) infinite bandwidth
 - (d) all of the above
- (iii) Op-amp with negative feedback having
 - (a) high gain and less band width
 - (b) less gain and high band width
 - (c) high gain and high band width
 - (d) none of the above
- (iv) A Schmitt trigger is a/an
 - (a) comparator without hysteresis
 - (b) amplifier with hysteresis
 - (c) comparator with hysteresis
 - (d) amplifier without hysteresis
- (v) Advantage of an instrumentation amplifier is
 - (a) low input impedance
 - (b) very high CMRR
 - (c) high output impedance
 - (d) very low CMRR.
- (vi) Recommended frequency range of Colpitts oscillator is
 - (a) 2Hz to 3MHz
 - (b) 1KHz to 10MHz
 - (c) 0.5 KHz to 40 MHz
 - (d) 20 KHz to 30 MHz
- (vii) Wien-Bridge Oscillators generate frequencies ranging between
 - (a) 2Hz to 2MHz
 - (b) 1KHz to 10MHz
 - (c) 20Hz to 20 KHz
 - (d) 20 KHz to 20 MHz
- (viii) In a monostable multivibrator, how many stable states are present?
 - (a) Three
 - (b) Two
 - (c) One
 - (d) None.

- (ix) What is the typical output waveform of an Astable Multivibrator?
 (a) Sine wave (b) Sawtooth wave
 (c) Square wave (d) Triangular wave.
- (x) What is the primary function of a Voltage Controlled Oscillator (VCO)?
 (a) Generate constant frequency (b) Vary frequency based on input voltage
 (c) Amplify an input signal (d) Generate a constant voltage.

Fill in the blanks with the correct word

- (xi) CMRR of an ideal op-amp is _____.
- (xii) The Barkhausen criterion is associated with _____ feedback.
- (xiii) The output of a particular Op-amp increases 8V in 12 μ s. The slew rate is _____.
- (xiv) IC _____ is commonly used to implement a Phase-Locked Loop (PLL).
- (xv) A Wien bridge Oscillator is used for generating _____.

Group - B

2. (a) What are the reasons for shifting the operating point of a transistor in an amplifier Circuit? [[C01](Remember/LOCQ)]
- (b) How to achieve a stable operating point of BJT against temperature variation? Explain. [[C01](Understand/LOCQ)]
- (c) What is buffer amplifier? Explain one application of buffer amplifier. [[C02](Understand/LOCQ)]
- 4 + 4 + 4 = 12**
3. (a) Design a differential amplifier using BJT and find the output voltage in dual input balanced output mode. Identify the inverting and non-inverting input terminal. [[C01](Understand/LOCQ)]
- (b) Describe the characteristics of an ideal operational amplifier. How do these characteristics differ from those of a practical operational amplifier? [[C02](Remember/LOCQ)]
- (6 + 2) + 4 = 12**

Group - C

4. (a) Design and explain the operation of an instrumentation amplifier. How does it differ from a standard difference amplifier? [[C03](Understand/LOCQ)]
- (b) Design and explain the working principle of a Schmitt trigger circuit using an operational amplifier. Explain the concept of hysteresis and describe how it can be used to eliminate noise. [[C03](Understand/LOCQ)]
- (4 + 1) + (4 + 3) = 12**
5. (a) In a non-inverting positive feedback amplifier, if $R_i = 10K$, $R_f = 56K$, $V_{in} = 1V$ p-p sine wave, and the op-amp is type 741 with $V_{CC} = +15V$ and $V_{EE} = -15V$. Determine the hysteresis voltage. [[C03](Apply/IOCQ)]

- (b) What are the disadvantages of a theoretical active integrator circuit? Design a practical active integrator circuit to solve the above problem. Also find the range of frequency for which proper integration will take place. *[[C03](Understand/LOCQ)]*
4 + (2 + 2 + 4) = 12

Group - D

6. (a) Design a low-pass, active filter with cut-off frequency and pass gain as 1KHz and 10 respectively. *[[C06](Analyse/IOCQ)]*
 (b) Explain the operation of Wien-Bridge oscillator with circuit diagram. *[[C04](Understand/LOCQ)]*
6 + 6 = 12
7. (a) How does an oscillator differ from an amplifier? What are the conditions required to be satisfied for an oscillator circuit? *[[C04](Understand/LOCQ)]*
 (b) Determine the oscillation frequency of Wien bridge oscillator with neat circuit diagram. *[[C04](Remember/LOCQ)]*
(3 + 3) + 6 = 12

Group - E

8. (a) Explain the operation of a monostable multivibrator using operational amplifier with circuit diagram. *[[C05](Understand/LOCQ)]*
 (b) How does a 555 timer IC work? Explain with a proper circuit diagram. *[[C05](Understand/LOCQ)]*
6 + 6 = 12
9. Design and explain the operation of a circuit to obtain rectangular pulse as output with duty ratio greater than 50% using IC555 timer. *[[C05](Apply/IOCQ)]*
(4 + 8) = 12

Cognition Level	LOCQ	IOCQ	HOCQ
Percentage distribution	77.08	22.92	0

