

B.TECH/EE/3RD SEM/ELEC 2101/2016
ANALOG & DIGITAL ELECTRONIC CIRCUITS
(ELEC 2101)

Time Allotted : 3 hrs

Full Marks : 70

Figures out of the right margin indicate full marks.

Candidates are required to answer Group A and any 5 (five) from Group B to E, taking at least one from each group.

Candidates are required to give answer in their own words as far as practicable.

Group - A
(Multiple Choice Type Questions)

1. Choose the correct alternative for the following: **10 × 1 = 10**
 - (i) The other name of voltage follower is
 - (a) inverting amplifier
 - (b) differential amplifier
 - (c) non-inverting amplifier
 - (d) unity gain amplifier.
 - (ii) An integrator is mostly preferred to a differentiator because of
 - (a) more stability
 - (b) less noise
 - (c) less voltage drift
 - (d) all of the above.
 - (iii) The gain (A_v) of inverting Op-amp in a phase shift oscillator is
 - (a) $A_v \geq -30$
 - (b) $A_v \geq -29$
 - (c) $A_v \geq -31$
 - (d) $A_v \geq 1$.
 - (iv) The comparator using Op-amp with input sine waveform produces
 - (a) cosine waveform
 - (b) sine waveform
 - (c) triangular waveform
 - (d) square waveform.
 - (v) The reason for an Op-amp to drive any number of devices connected to its output is
 - (a) zero output resistance
 - (b) infinite output resistance
 - (c) infinite input resistance
 - (d) none of these.
 - (vi) The binary code of $(21.125)_{10}$ is
 - (a) 10101.001
 - (b) 10111.011
 - (c) 11000.001
 - (d) 10111.101.
 - (vii) Determine the values of A, B, C, and D such that the sum of the term $A + B^c + C^c + D$ is equal to zero.
 - (a) A=1, B=1, C=1, D=1
 - (b) A=1, B=0, C=1, D=0
 - (c) A=0, B=1, C=1, D=0
 - (d) A=0, B=0, C=0, D=0.


- (viii) NAND gate is called a universal gate because they
 - (a) have lower fabrication area
 - (b) can be used to make any gate
 - (c) consumes least electronic power
 - (d) none of these.
- (ix) Which gate can be used to add two bits?
 - (a) Ex-OR
 - (b) Ex-NOR
 - (c) NAND
 - (d) NOR.
- (x) The hexadecimal equivalent of 1100101000110101_2 is
 - (a) 121035
 - (b) CA35
 - (c) 53AC
 - (d) 530121.

Group - B

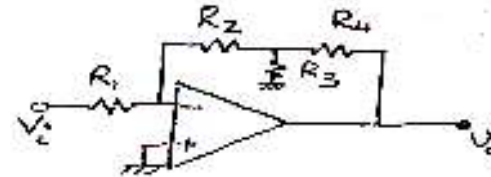2. (a) Explain the function and purpose of the constant current source in the circuit of a differential amplifier using BJT.
- (b) Realise the following linear differential equation using Op-amp:

$$\frac{d^2y}{dt^2} + 4 \frac{dy}{dt} + y = 5$$
- (c) A differential amplifier has two inputs: $V_1 = 10\text{mV}$ connected to pin 3 and $V_2 = 9\text{mV}$ connected to pin 2 of IC 741 Op-amp. It has a differential mode gain of 60dB and CMRR = 80dB. Determine the output voltage and the percentage error in output voltage.

3 + 5 + 4 = 12
3. (a) Draw the circuit diagram of integrator using Op-amp. Deduce the expression for output voltage. Mention the problems in the circuit and how do we modify the circuit to overcome them?
- (b) Determine the voltage gain of the following amplifier:



- (c) A non-inverting amplifier using Op-amp has input resistance $1\text{k}\Omega$ and feedback resistance $10\text{k}\Omega$. Determine the closed loop gain, input resistance with feedback, output resistance with feedback, total output offset voltage with feedback. Given $A = 2,00,000$, $R_i = 2\text{M}\Omega$, $R_o = 75\Omega$, $V_{CC} = 12\text{V}$, $-V_{EE} = -12\text{V}$.

4 + 4 + 4 = 12

Group – C

4. (a) Show how the trigger and threshold pins of IC 555 timer works?
 (b) Explain with the help of a neat circuit diagram the principle of operation of an astable multivibrator using Op-amp. Sketch the output voltage and the capacitor voltage waveforms. Derive the expression of time period.

$$2 + 10 = 12$$

5. (a) Using schematics briefly describe the working principle of a phase – shift oscillator. Derive the expression of oscillation frequency and gain required for sustained oscillation.
 (b) Using 7805C voltage regulator design a current source that will deliver 0.5A current to 100Ω, 10W load.

$$10 + 2 = 12$$

Group – D

6. (a) Subtract using 10's complement for the following : (25 - 5), (32 - 19).
 (b) Subtract using 1's complement: $(10010_2 - 01001_2)$, $(1101_2 - 1010_2)$.
 (c) What are the special characteristics of Gray code? Why is it used in K-map reduction technique?
 (d) Realise AND gate function using NOR gates only.
 (e) Convert the following binary to Gray code: 1001_2 , 10010_2 .

$$2 + 2 + 3 + 3 + 2 = 12$$

7. (a) $f(A,B,C,D) = \sum m(1,2,6,7,8,10,12,13,15)$
 Find out the minimal SOP form and POS form of the function.
 (b) Draw the functional diagram of a 4X1 multiplexer.
 (c) Realise the function $f(A,B,C) = \sum m(0,2,3,5,7)$ using 2X1 multiplexer.
 (d) Design a 4-line to 2-line priority encoder. Include an output E to indicate that atleast one input is 1.

$$(2 + 2) + 2 + 3 + 3 = 12$$

Group – E

8. (a) Tabulate the next- state of JK flip flop for different input conditions.
 (b) Find out the characteristic equation for JK flip flop.

- (c) How do you realise T flip flop using JK flip flop.
 (d) Realise a 3-bit synchronous binary counter using flip flop and show the logic diagram.
 (e) Why do we prefer synchronous counter to asynchronous counter?

$$2 + 2 + 2 + 5 + 1 = 12$$

9. (a) Draw the circuit diagram for R-2R ladder DAC. Explain its principle of operation.
 (b) Write short notes on the following:
 EPROM, ECL

$$5 + (3 + 4) = 12$$