
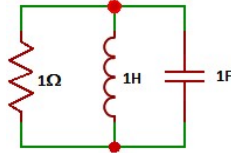


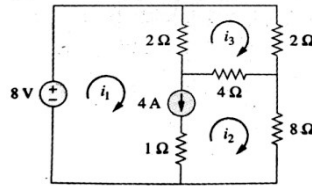- (vii) A two port network to be reciprocal,
 (a) $z_{11} = z_{22}$ (b) $y_{21} = y_{12}$
 (c) $h_{21} = -h_{12}$ (d) $AD - BC = 0$.
- (viii) A network has 7 nodes and 5 fundamental loops. The number of branches in the network is
 (a) 13 (b) 12 (c) 11 (d) 10.
- (ix) For the given parallel RLC circuit the response will be
 (a) over damped (b) under damped
 (c) critically damped (d) none of these.
- (x) The inverse Laplace transform of $(s+2)/(s+2)^2+1$ is:
 (a) $e^{-t}\cos 2t$ (b) $e^{-t}\sin 2t$ (c) $e^{-t}\cos t$ (d) $e^{-2t}\sin 2t$.




Group - B

2. (a) Use mesh analysis to determine i_1 , i_2 , & i_3 in the given circuit.




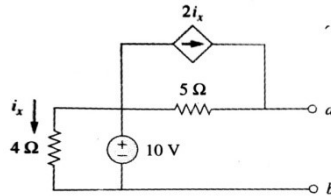- (b) Using Norton's theorem to find R_N & I_N of the circuit in the following figure.




6 + 6 = 12

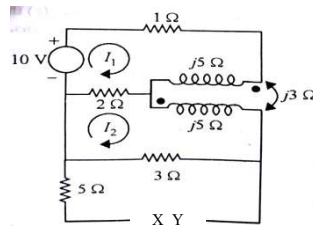3. (a) Find the open circuit voltage across the terminals A & B of the following circuit.



- (b) Design a second order band pass filter with a centre frequency of 1kHz and band-width of 100Hz. Take the centre frequency gain to be 2.
 6 + 6 = 12

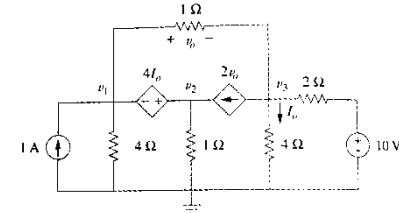9. (a) Write the SPICE program to find out the node voltage V_1 , V_2 , V_3 for the circuit shown below.



- (b) Write the input file in SPICE to determine the unit step response of a series RC circuit.

6 + 6 = 12

**CIRCUIT THEORY AND FILTERS
(ECEN 2105)**

Time Allotted : 3 hrs

Full Marks : 70


Figures out of the right margin indicate full marks.

*Candidates are required to answer Group A and
any 5 (five) from Group B to E, taking at least one from each group.*

Candidates are required to give answer in their own words as far as practicable.


**Group - A
(Multiple Choice Type Questions)**

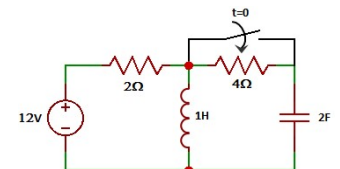1. Choose the correct alternative for the following: **10 × 1 = 10**
- (i) When port 1 of a two-port circuit is short-circuited, $I_1=4I_2$ and $V_2=0.25I_2$. Which of the following is true
 (a) $Y_{11} = 4$ (b) $Y_{12} = 16$ (c) $Y_{21} = 16$ (d) $Y_{22} = 0.25$.
- (ii) The average power delivered to an impedance $(4 - j3)\Omega$ by a current $5\cos(100\pi t + 100)$ A is
 (a) 44.2W (b) 50W (c) 62.5W (d) 125W.
- (iii) A DC voltage source is connected across a series RLC circuit. Under steady state condition, the applied DC voltage drops entirely across the
 (a) R only (b) L only
 (c) C only (d) R & L combination.
- (iv) A two-port is described by the following equations
 $V_1 = 50I_1 + 10I_2$
 $V_2 = 30I_1 + 20I_2$
 Which of the following is not true
 (a) $Z_{12} = 10$ (b) $Y_{12} = -0.0143$
 (c) $H_{12} = 0.5$ (d) $A = 50$.
- (v) A load is connected to a net work with $R_{th} = 10\Omega$ and $V_{th} = 40V$. The maximum power supplied to the load is
 (a) 160W (b) 80W (c) 40W (d) 1W.
- (vi) In the given figure the capacitor voltage at $t = 0$ is
 (a) 0V (b) 4V
 (c) 8V (d) 12V



- (b) To deliver maximum power to any load, show that the load impedance needs to be the complex conjugate of the Thevenin's equivalent impedance of the network.

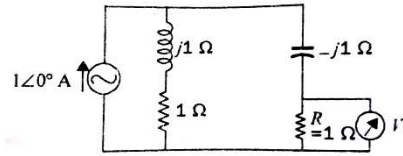
- (c) Find the reading of the voltmeter V in the given circuit. Interchange the current source and the voltmeter and verify the Reciprocity theorem.




$$5 + 3 + 4 = 12$$

Group - C

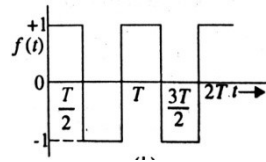4. (a) Find out the Laplace Transform of the given periodic waveform.




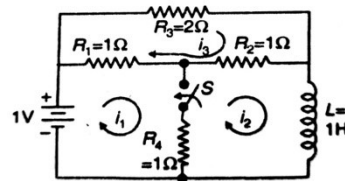- (b) A pulse excitation of height 'V' and width 'a' is applied to a series RC network. Derive the current $i(t)$ in the series circuit for $t \geq 0$. Also plot the voltages across the resistor and capacitor against time for $t \geq 0$.
- (c) The circuit shown below is initially in steady state with the switch S open. At $t = 0$, the switch S is closed. Obtain the current in the inductor for $t > 0$.




$$3 + (4 + 1) + 4 = 12$$

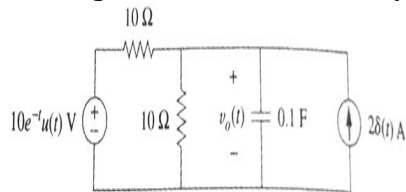5. (a) Find $V_0(t)$ in the circuit given below. Assume $V_0(0) = 5V$



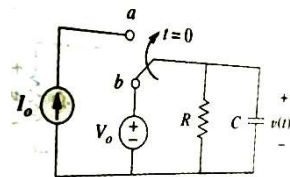
- (b) The switch in the given figure has been in position b for a long time. It is moved to position a at $t = 0$. Determine $v(t)$ for $t > 0$.




$$7 + 5 = 12$$

Group - D

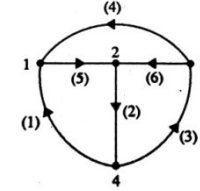6. (a) Find the reduced incidence and tie-set matrices for the graph given below.




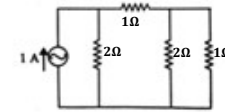- (b) Form the fundamental cut-set matrix for the given network and hence find the matrix form of KCL equations.




$$(3 + 3) + 6 = 12$$

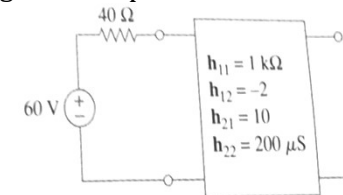7. (a) Determine the Thevenin's equivalent resistance R_{th} across the output terminals for the given two port network.



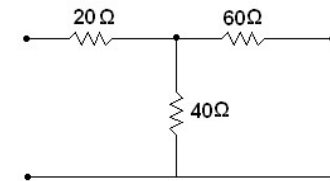- (b) Find the Z parameters and hybrid parameters for the circuit given below.



$$4 + (4 + 4) = 12$$

Group - E

8. (a) Derive the transfer function of the given circuit and identify the filter type and order.

