

**CIRCUIT THEORY AND NETWORKS
(AEIE 2102)**

Time Allotted : 3 hrs

Full Marks : 70

Figures out of the right margin indicate full marks.

*Candidates are required to answer Group A and
any 5 (five) from Group B to E, taking at least one from each group.*

Candidates are required to give answer in their own words as far as practicable.


**Group – A
(Multiple Choice Type Questions)**

1. Choose the correct alternative for the following: **10 × 1 = 10**
- (i) Norton current (I_N) of a circuit comprising of dependent source and resistive components is
 - (a) indeterminate
 - (b) $0A < I_N < 1A$
 - (c) $0A$
 - (d) finite value greater than $1A$
 - (ii) The Voltage division rule is valid for
 - (a) Series circuit
 - (b) Parallel Circuit
 - (c) Resonant circuit
 - (d) All of these
 - (iii) In an oriented graph, the reduced incidence matrix is used to find the number of
 - (a) valid trees
 - (b) KVL equations
 - (c) KCL equations
 - (d) all of the above.
 - (iv) The value of coefficient of coupling in a practical magnetically coupled circuit
 - (a) equal to 0
 - (b) equal to 1
 - (c) greater than one
 - (d) greater than zero but less than 1
 - (v) A reciprocal circuit should have only
 - (a) one independent source
 - (b) at least two independent sources
 - (c) dependent source
 - (d) independent and dependent sources
 - (vi) In an RLC series circuit the power factor at resonance is
 - (a) lagging
 - (b) leading
 - (c) unity
 - (d) zero
 - (vii) In a series resonant circuit, increasing inductance to its twice value and reducing capacitance to its half value
 - (a) will change the maximum value of current at resonance
 - (b) will change the resonance frequency
 - (c) will change the impedance at resonance frequency
 - (d) will alter the bandwidth of the circuit


- (viii) Time constant of an RL series circuit is
 (a) L/R (b) R/L (c) RL (d) R
- (ix) A network, described by ABCD paramaters, will be reciprocal if
 (a) $A=D$ (b) $(AD-BC)=1$ (c) $(AC-BD)=1$ (d) $(AD-BC)=0$
- (x) The number of links in an oriented graph having 7 branches and 5 nodes is
 (a) 3 (b) 4 (c) 5 (d) 7

Group - B

2. (a) Draw the Thevenin's equivalent circuit across the load R_2 of the circuit shown in the fig. 1. Find current through the load R_2 .

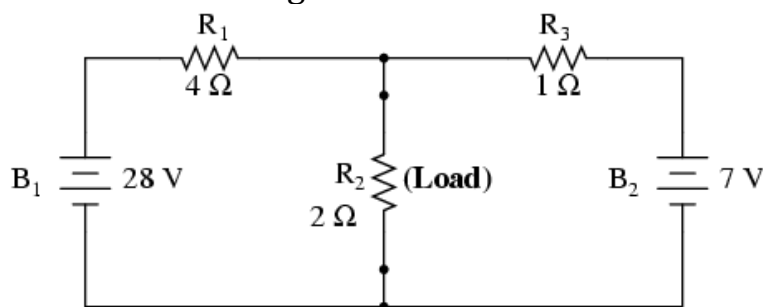
**Fig. 1**

- (b) In the circuit shown in fig. 2, find the values of V_1 and V_2

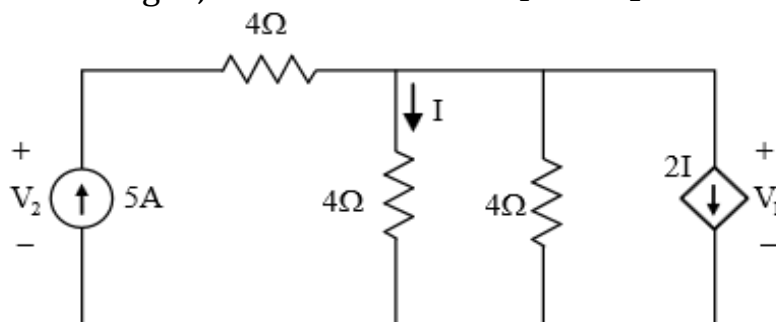
**Fig. 2**

$$(4 + 2) + 6 = 12$$

3. (a) For the circuit in the fig. 3, the following data are given:
 (i) 57% of the primary flux gets linked with the secondary
 (ii) $i_1(t) = 4 \sin 2t$ A, and
 (iii) $i_2 = 0$ A. Then find (A) the coefficient of coupling and (B) v_1 and v_2 .

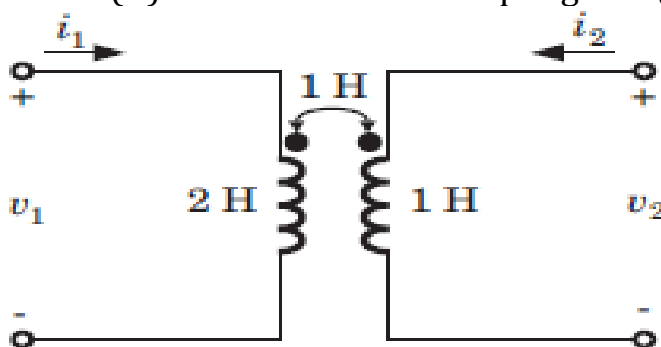**Fig. 3**

- (b) A series RLC circuit is excited with an ac voltage source as shown in the fig. 4. The quality factor (Q) of the circuit is given as $Q = 30$. Find the value of R in the circuit.

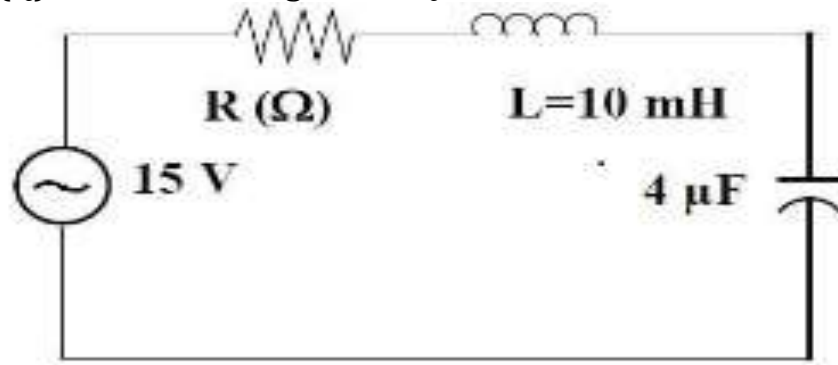**Fig. 4****(2 + 6) + 4 = 12****Group – C**

4. (a) An impulse voltage excites an RC circuit. Derive an expression of voltage across the capacitor using the concepts of Laplace transform. Assume that the circuit is initially relaxed.
- (b) In an RLC circuit, find the condition of the critically damped response.

6 + 6 = 12


5. (a) Find the inverse Laplace transform of the following function $F(s) = \frac{(s+3)}{(s+1)(s+2)}$

Using the initial value theorem, find the value of the above function at $t=0$

- (b) Write the Laplace transforms of the following time domain functions:
(i) Unit impulse (ii) unit step (iii) exponentially decaying and (iv) unit parabola.

(5 + 3) + 4 = 12**Group – D**


6. (a) Consider the electrical circuit shown in the fig. 5. Obtain the reduced incidence matrix.

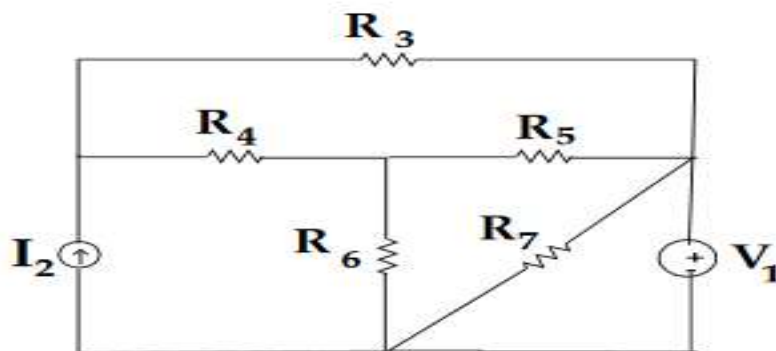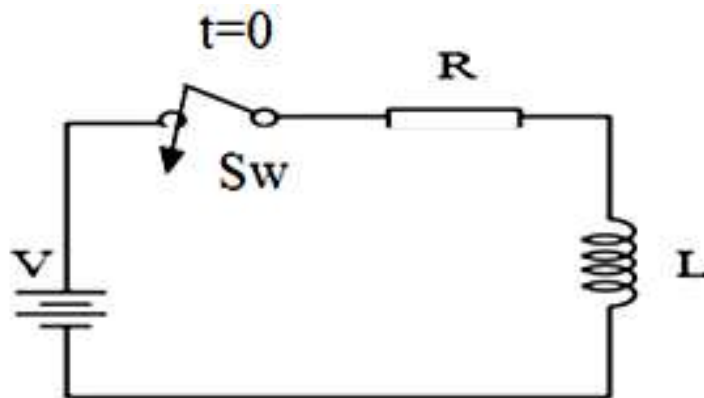**Fig. 5**

- (b) Find the total number of valid trees that may be obtained from the graph.

6 + 6 = 12

7. (a) A series RL circuit is excited at $t = 0$ by closing a switch (Sw) as shown in the fig. 6. Find (i) $i_L(0^+)$ (ii) $v_L(0^+)$ (iii) $i_L(\infty)$ (iv) $v_L(\infty)$.

**Fig. 6**

- (b) Express the Z-parameters in terms of the Y-parameters.

$$4 + (6 + 2) = 12$$

Group – E

8. (a) Draw the ideal and practical characteristics of a band-pass and a stop-band filter.

The driving point impedance of a circuit is given by $Z(s) = \frac{(s+1)}{s(s+2)}$


- (b) Realize a circuit using Cauer form-I.

$$(2 + 2) + 8 = 12$$

9. (a) The driving point impedance of a circuit is given by $Z(s) = \frac{(s+1)}{s(s+2)}$

Realize a circuit using any one of the Foster's forms (I or II).

- (b) A filter circuit, as shown in the fig. 7, receives a signal from a rectifier having certain frequency. Analyse the circuit to know the type of the filter.

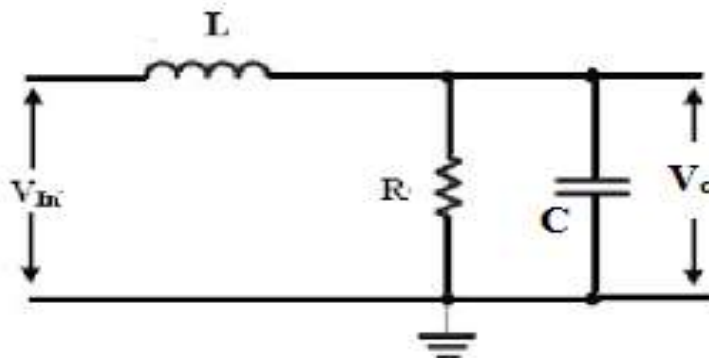**Fig. 7**

$$8 + 4 = 12$$

Department & Section	Submission Link
AEIE	https://classroom.google.com/c/Mjc0MDY4MTQxNTc3/a/Mjc0MDY4MTQxNTkx/details