

CIRCUIT THEORY AND FILTERS
(ECEN 2105)

Time Allotted: 3 hrs

Full Marks : 70

Figures out of the right margin indicate full marks.

Candidates are required to answer Group A and any 5 (five) from Group B to E, taking at least one from each group.

Candidates are required to give answer in their own words as far as practicable.

Group – A
(Multiple Choice Type Questions)

1. Choose the correct alternative for the following: **10 × 1 = 10**
- (i) Which of the following is not a reactive circuit element
 - (a) Capacitor
 - (b) Inductor
 - (c) Resistor
 - (d) None.
 - (ii) The voltage can never be exactly in phase with the current in a circuit that contains
 - (a) Only Capacitor
 - (b) Only Resistor
 - (c) Inductor & capacitor
 - (d) Inductor, capacitor & resistor.
 - (iii) The rank of a graph containing n number of nodes is
 - (a) n-1
 - (b) n
 - (c) 2n+1
 - (d) n+1.
 - (iv) In a series RC circuit, if the output is measured across the resistor, then the circuit can be considered as a
 - (a) Band Pass Filter
 - (b) Band Reject Filter
 - (c) Low Pass Filter
 - (d) High Pass Filter.
 - (v) The centre frequency of a bandpass filter is always equal to
 - (a) The bandwidth
 - (b) Arithmetic average of the cut off frequencies
 - (c) 3dB frequency
 - (d) The product of bandwidth & quality factor.

- (vi) If the Laplace Transform of $f(t)$ is $F(s)$, then the Laplace Transform of $f(t-\alpha)$ is
(a) $e^{-s\alpha} F(s)$ (b) $e^{s\alpha} F(s)$
(c) $F(s-\alpha)$ (d) $F(s+\alpha)$.
- (vii) For steady state in a circuit capacitor should behave as
(a) Short circuit (b) Open Circuit
(c) Voltage Source (d) Current Source.
- (viii) The condition for reciprocity of any two port network is
(a) $Z_{12} = Z_{21}$ (b) $Y_{12} = Y_{11}$
(c) $AD - BC = 0$ (d) $Z_{12} = Y_{12}$.
- (ix) The condition for a series RLC circuit to be under-damped when excited with a step input, is
(a) $(R^2/4L^2) > (1/LC)$ (b) $(R^2/4L^2) = (1/LC)$
(c) $(R^2/4L^2) < (1/LC)$ (d) None of these.
- (x) If two 6mH inductors are connected in parallel without mutual inductance, then the equivalent inductance is,
(a) 3Mh (b) 12mH (c) 36mH (d) 1mH.

Group – B

2. (a) Determine the condition for the maximum power transfer for a purely resistive circuit in which load resistance is variable.
- (b) In the circuit of Fig:1 find the power delivered by the current and voltage sources.

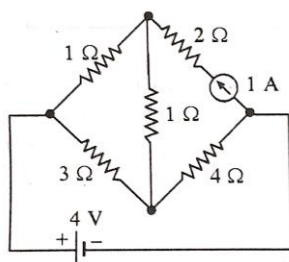


Fig: 1

5 + 7 = 12

3. (a) State the Thevenin's theorem. Find the Thevenin equivalent circuit across the terminals a and b of the following network of Fig:2.

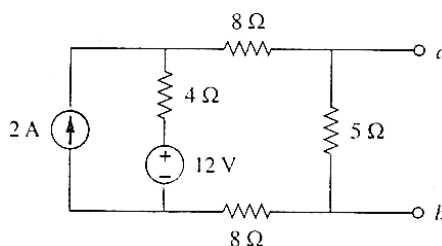


Fig: 2

- (b) Use star-delta transformation to find the input resistance offered between the terminals A & C in Fig: 3.

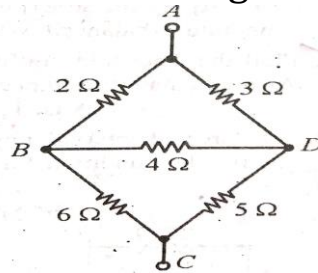


Fig: 3

$$(2+5) + 5=12$$

Group – C

4. (a) Derive the current expression for a series R-C network excited by a step input voltage $V_u(t)$ volt considering zero initial condition. Also plot the current.
- (b) The circuit of Fig: 4 is in steady state with the switch in position 'a'. The switch is moved to position 'b' at $t = 0$. Find the current in the inductor for all t .

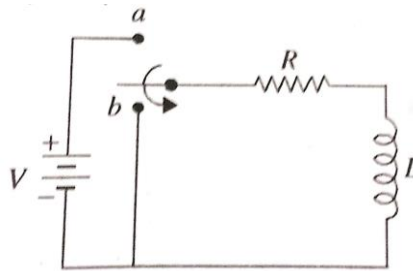


Fig : 4

$$(5 + 1) + 6=12$$

5. (a) In the circuit of Fig:5, determine the voltage $v(t)$ and the currents $i_R(t)$ and $i_L(t)$ for $t > 0$. The circulating current at $t = 0$ in RL loop is 1A clockwise.

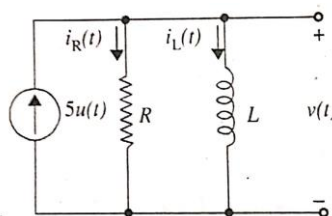


Fig: 5

- (b) Determine the Laplace transform of the periodic function in Fig:6.

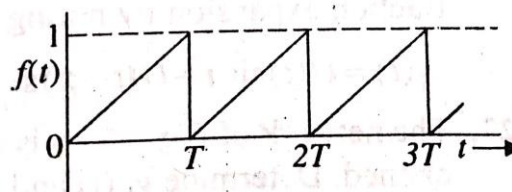


Fig: 6

$$6 + 6=12$$

Group - D

6. (a) Find the tie-set and f-cut-set matrices using the given graph of Fig:7.

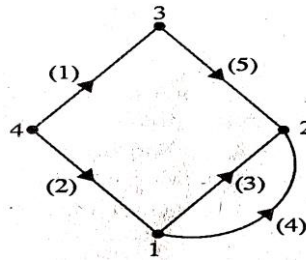


Fig:7

- (b) How many trees are possible for the graph of the network of Fig : 8.

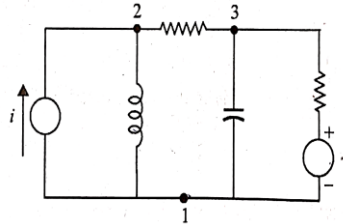


Fig: 8

$$6 + 6 = 12$$

7. (a) What do you mean by driving point impedance of a network? Two four terminal networks are connected in cascade, show that the transmission parameter matrix of the overall network is the sum of the transmission parameter matrices of the individual network.

- (b) Determine the z-parameters for network of Fig:9.

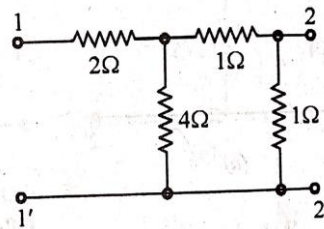


Fig : 9

$$(2+4) + 6 = 12$$

Group - E

8. (a) Derive the transfer function of the circuit of Fig:10. Find the passband gain. Sketch the proper frequency response and identify the filter.

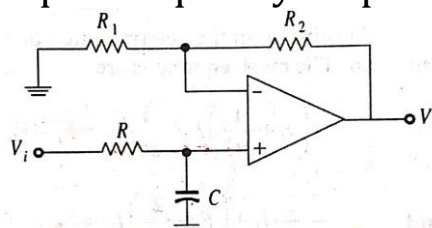


Fig : 10

- (b) Design a 1st order low pass filter having a dc gain of 5 and corner frequency of 1000Hz using ideal OPAMP.

$$(4+2+2) + 4 = 12$$

9. (a) Write the input file in PSPICE for the following circuit of Fig:11 to find the node voltages.

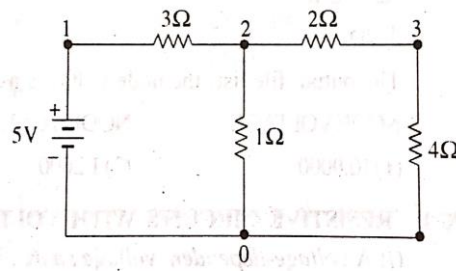


Fig: 11

- (b) Write the input file in PSPICE to determine i and v for the given circuit of Fig: 12 which is initially relaxed. The switch S is closed at time $t = 0$.

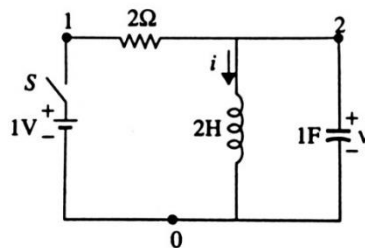


Fig: 12

6 + 6=12

Department & Section	Submission Link (for Backlog)
ECE	https://classroom.google.com/c/Mjc0NDM1ODA0MDA4?cjc=vpbpst5

